

MODULAR ELECTRONICS LEARNING (MODEL) PROJECT



SPICE MODELING OF POWER CIRCUITS

© 2016-2024 BY TONY R. KUPHALDT – UNDER THE TERMS AND CONDITIONS OF THE
CREATIVE COMMONS ATTRIBUTION 4.0 INTERNATIONAL PUBLIC LICENSE

LAST UPDATE = 6 SEPTEMBER 2024

This is a copyrighted work, but licensed under the Creative Commons Attribution 4.0 International Public License. A copy of this license is found in the last Appendix of this document. Alternatively, you may visit <http://creativecommons.org/licenses/by/4.0/> or send a letter to Creative Commons: 171 Second Street, Suite 300, San Francisco, California, 94105, USA. The terms and conditions of this license allow for free copying, distribution, and/or modification of all licensed works by the general public.

Contents

1	What is SPICE?	3
2	Using SPICE	5
2.1	Summary of steps	7
2.2	Demonstration on Microsoft Windows	8
2.2.1	Invoking a text editor	8
2.2.2	Saving the deck	9
2.2.3	Invoking SPICE	11
2.2.4	Viewing the SPICE analysis	12
2.3	Demonstration on Linux or CygWin	13
2.3.1	Invoking a text editor	13
2.3.2	Saving the deck	14
2.3.3	Invoking SPICE	15
2.3.4	Viewing the SPICE analysis	16
2.4	Demonstration of NGSPICE interactive mode	17
2.4.1	Creating the netlist	18
2.4.2	Starting NGSPICE	18
2.4.3	Verifying the loaded netlist	19
2.4.4	Running the analysis	19
2.4.5	Printing a voltage	20
2.4.6	Plotting graphs using NGSPICE	21
2.4.7	Issuing multiple commands in a single line	22
2.5	Idiosyncrasies of SPICE	23
2.5.1	Beginning and ending cards	23
2.5.2	Node zero	23
2.5.3	Current measurement	23
2.5.4	Open and short circuits	24
2.5.5	Multiple sources	25
2.5.6	Multiple inductors/capacitors	26
3	SPICE component descriptions	27
3.1	Independent voltage sources	28
3.1.1	Example: DC source	28
3.1.2	Example: “Dummy” source	28

3.1.3	Example: AC source	29
3.1.4	Example: Sinusoidal source	31
3.1.5	Example: Pulse source	32
3.2	Independent current sources	33
3.2.1	Example: DC source	33
3.2.2	Example: AC source	33
3.3	Resistors	34
3.3.1	Example	34
3.4	Capacitors	35
3.4.1	Example: Capacitor with initial charge	35
3.4.2	Example: Uncharged capacitor	35
3.5	Inductors	36
3.5.1	Example: Inductor with initial charge	36
3.5.2	Example: Uncharged inductor	36
3.6	Transformers	37
3.6.1	Example: 2:1 ratio step-down transformer	37
3.7	Transmission lines	38
3.7.1	Example: 50-Ohm transmission line with 10 nanosecond delay	38
3.7.2	Example: half-wavelength (at 35 MHz) 300-Ohm transmission line	38
3.8	Linear dependent sources	39
3.8.1	Example: voltage-controlled voltage source	40
3.8.2	Example: voltage-controlled current source	40
3.9	Nonlinear dependent sources	41
3.9.1	Example: multiplier	41
3.10	Diodes	42
3.10.1	Example: Generic diode	42
3.10.2	Example: 1N4001	43
3.11	Bipolar Junction Transistors (BJTs)	44
3.11.1	Example: Generic NPN transistor	45
3.11.2	Example: 2N2907	45
3.12	Junction Field-Effect Transistors (JFETs)	46
3.12.1	Example: Generic N-channel JFET	47
3.13	Metal-Oxide Field-Effect Transistors (MOSFETs)	48
3.13.1	Example: Generic N-channel depletion-type MOSFET	49
3.13.2	Example: Generic N-channel enhancement-type MOSFET	49
3.13.3	Example: Generic P-channel depletion-type MOSFET	50
3.13.4	Example: Generic P-channel enhancement-type MOSFET	50
3.14	Subcircuits	51
3.14.1	Example: resistor subnetwork	52
3.14.2	Example: solar cell array	53
4	SPICE analysis descriptions	55
4.1	DC voltage/current “sweep” analysis	56
4.1.1	Example: sweep of voltage source	56
4.1.2	Example: sweep of voltage and current sources	56
4.2	AC frequency “sweep” analysis	57

4.2.1	Example: linear frequency sweep	57
4.2.2	Example: decade logarithmic frequency sweep	57
4.2.3	Example: octave logarithmic frequency sweep	57
4.3	Transient analysis	58
4.3.1	Example: using initial conditions, beginning at time $t = 0$	58
4.3.2	Example: using initial conditions, beginning at non-zero time	58
4.4	Fourier analysis	59
4.4.1	Example: analysis of 60 Hz waveform	59
4.5	Display option: print	60
4.5.1	Example: printing a DC analysis	60
4.5.2	Example: printing an AC analysis	60
4.6	Display option: plot	61
4.6.1	Example: plotting a DC analysis	61
4.6.2	Example: plotting an AC analysis	61
4.6.3	Example: plotting a transient analysis	62
4.6.4	Example: plotting parametric functions	62
4.7	Display option: width	63
4.7.1	Example	63
5	Primitive circuit examples	65
5.1	DC voltage source with .op analysis	66
5.2	DC voltage source with single-point .dc sweep analysis	70
5.3	DC current source with single-point .dc sweep analysis	73
5.4	DC voltage source with multi-point .dc sweep analysis	74
5.5	AC voltage source with single-point .ac sweep analysis	77
5.6	AC voltage source with multi-point .ac sweep analysis	78
5.7	Additive AC voltage sources with single-point .ac sweep analysis	82
5.8	Transient analysis of discharging RC circuit	84
5.9	Transient analysis of a steady sinusoidal voltage source	89
5.10	Transient analysis of a sinusoidal capacitive circuit	92
5.11	Transient analysis of a damped, offset sinusoidal voltage source	95
5.12	Additive AC voltage sources with transient analysis	98
5.13	Solar cell array simulation	100
5.14	Solar panel array simulation	103
6	Gallery	109
6.1	Using gallery examples for practice	110
6.2	Three-phase AC direct-coupled circuits	111
6.2.1	Wye source, Wye load	111
6.2.2	Wye source, Wye load with shunt resistors	115
6.2.3	Wye source, Delta load	118
6.2.4	Wye source, Delta load with shunt resistors	123
6.2.5	Delta source, Wye load	127
6.2.6	Delta source, Wye load with shunt resistors	130
6.2.7	Delta source, Delta load	135
6.2.8	Delta source, Delta load with shunt resistors	140


CONTENTS	1
6.2.9 Wye source with phase-to-phase fault	145
6.3 Three-phase AC transformer circuits	148
6.3.1 Wye primary, Wye secondary	148
6.3.2 Wye primary, Delta secondary	151
6.3.3 Delta primary, Wye secondary	151
6.3.4 Delta primary, Delta secondary	151
A Problem-Solving Strategies	153
B Instructional philosophy	155
C Tools used	161
D Creative Commons License	165
E References	173
F Version history	175
Index	176

Chapter 1

What is SPICE?

SPICE is a general-purpose computer simulator for electronic circuits, with several “freeware” versions available for academic use. Although its text-based user interface may seem clumsy and archaic at first, it is quite powerful, and also neatly side-steps the many problems students tend to experience with graphic-entry (“WYSIWYG”)¹ circuit simulators.

Circuits are described to SPICE in the form of a *netlist*, which is a text-based code listing of each component within the circuit, the “nodes” connecting them to each other, and the types of analyses requested of SPICE to perform on that circuit. A simple three-resistor DC circuit is shown in schematic form below, along with the netlist you would write and input to SPICE instructing it to analyze this circuit for a single source voltage value of 15 Volts and displaying the voltage drop across each resistor as well as the current through the voltage source:

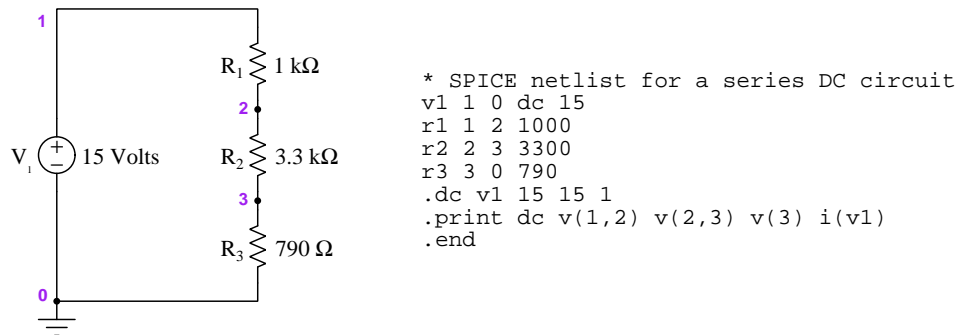

The purpose of this document is to give a general introduction to the use of SPICE, and also to showcase a “gallery” of examples where SPICE is used to perform analyses on circuits containing semiconductor components. This gallery will not only help new users of SPICE learn how to format netlists and interpret analyses, but they also serve as an extensive bank of practice problems for new students of electricity and electronics to use as they build and sharpen their circuit analysis skills.

This last point deserves some elaboration. The study of electricity and electronics, like all scientific studies, is aided by the solution of practice problems. Problem-solving is a skill like any

¹“WYSIWYG” is an acronym meaning *What You See Is What You Get*.

other, and practice helps to build an arsenal of tools useful to any new problems you may encounter. Having answers provided for these problems allows students to check their work and to self-identify any misconceptions or bad problem-solving habits.

Traditional textbooks provide banks of practice problems for students to solve, and while these are useful, the availability of computer simulation software take this concept one enormous step further. Not only may the sample simulations given in this learning module serve as practice problems for students, but they will also serve as templates for creating one's own practice problems, so you will never be wanting for more practice opportunities. Like all computer simulations, SPICE rigorously applies known laws and principles of physics to predict how specific systems will behave, and as such it never makes mistakes².

SPICE has played a pivotal role in my own self-education on the topic of circuits, being an excellent tool to check my own analytical skills and to explore the properties of certain devices (e.g. transistors, transmission lines, transformers) with relative ease. The ultimate goal of any scientific education is to equip the student with mental tools to solve problems and to continue their own learning. SPICE is a software tool that can aid in the development of these mental tools, and should be used as such.

²Some simulations can and do miss certain details if they are not set up properly, but this is not the same kind of error as a human is prone to committing, and it is precisely this difference between computers and humans that makes computer simulations useful learning tools. Simply put, the computer will not repeat *your* mistakes.

Chapter 2

Using SPICE

SPICE is computer software designed to simulate the behavior of electric circuits. It was developed in the early days of digital computing when the dominant user interface was the *command prompt*, and the most common user file format was plain “ASCII” text. Graphic, mouse- or touchscreen-driven interfaces simply did not exist at that time except for prototype systems or highly specialized applications. Most general-purpose computing of that era occurred through the use of a keyboard and a monochrome text-based monitor, or worse yet in the form of punched paper cards and teletyped output.

This is why SPICE usage seems to resemble text-based code programming. The user (that means *you*) enters a description of the circuit to be analyzed and the analysis/display methods preferred by means of typed text, then the SPICE program is run and the output is viewed again in text form.

This may all seem terribly anachronistic in the 21st century, but there are some decided advantages to using SPICE with this legacy interface:

- These legacy versions of SPICE are free to use. No license fees, nothing.
- The relatively small (by modern standards) SPICE software runs very fast on modern computers.
- Circuits that are challenging to graphically draw are easy to “code”
- Errors resulting from the computer’s incorrect interpretation¹ of a diagram are eliminated
- Learning to use SPICE in this manner is an excellent orientation to simple programming

The first step in setting up SPICE to analyze a circuit is to describe that circuit using SPICE’s own language, and to type this description into a plain-text file on your computer. This file is often referred to as a *deck*, with each line of text in that file called a *card*. Taken together, those lines of text (a.k.a. *cards*) comprise a *netlist* describing the circuit and the intended analysis for SPICE. The

¹I have struggled multiple times to get a WYSIWYG circuit analyzer program to simply analyze what I have drawn, due to “hidden” wire connections, or intended wire connections that don’t exist – all “bugs” in the software stemming from the non-trivial challenge of getting a computer to recognize and correctly interpret a hand-made diagram. SPICE, with its “netlist” input and clear node-labeling protocol, neatly eliminates this whole problem.

anachronistic terms “card” and “deck” harken back to the days of punched-card input for computer systems, where each separate instruction for SPICE was a series of punched holes on its own paper card, the collection of cards representing one circuit being a “deck of cards” that would be fed into the card reader one at a time².

Once you have typed the netlist and saved it as a text file (a.k.a. *deck*) to your computer, you are ready to run a SPICE analysis on it. This is done by typing the word `spice` on a command-line interface³ followed by a less-than symbol (<) and then followed by the name of the text file “deck”, and finally terminated by pressing the Enter key. Here is an example, showing a screenshot of a SPICE analysis about to happen on a “deck” file named `test.cir` just prior to pressing the Enter key:

A screenshot of a terminal window. The title bar at the top reads "File Edit View Terminal Go Help". The terminal content shows a prompt "[tony@Renegade ~]" followed by the command "spice < test.cir" with a green cursor at the end. The rest of the terminal area is black.

After entering this command, SPICE performs its analysis and by default dumps a report as plain text to the same command-line terminal. If you desire to save SPICE’s text output to another plain-text file for posterity, or to be able to paste that analysis into another document, you may “redirect” SPICE to send its plain-text analysis to another file of your choosing by using the greater-than symbol (>) in the command. Here is an example showing how to instruct SPICE to read the contents of `test.cir` and place all the analysis text into another file named `test.out`:

```
spice < test.cir > test.out
```

²Interestingly, legacy versions of SPICE do not care what order these “cards” appear in the “deck” with the exception of the first line (the Title) and the last line (the `.end`) statement.

³Microsoft Windows operating systems provide a general-purpose command line interface terminal named `cmd`. Unix-based systems such as Apple’s OS X and Linux typically offer a variety of terminal programs suitable for this purpose.

2.1 Summary of steps

To summarize, using SPICE in this legacy format requires the use of a *text editor* program (such as “Notepad” on Microsoft Windows operating systems) to write the netlist, and a command-line interface on your computer to invoke SPICE to perform its analysis. The sequence of steps may be listed:

1. Invoke a text editor program and type the netlist (instructions) describing the circuit and the type of analysis you wish SPICE to perform
2. Save this netlist as a plain-text file to your computer
3. Type `spice < deck_filename` on the command-line interface and then press Enter
4. View the analysis in the command-line interface


Most of SPICE’s “learning curve” is in becoming familiar with the syntax of the netlist: exactly which letters, numbers, and sequences must be entered in order to properly describe the circuit and the type(s) of analysis desired. A few cardinal rules must be obeyed when creating or editing netlists:

- The first line (card) of the netlist is the Title. It cannot be omitted.
- The last line (card) of the netlist is the `.end` command. It cannot be omitted.
- Each and every unique connection point in the circuit must be assigned a number called a *node*. This is how you describe the “shape” of the circuit to SPICE: by describing which nodes each component connects to. Components sharing common node numbers are electrically common to each other; components with differing node numbers are electrically distinct from each other. There *must* be a node 0, and this is the “Ground” node of the circuit.

2.2 Demonstration on Microsoft Windows

Here I will demonstrate this four-step process as a series of screenshots from a computer running SPICE version 2G6 on the Microsoft Windows version 7 operating system.


2.2.1 Invoking a text editor

 

Here, the screenshot shows an empty file, ready for me to type text. *Text editors* are similar to *word processors* except they lack provision for neatly formatting the text (e.g. no font selections, no paragraph formatting, etc.). Their sole purpose is to facilitate the creation and editing of plain-text files.

Text editors are the go-to application for practically all text-based computer programming. *Many* different text editors exist, each with their own features, and computer programmers tend to develop a fondness for one particular editor that best suits their programming needs. A “stock” text editor comes with every version of Microsoft Windows called `notepad`, but this editor is extremely limited in its capabilities, and I do not recommend it. The editor shown here (`notepad++`) is *vastly* superior and highly recommended.

2.2.2 Saving the deck

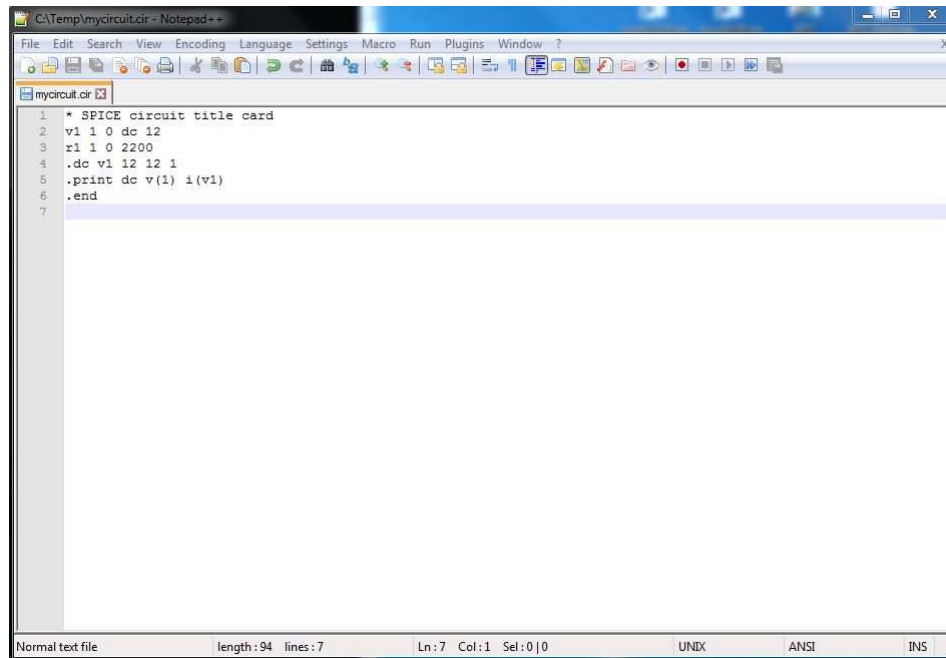

```

1 * SPICE circuit title card
2 v1 1 0 dc 12
3 r1 1 0 2200
4 .dc v1 12 12 1
5 .print dc v(1) i(v1)
6 .end
7

```

Here, I have chosen the filename `mycircuit.cir` for the deck. Note that you do not have to end every deck filename with the suffix “.cir” – this is simply my personal choice. Any filename consistent with the naming conventions of your computer’s filesystem and containing no space characters is permissible. We avoid space characters because command-line interfaces typically interpret spaces as delimiting characters designed to separate commands and filenames from each other. If you must have a “space” in your filename, use an underscore character or a dash (_ or -). For example, `my_circuit` is acceptable, but `my circuit` is not.

Here is a line-by-line (a.k.a. *card-by-card*) interpretation of the netlist:


```

* SPICE circuit title card This is the arbitrary “title” line
v1 1 0 dc 12 Defines a 12 Volt DC voltage source named “v1” between nodes 1 and 0
r1 1 0 2200 Defines a 2200 Ohm resistor between nodes 1 and 0
.dc v1 12 12 1 Requests a DC “sweep” analysis from 12 Volts to 12 Volts on source “v1”
.print dc v(1) i(v1) Measures the voltage at node 1 and current through source “v1”
.end Tells SPICE to stop


```

Note how components are “connected” to each other in the netlist by common node (connection-point) numbers. This is how SPICE is able to “picture” circuits without the use of graphical images. Each electrically distinct point in a circuit is given a unique number, and different components specified by the points they’re connected to.

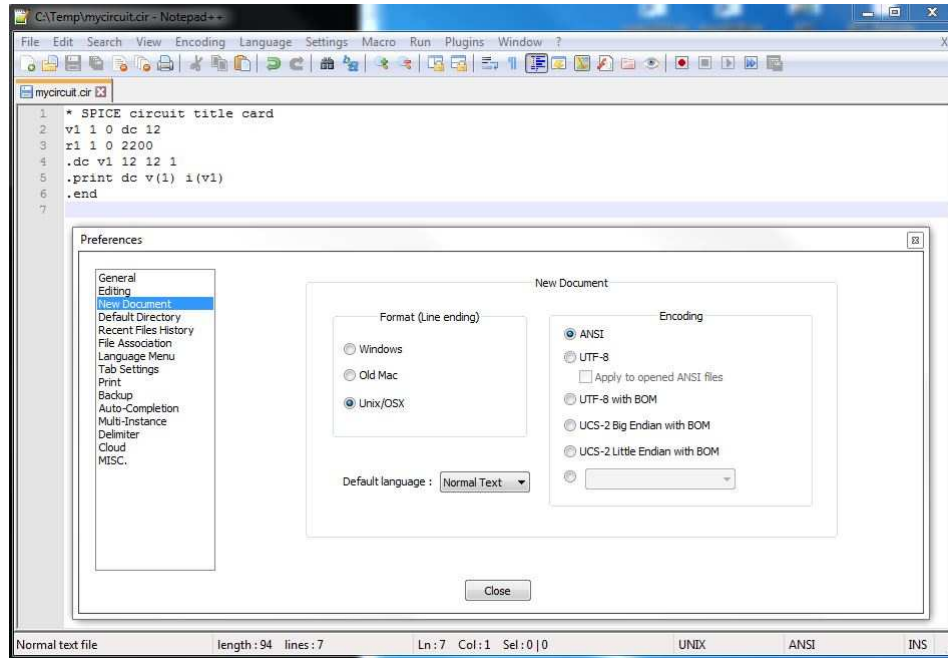An idiosyncrasy of SPICE version 2G6 is that it must receive its “deck” file in Unix text format rather than Windows text format. Thankfully, `notepad++` provides a means to select which text format the deck file will be written in, as shown in this screenshot of the “Preferences” dialog window:



2.2.3 Invoking SPICE

 

This screenshot shows the command-line interface terminal (not the text editor), with the command ready to enter. This terminal may be access on any Windows operating system by invoking the `cmd` command.

Note that the exact command being entered here is `spice.exe < mycircuit.cir` because the SPICE executable file installed on this computer is named `spice.exe` rather than just `spice`.

2.2.4 Viewing the SPICE analysis

```

C:\Windows\system32\cmd.exe
C:\Temp>spice.exe < mycircuit.cir
1*****09/12/16 ***** spice 2g.6  3/15/83 *****13:13:17*****
0* spice circuit title card
0****   input listing           temperature =  27.000 deg c
0*****
v1 1 0 dc 12
r1 1 0 2200
.dc v1 12 12 1
.print dc v(1) i(v1)
.end
1*****09/12/16 ***** spice 2g.6  3/15/83 *****
*****13:13:17*****
0* spice circuit title card
0****   dc transfer curves           tempe
rature =  27.000 deg c
0*****
v1      v(1)      i(v1)
x
1.200E+01  1.200E+01  -5.455E-03
y
0
0      job concluded
0      total job time      .00
C:\Temp>

```


As you can see, SPICE is a very “chatty” program that displays a fair amount of extraneous text on the screen following an analysis. Ignoring all the headings and labels, you can see in this display a reiteration of the original netlist (deck) followed by the requested measurements of $v(1)$ (i.e. voltage between node 1 and ground, which is node 0) and $i(v1)$ (current through source $v1$).

This concludes a *very* brief orientation on using SPICE. For more information, I refer you to the following sections on SPICE component descriptions and analysis descriptions, as well as to the “Gallery” chapter which shows you tested SPICE netlists and output results so you may learn by example.

2.3 Demonstration on Linux or CygWin

Now, I will show you this same four-step process using SPICE version 2G6 running under the Linux operating system. The steps shown here are virtually identical within the “CygWin” emulator which adds a Unix-like command line environment to any Microsoft Windows operating system.

2.3.1 Invoking a text editor

 

Here, the screenshot shows an empty file, ready for me to type text. *Text editors* are similar to *word processors* except they lack provision for neatly formatting the text (e.g. no font selections, no paragraph formatting, etc.). Their sole purpose is to facilitate the creation and editing of plain-text files.

Text editors are the go-to application for practically all text-based computer programming. *Many* different text editors exist, each with their own features, and computer programmers tend to develop a fondness for one particular editor that best suits their programming needs. I personally prefer `gvim` (or `vim` in the CygWin emulator) and loathe the Microsoft `notepad`, but text editors tend to be a highly personal choice.

2.3.2 Saving the deck

```

File Edit Tools Syntax Buffers Window Help
* SPICE circuit title card
v1 1 0 dc 12
r1 1 0 2200
.dc v1 12 12 1
.print dc v(1) i(v1)
.end
"mycircuit.cir" [New] 6L, 93C written 1,1 All

```

Here, I have chosen the filename `mycircuit.cir` for the deck. Note that you do not have to end every deck filename with the suffix `“.cir”` – this is simply my personal choice. Any filename consistent with the naming conventions of your computer’s filesystem and containing no space characters is permissible. We avoid space characters because command-line interfaces typically interpret spaces as delimiting characters designed to separate commands and filenames from each other. If you must have a “space” in your filename, use an underscore character or a dash (`_` or `-`). For example, `my-circuit` is acceptable, but `my circuit` is not.

Here is a line-by-line (a.k.a. *card-by-card*) interpretation of the netlist:


```

* SPICE circuit title card This is the arbitrary “title” line
v1 1 0 dc 12 Defines a 12 Volt DC voltage source named “v1” between nodes 1 and 0
r1 1 0 2200 Defines a 2200 Ohm resistor between nodes 1 and 0
.dc v1 12 12 1 Requests a DC “sweep” analysis from 12 Volts to 12 Volts on source “v1”
.print dc v(1) i(v1) Measures the voltage at node 1 and current through source “v1”
.end Tells SPICE to stop

```

Note how components are “connected” to each other in the netlist by common node (connection-point) numbers. This is how SPICE is able to “picture” circuits with no graphics. Each and every electrically distinct point in a circuit is given a unique number, component placement being specified by these numbered connection points.

2.3.3 Invoking SPICE

 

This screenshot shows the command-line interface terminal (not the text editor), with the command ready to enter.

2.3.4 Viewing the SPICE analysis

```

File Edit View Terminal Go Help
[tony@Renegade ~]$ spice < mycircuit.cir
1*****09/06/16 ***** spice 2g.6 3/15/83 *****17:54:03*****

0* spice circuit title card
0**** input listing temperature = 27.000 deg c
0*****
*****

v1 1 0 dc 12
r1 1 0 2200
.dc v1 12 12 1
.print dc v(1) i(v1)
.end
1*****09/06/16 ***** spice 2g.6 3/15/83 *****17:54:03*****
*****

0* spice circuit title card
0**** dc transfer curves temperature = 27.000 deg c
0*****
*****

v1          v(1)          i(v1)
x
1.200E+01   1.200E+01   -5.455E-03
y
0
job concluded
total job time 0.00
[tony@Renegade ~]$

```

As you can see, SPICE is a very “chatty” program that displays a fair amount of extraneous text on the screen following an analysis. Ignoring all the headings and labels, you can see in this display a reiteration of the original netlist (deck) followed by the requested measurements of $v(1)$ (i.e. voltage between node 1 and ground, which is node 0) and $i(v1)$ (current through source $v1$).

This concludes a *very* brief orientation on using SPICE. For more information, I refer you to the following sections on SPICE component descriptions and analysis descriptions, as well as to the “Gallery” chapter which shows you tested SPICE netlists and output results so you may learn by example.

2.4 Demonstration of NGSPICE interactive mode

A more modern (yet still free) version of SPICE is NGSPICE which provides all the old command-line functionality of legacy SPICE versions, plus a window-based *interactive* mode where you may call for certain analyses of a circuit without editing the netlist (deck file). This interactive display window contains a command-entry field as well as a display showing the results of those commands. The procedure for doing this, which I have tested on NGSPICE version 26 on a computer running the Microsoft Windows 7 operating system, is as follows:


1. Create the netlist using your favorite text editor and save it under a convenient filename in a convenient location. I will arbitrarily choose the filename `test.cir` for this demonstration.
2. Start the interactive version of NGSPICE and then enter the command `source test.cir` to instruct it to read the contents of that netlist file. Alternatively, instruct the Windows operating system to associate all `*.cir` files with NGSPICE by right-clicking on the file's icon and choosing the "Open with..." option, selecting `ngspice.exe` as the application you *always* wish to use for opening any `.cir` files. From then on, all netlist files ending in `.cir` will appear as icons bearing the NGSPICE logo, and double-clicking on it will start NGSPICE and automatically run the `source` instruction. *You should be able to skip this filename-association step for all future uses of NGSPICE.*
3. (Optional) – Type `listing` and press Enter to execute the "listing" command. NGSPICE will print the netlist in its display window, letting you verify that NGSPICE has loaded your intended netlist.
4. Enter the `run` command.
5. Enter various display commands such as `print` and `plot`. If you choose to plot results using the `plot` command, for example if you are testing a circuit's response over a range of time, or of source values swept over a specified interval, NGSPICE will open up an additional graphic window showing the results in color. When in doubt, `print all` and `plot all` are good display commands to try.

If you decide to alter the circuit after having run an analysis, simply close down NGSPICE, edit the netlist file using your text editor (re-saving that file), and then re-open NGSPICE by double-clicking on the netlist file icon again. Then, just issue the `run` command followed by any display commands you wish.

A very nice feature of this interactive mode is the ability to recall past commands without the need to re-type them. Simply press the "up" and down "arrow" keys to recall all past typed commands from history buffer, then press Enter to re-issue that command. This will save you much time and potential for keystroke errors!

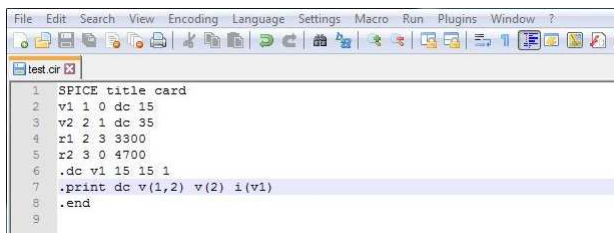2.4.1 Creating the netlist

To begin our demonstration, we will first create a netlist using a text editor. In this case, the editor happens to be `notepad++` which is much more capable than the stock `notepad` that comes with Microsoft Windows. After writing the netlist, it will be saved under the filename `test.cir`:




```

1 SPICE title card
2 v1 1 0 dc 15
3 v2 2 1 dc 35
4 r1 2 3 3300
5 r2 3 0 4700
6 .dc v1 15 15 1
7 .print dc v(1,2) v(2) i(v1)
8 .end
9

```

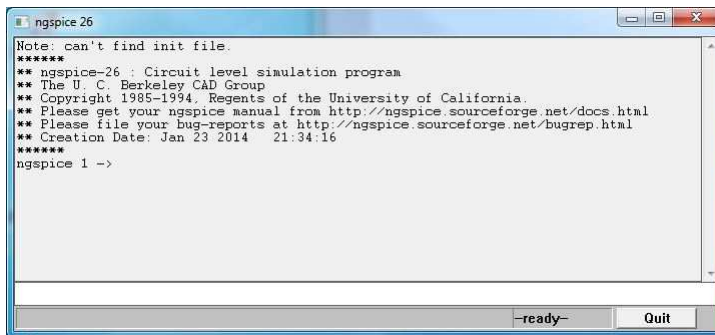2.4.2 Starting NGSPICE

When NGSPICE is started with no command-line arguments (or simply started by double-clicking on the `ngspice.exe` filename), you will see this interactive window appear on your computer's screen. Commands are typed into the rectangular field at the bottom of the window, and after pressing Enter you will see the results of that command displayed in the upper portion of the window:



```


ngspice 26
Note: can't find init file.
*****
** ngspice-26 : Circuit level simulation program
** The U. C. Berkeley CAD Group
** Copyright 1985-1994, Regents of the University of California.
** Please get your ngspice manual from http://ngspice.sourceforge.net/docs.html
** Please file your bug-reports at http://ngspice.sourceforge.net/bugrep.html
** Creation Date: Jan 23 2014 21:34:16
*****
ngspice 1 ->

```

Please note that if you take the time to associate `.cir` files with NGSPICE in Microsoft Windows, this step (as well as the “Loading the netlist” step and “Verifying the loaded netlist” step) will be performed automatically for you whenever you double-click on the netlist file icon. You will know you have been successful in setting up this association if all files with filenames ending in `.cir` appear with the NGSPICE logo in their Windows icons.

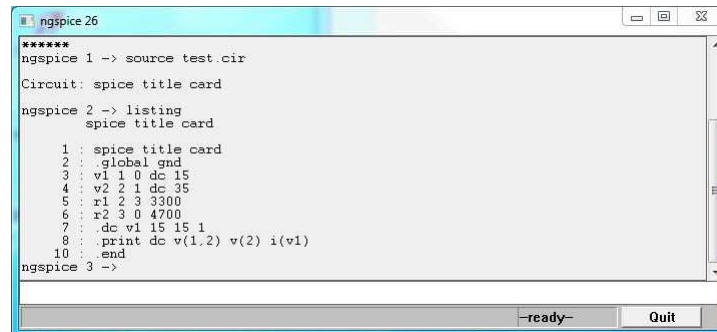2.4.3 Verifying the loaded netlist

Now we will verify the successful loading of our netlist by issuing the `listing` command. Our netlist now appears in the display window:



```


ngspice 26
*****
ngspice 1 -> source test.cir
Circuit: spice title card
ngspice 2 -> listing
spice title card
1 : spice title card
2 : .global gnd
3 : v1 1 0 dc 15
4 : v2 2 1 dc 35
5 : r1 2 3 3300
6 : r2 3 0 4700
7 : .dc v1 15 15 1
8 : .print dc v(1,2) v(2) i(v1)
10 : .end
ngspice 3 ->
ready Quit

```

This step is optional, but is a good habit. If you approach SPICE as a learning tool, using it to run simulated experiments on virtual circuits to help you master certain electrical concepts, you will find yourself making many changes to your netlists and re-running analyses on those revised circuits. The `listing` step gives you opportunity to verify each time that your edited netlist has been loaded into NGSPICE and is ready for analysis. It also shows, as in this case, if NGSPICE inserted any statements of its own (e.g. `.global gnd`).

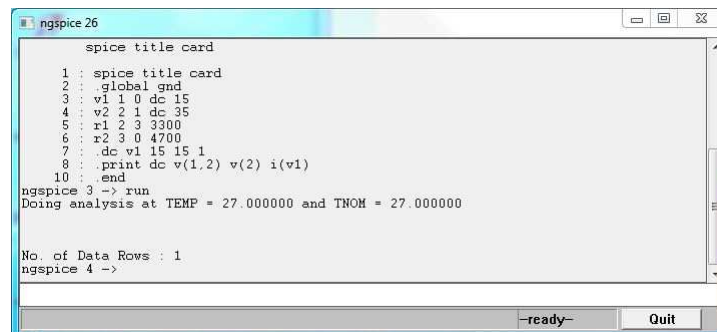2.4.4 Running the analysis

Before we may request any displayed results from NGSPICE, we must issue the `run` command:



```

ngspice 26
spice title card
1 : spice title card
2 : .global gnd
3 : v1 1 0 dc 15
4 : v2 2 1 dc 35
5 : r1 2 3 3300
6 : r2 3 0 4700
7 : .dc v1 15 15 1
8 : .print dc v(1,2) v(2) i(v1)
10 : .end
ngspice 3 -> run
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000


No. of Data Rows : 1
ngspice 4 ->
ready Quit

```

An interesting feature of NGSPICE is that it ignores the `print` command within the netlist. Running the simulation merely performs the calculations, but provides no automatic output of results. In the “interactive” version of NGSPICE, it waits for you to enter specific commands before actually displaying any results to the screen. Even with `.print` or `.plot` instructions (cards) contained in the netlist, NGSPICE’s interactive mode demands you type the display command yourself after it has “run” the simulation. To print the voltage between nodes 1 and 2, for example, you would enter the command `print v(1,2)`. NGSPICE relies on the analysis option in the netlist to discern whether this is a DC or AC analysis.

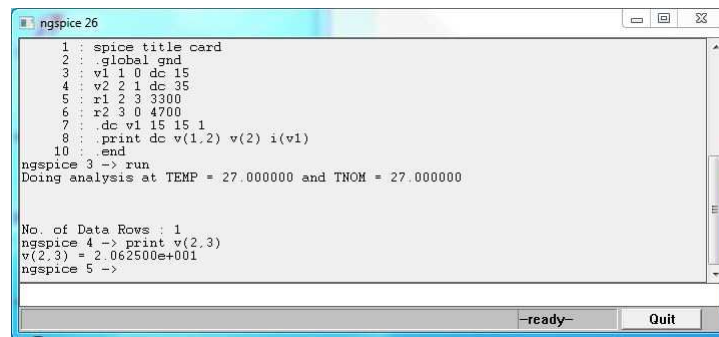2.4.5 Printing a voltage

Now we are ready to make `print` or `plot` requests of NGSPICE. Here we request NGSPICE to print the voltage between nodes 2 and 3 with the `print v(2,3)` command:



```


ngspice 26
1 : spice title card
2 : global gnd
3 : v1 1 0 dc 15
4 : v2 2 1 dc 35
5 : r1 2 3 3300
6 : r2 3 0 4700
7 : .dc v1 15 15 1
8 : .print dc v(1,2) v(2) i(v1)
9 : .end
ngspice 3 -> run
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000

No. of Data Rows : 1
ngspice 4 -> print v(2,3)
v(2,3) = 2.062500e+001
ngspice 5 ->
  
```

Please note how NGSPICE does not require a preceding period symbol with the `print` command when it is typed at the interactive command line, nor does it require we specify `dc` analysis as part of the `print` command! In fact we could have omitted the entire `.print` card in the netlist, as NGSPICE's interactive mode only follows output instructions typed at the command line.

Note also how NGSPICE defaults to scientific notation, in this case the voltage displayed as `2.062500e+001` which means 2.062500×10^1 Volts, or 20.62500 Volts.

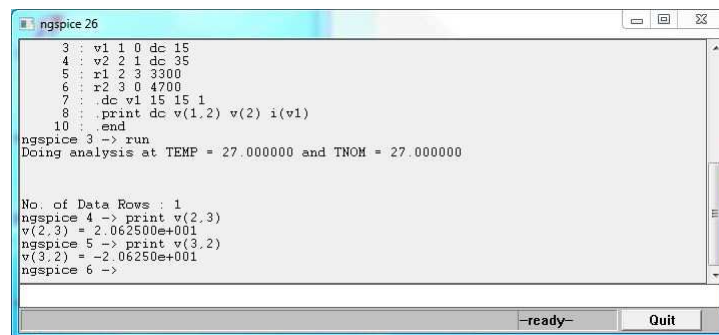If we issue the `print` command with the node numbers swapped, NGSPICE displays the DC voltage as though measuring with a DC voltmeter with the red test lead on node 3 and black test lead on node 2, showing a negative value instead of positive:



```

ngspice 26
3 : v1 1 0 dc 15
4 : v2 2 1 dc 35
5 : r1 2 3 3300
6 : r2 3 0 4700
7 : .dc v1 15 15 1
8 : .print dc v(1,2) v(2) i(v1)
9 : .end
ngspice 3 -> run
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000

No. of Data Rows : 1
ngspice 4 -> print v(2,3)
v(2,3) = 2.062500e+001
ngspice 5 -> print v(3,2)
v(3,2) = -2.062500e+001
ngspice 6 ->
  
```

If we wish to see more than one voltage reported, we may specify this at the interactive command line in exactly the same manner as we would have specified within the netlist. For example, issuing the command `print v(1,2) v(2) i(v1)` would result in NGSPICE printing the voltage between nodes 1 and 2, followed by the voltage between nodes 2 and 0, followed by the current through voltage source `v1`. Alternatively, we can type `print all` in the NGSPICE command line and receive a report of all voltages (with reference to node 0 which is ground) rather than just the voltage(s) we specify.


2.4.6 Plotting graphs using NGSPICE

Now we will explore the graphic plotting capabilities of NGSPICE. This is much more advanced than the text-based plots of legacy SPICE versions such as 2G6. Let's begin our example with the following netlist:

```
SPICE title card
c1 1 0 47e-6 ic=24
r1 1 0 2200
.tran 10m 500m uic
.plot tran v(1)
.end
```

This particular netlist defines a simple capacitor-resistor circuit with the $47\ \mu\text{F}$ capacitor pre-charged to 24 Volts. The `.tran` card calls for a time-domain analysis from $t = 0$ to $t = 500$ milliseconds, in 10 millisecond steps, using the initial condition specified in the capacitor's card.

Once having loaded this netlist into NGSPICE and issuing the `run` command, we may type `plot v(1)` and get the following output in its own window. As with the previous (DC) analysis, there is no need to specify the analysis type in the `plot` instruction (i.e. `plot v(1)` rather than `plot tran v(1)`) because NGSPICE takes its analysis cue from the `.tran` card in the netlist. In fact, the `.plot tran v(1)` card in the netlist is entirely ignored (and could have been omitted!) when using NGSPICE in interactive mode:

 

As with the `print` command, we may issue a `plot all` instruction at the command line which

will prompt NGSPICE to plot *all* variables in the simulation. This may make for a cluttered result when done with complex circuits containing many nodes, but in simple cases such as this example it may be more convenient to simply enter `plot all` rather than specify each of the desired variables one by one.

2.4.7 Issuing multiple commands in a single line

A very convenient feature of NGSPICE's interactive command line is its support for multiple commands in a single typed line. This is useful if you wish to edit the netlist and re-run the simulation without re-starting NGSPICE. Instead of typing in `source test.cir` followed by `run` followed by any specific analysis commands such as `print` and/or `plot` commands, it is possible to type all these commands on a single line in the interactive window (separated by semicolons), after which the entire string of commands may be repeated by pressing the “up” arrow key followed by the “Enter” key.

Consider for example the following sequence of commands, typically entered one command at a time in the NGSPICE interactive environment to read, execute, and finally plot data from a netlist file named `test.cir`:

```
source test.cir
```

```
run
```

```
plot v(2) v(4,3)
```

These three commands may alternatively be entered at once on a single line, then recalled with a single press of the “up” arrow key, thus conserving many keystrokes and shortening the test/development cycle:

```
source test.cir ; run ; plot v(2) v(4,3)
```

2.5 Idiosyncrasies of SPICE

SPICE, particularly early versions such as 2G6, is intolerant of certain omissions and circuit topologies. Some of them are listed here.

2.5.1 Beginning and ending cards

Every SPICE deck must begin with a “title” line of plain text. I typically insert a comment (a line beginning with a `*` character) in the first line, but a comment is not strictly necessary. The deck cannot begin with a component or analysis description.

Similarly, every SPICE deck must finish with an `.end` card to instruct the program to stop its analysis. There should be no lines past the `.end` card, not even blank lines! Similarly, the `.end` line should not be terminated with either a linefeed nor a carriage return character; i.e. do *not* press the Enter key when typing in this last line! SPICE version 2G6 will still process the deck properly with a terminated `.end` card, but it generates an annoying *missing .end card* statement anyway.

2.5.2 Node zero

Every SPICE deck must contain reference to node zero (0). Node zero is not just the default “ground” reference point in a circuit, it is a *necessary* point of reference in order for SPICE to perform its mathematical analyses of the circuit. Furthermore, every other node in the circuit must have some DC path to node 0 (ground) or else SPICE will refuse to analyze the circuit, even if the specified analysis is not DC.

2.5.3 Current measurement

Early versions of SPICE lacked the ability to print or plot values for current through any component but a voltage source. Therefore, if you need to display the calculated current at any point in a circuit being analyzed by a legacy version of SPICE, you must insert special “dummy” voltage sources (set to zero volts each) in the circuit, and then instruct the `.print` or `.plot` analysis statements to display the current through those “dummy” sources.

Alternatively, you may insert low-valued “shunt” resistors in series with the point of interest through which you wish to measure current, and then have SPICE measure the voltage(s) across the resistor(s), just the same as you might do for any real circuit where you lack an ammeter suitable for measuring current. So long as these shunt resistor values are considerably less than the other resistances through which you need to measure current, their impact on the circuit will be negligible. Shunt resistor values of $1\ \Omega$ are common for many practical current-measurement applications in the milliAmpere range. For greater currents, shunt resistances of $1\ \text{m}\Omega$ or even $1\ \mu\Omega$ may be used.

Interestingly, the mathematical sign of the calculated current is negative when the voltage source in question is actually functioning as a source (i.e. conventional current flow out the $+$ terminal and in the $-$ terminal). In order to display a positive current value, current must be entering the voltage source’s $+$ terminal and exiting the $-$ terminal, like a load.

2.5.4 Open and short circuits

The fundamental problem with open or shorted circuits is that either condition creates an *undefined* mathematical quantity that SPICE cannot compute. Opens create a condition of infinite (undefined) resistance. Shorts create a condition of zero resistance, which leads to infinite (undefined) current.

Since the insertion of a “short” or an “open” condition may be very useful for simulating a failed component, a common strategy in SPICE modeling is to use a resistor having a very low resistance (short) or a very high resistance (open). For example, a resistance with a value of $1\text{e-}9$ Ohms is a short for all practical purposes. Similarly, a resistance with a value of $1\text{e}9$ Ohms is tantamount to an open for most applications.

2.5.5 Multiple sources


Multiple voltage and/or current sources are permitted in SPICE, but only in certain configurations. Connecting multiple voltage sources in parallel creates a *voltage source loop* error which will cause the analysis to abort, and connecting multiple current sources in series creates a *no dc path to ground* error that is similarly fatal, regardless of source values.

The problem may be understood by considering the internal impedance of each source, and how that impedance “appears” from the perspective of any other source(s). Ideal voltage sources have zero internal impedance, which is why SPICE balks at parallel-connected voltage sources: from the perspective of one voltage source, any other paralleled voltage source appears to be a direct short-circuit. Ideal current sources have infinite internal impedance, which is why SPICE balks at series-connected current sources: from the perspective of one current source, any others connected in series appear to create an open-circuit condition.


It is permissible, however, to connect multiple voltage sources in series with each other. Likewise, multiple current sources connected in parallel are also permissible.

If paralleled voltage sources and/or series-connected current sources are necessary for your circuit design, you may “break up” the offending configuration by inserting *buffer components*. For example, inserting resistors of extremely low value in series with each voltage source before paralleling them will allow the analysis to proceed. A resistor of extremely high value inserted in parallel with a current source will provide the dc path around the other current source that SPICE is looking for, similarly allowing the analysis to proceed.

Impermissible source connections

 

Permissible source connections

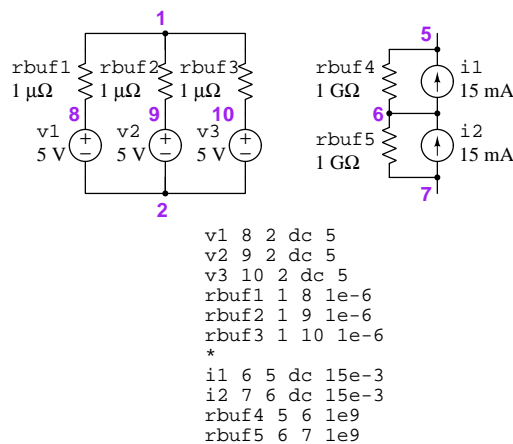


2.5.6 Multiple inductors/capacitors

Similar problems arise when connecting multiple inductors directly in parallel with each other, or multiple capacitors directly in series with each other. SPICE views an inductor as being a short (zero resistance) under DC conditions, and a capacitor as being an open (infinite resistance) under DC conditions. As with multiple sources, the problem may be understood by considering the DC resistance of each component as seen from the other components. Parallel-connected inductors are problematic because any attempt to analyze the behavior of one inductor is thwarted by the apparent short-circuit formed by the other inductor(s); series-connected capacitors are problematic because any attempt to analyze the behavior of one capacitor is thwarted by the apparent open-circuit formed by the other capacitor(s).


Likewise, SPICE cannot tolerate any voltage source being connected in parallel with any inductor, nor any current source being connected in series with any capacitor.

If any of these offending configurations are necessary for your circuit design, you may skirt the problem by inserting buffer components as previously described:

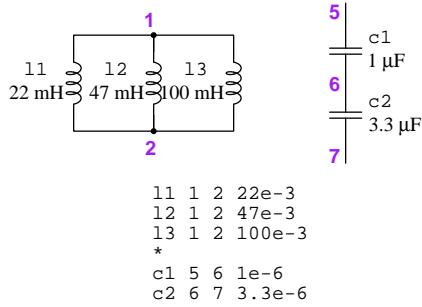Impermissible inductor/capacitor connections



Permissible inductor/capacitor connections

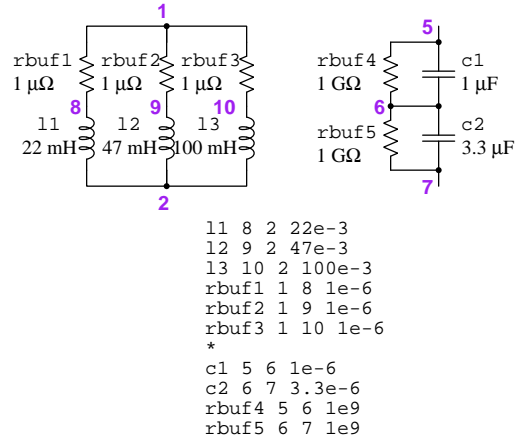

Chapter 3

SPICE component descriptions

To review, here are some of the “cardinal rules” for writing SPICE netlists:

- The first line (card) of the netlist is the Title. It cannot be omitted.
- The last line (card) of the netlist is the `.end` command. It cannot be omitted.
- Each and every unique connection point in the circuit must be assigned a number called a *node*. This is how you describe the “shape” of the circuit to SPICE: by describing which nodes each component connects to. Components sharing common node numbers are connected to each other. There *must* be a node 0, and this is the “Ground” node of the circuit.
- Comment lines (cards) must begin with an asterisk symbol (*). These are lines of text inserted into the netlist strictly for the benefit of human readers. SPICE skips over them.

Note that SPICE is case-insensitive. Any instances of capitalization in the following SPICE examples are included solely for clarity and readability, and do not matter when entered into a SPICE netlist.

3.1 Independent voltage sources

General format for DC and AC analyses:

[Vname] [+node_ID] [-node_ID] [DC/AC voltage] [AC voltage phaseangle]

The first node specified is always the positive (+) terminal of the voltage source, while the second node is always the negative (-) terminal.


3.1.1 Example: DC source

- Name = *supply*
- Polarity = + on node 5 and - on node 2
- Value = 15 Volts DC

SPICE element description

```
Vsupply 5 2 dc 15
```

Schematic representation

 


3.1.2 Example: “Dummy” source

- Name = *meter*
- Polarity = + on node 2 and - on node 1
- Value = 0 Volts

SPICE element description

```
Vmeter 2 1 0
```

Schematic representation

 

“Dummy” voltage sources are useful in SPICE netlists, to serve as points of measurement for current. Legacy versions of SPICE could not display a calculated current value for any element other than a voltage source, so a “dummy” voltage source with a value of 0 Volts served the purpose quite well.


3.1.3 Example: AC source

- Name = *gen*
- Polarity = + on node 3 and - on node 0
- Value = 120 Volts \angle 30 degrees

SPICE element description

Vgen 3 0 ac 120 30

Schematic representation

 

AC sources specified in this manner are assumed to be sinusoidal in waveform with a constant magnitude and phase shift, and the analysis performed by SPICE will be in the frequency domain.

In addition to steady-state DC and AC sources, SPICE also supports multiple types of time-dependent sources, useful for simulating waveforms and pulse trains in the time domain.

General format for time-domain analyses:

<code>[Vname] [+node.ID] [-node.ID] [waveform_type] ([option1 option2] [option3 ...])</code>
--

The first node specified is always the positive (+) terminal of the voltage source, while the second node is always the negative (−) terminal. Five different waveform types are supported, each with their own options. The waveform types are Sinusoidal (**sin**), Pulse (**pulse**), Exponential (**exp**), Piecewise Linear (**pwl**), and Frequency-Modulated Sinusoidal (**sfm**).

No provision for phase angle exists for AC time-domain sources. Instead, one must make creative use of the start delay time option. A positive start delay time means that the waveform’s start becomes delayed, representing a negative phase shift angle. Conversely, a negative start delay time means the waveform has an “early” start, or a positive phase shift angle. Unfortunately, SPICE version 2G6 does not support negative start delay time values.



3.1.4 Example: Sinusoidal source

- Name = *signal*
- Polarity = + on node 6 and - on node 2
- Wave type = *sinusoidal*
- DC offset = 10 Volts
- Peak amplitude = 120 Volts
- Frequency = 60 Hz
- Start delay = 8 milliseconds
- Damping factor = 0 seconds^{-1} (i.e. an undamped waveform)

SPICE element description

```
Vsignal 6 2 sin(10 120 60 8m 0)
```

Schematic representation

  

As opposed to a simple AC voltage sources which is assumed to be sinusoidal in waveform and constant in magnitude (i.e. no growth or decay over time), this source is explicitly sinusoidal, and the analysis performed by SPICE will be in the time domain.

Note that the damping factor assumes a decaying signal with a positive value. In order to generate an exponentially growing waveform you will need to use a *negative* value for the damping factor. In other words, the damping factor is equal to $-\sigma$.

3.1.5 Example: Pulse source


- Name = *signal*
- Polarity = + on node 3 and - on node 1
- Wave type = *pulse*
- Initial value = -5 Volts
- Pulsed value = 5 Volts
- Start delay = 3 milliseconds
- Rise time = 1 millisecond
- Fall time = 2 millisecond
- Pulse width = 5 milliseconds
- Period = 10 milliseconds

SPICE element description


```
Vsignal 3 1 pulse (-5 5 3m 1m 2m 5m 10m)
```

Schematic representation

V_{signal}

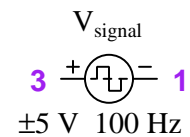

$\pm 5 \text{ V } 100 \text{ Hz}$

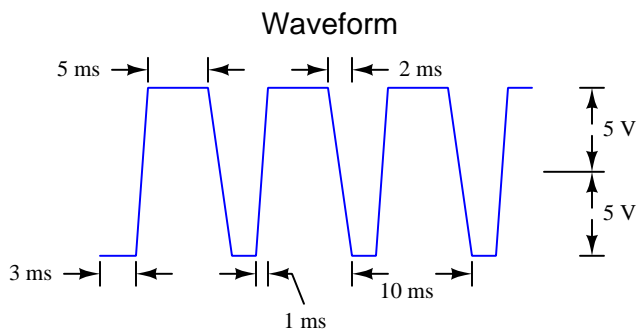

Like other time-dependent sources, a pulse source requires analysis in the time domain using the `.tran` analysis option.

3.2 Independent current sources

General format for DC and AC analyses:

[Iname] [sink_node_ID] [source_node_ID] [DC/AC current] [AC current phaseangle]

The first node specified is always the terminal where current (conventional flow) enters the current source, while the second node is always the terminal where current exits the source.


3.2.1 Example: DC source

- Name = *g*
- Polarity = *current enters node 3 and exits node 7*
- Value = *10 milliAmperes*

SPICE element description

```
I9 3 7 dc 10e-3
```

Schematic representation

 


3.2.2 Example: AC source

- Name = *in*
- Polarity = *current enters node 2 and exits node 5*
- Value = *8 milliAmperes ∠ -20 degrees*

SPICE element description

```
Iin 2 5 ac 8m -20
```

Schematic representation

 

3.3 Resistors

General format:

`[Rname] [node_ID] [node_ID] [value]`

As with all SPICE elements, resistor values may be specified using plain decimal notation, power-of-ten notation, or metric-prefix notation as alternatively shown in the example.

3.3.1 Example

- Name = *limit*
- Nodes = *connected between nodes 2 and 8*
- Value = *33 kilo-Ohms Ω*

SPICE element description

```
Rlimit 2 8 33000
```

(or)

```
Rlimit 2 8 33e3
```

(or)

```
Rlimit 2 8 33k
```

Schematic representation

R_{limit}

2  8

33 k Ω

3.4 Capacitors

General format:

```
[Cname] [+node.ID] [-node.ID] [value] [IC= initial_voltage]
```

An important caveat when using capacitors in a SPICE netlist is that SPICE cannot tolerate multiple capacitors connected directly in series. If your circuit design requires this configuration, you will need to insert a “buffer” component (e.g. a resistor with an extremely high resistance value) in parallel with one or more of the capacitors so that the offending components are no longer directly in series with each other.

3.4.1 Example: Capacitor with initial charge


- Name = *2*
- Polarity = *+ on node 9 and - on node 3, initially charged to 3.5 Volts*
- Value = *22 micro-Farads*

SPICE element description

```
C2 9 3 22e-6 ic=3.5
```

Schematic representation

C_2

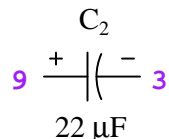

3.4.2 Example: Uncharged capacitor


- Name = *filter*
- Nodes = *connected between nodes 1 and 4, no initial voltage*
- Value = *4700 micro-Farads*

SPICE element description

```
Cfilter 1 4 4700e-6
```

Schematic representation

C_{filter}

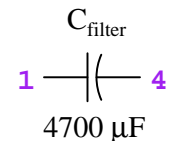

3.5 Inductors

General format:

[**L***name*] [sink_node_ID] [source_node_ID] [*value*] [**IC=** *initial_current*]

An important caveat when using inductors in a SPICE netlist is that SPICE cannot tolerate multiple inductors connected directly in parallel, nor can it abide any voltage source connected directly in parallel with an inductor. If your circuit design requires either of these configurations, you will need to insert a “buffer” component (e.g. a resistor with a negligible resistance value) between the inductors or inductor/voltage source so that the offending components are no longer directly in parallel with each other.


3.5.1 Example: Inductor with initial charge

- Name = *5*
- Polarity = *current enters node 2 and exits node 6, initially carrying 25 milliAmperes*
- Value = *100 milliHenrys*

SPICE element description

```
L5 2 6 100e-3 ic=25e-3
```

Schematic representation

 


3.5.2 Example: Uncharged inductor

- Name = *filter*
- Nodes = *connected between nodes 8 and 1, no initial current*
- Value = *0.75 Henrys*

SPICE element description

```
Lfilter 8 1 0.75
```

Schematic representation

 

3.6 Transformers

Transformers do not exist as independent entities in SPICE. Instead, one must specify the windings of a transformer as separate inductors, then specify a *coupling* factor k magnetically linking those inductors. The relationship between mutual inductance (M), k , and the two inductor values (L_1 and L_2) are given by the formula $M = k\sqrt{L_1L_2}$.

General format:

[Kname] [Lname_1] [Lname_2] [value]


3.6.1 Example: 2:1 ratio step-down transformer

- Name = *xfmr1*
- Nodes = *primary inductor L1 connected between nodes 1 and 2, secondary inductor L2 connected between nodes 3 and 4*
- Value = *0.9999*

SPICE element description

```
L1 1 2 20
L2 3 4 5
Kxfmr1 L1 L2 0.9999
```

Schematic representation

 

Note how the ratio of primary to secondary inductance is equal to the square of the turns ratio, because inductance is proportional to the square of the winding turns. Thus, in order to achieve a 2:1 turns ratio, we need a 4:1 inductance ratio.

3.7 Transmission lines

Transmission lines are four-terminal devices, much like dependent sources. Rather than specifying a physical length for the transmission line, we may *either* specify delay time (i.e. the time it takes for the signal to propagate along the entire length of the line) *or* the signal frequency and corresponding electrical length of the line (in units of wavelengths). These two methods of specifying line length are exclusive to each other. If using the frequency option, the electrical line length defaults to 0.25 ($\frac{\lambda}{4}$) unless specified otherwise.

General format:

[**T***name*] [node_ID] [node_ID] [node_ID] [node_ID] [**Z0**= *characteristic impedance*] [**TD**= *delay time*] [**F**= *frequency* and **NL**= *electrical length*]


3.7.1 Example: 50-Ohm transmission line with 10 nanosecond delay

- Name = *cable*
- Nodes = *one end of cable has nodes 1 and 2, other end of cable has nodes 3 and 4*
- Delay = *10e-9 seconds*

SPICE element description

```
Tcable 1 2 3 4 z0=50 td=10e-9
```

Schematic representation

 


3.7.2 Example: half-wavelength (at 35 MHz) 300-Ohm transmission line

- Name = *feedline*
- Nodes = *one end of cable has nodes 3 and 0, other end of cable has nodes 4 and 0*
- Frequency = *35 MHz*
- Electrical length = *0.5 wavelengths*

SPICE element description

```
Tcable 3 0 4 0 z0=300 f=35e6 nl=0.5
```

Schematic representation

 

3.8 Linear dependent sources

While independent sources output a prescribed voltage or current, dependent sources output a voltage or current as a function of some other voltage or current signal in the circuit. While there is no real-world equivalent component for a dependent source, dependent sources are useful for modeling a variety of phenomena and are often used as portions of a SPICE model for some real-world component.

SPICE offers dependent sources in four different types:

- Voltage-controlled voltage source (E)
- Voltage-controlled current source (G)
- Current-controlled voltage source (H)
- Current-controlled current source (F)

Voltage-controlled sources (types E and G) have four nodes specified in their SPICE card: two nodes for the input terminals of the controlling voltage, and two nodes for the output terminals. Current-controlled sources (types H and F) only specify the two output terminal nodes, the controlling current being specified by the name of some independent voltage source used as a current sensor.

General formats:

$[Ename] [+output_node_ID] [-output_node_ID] [+input_node_ID] [-input_node_ID] [gain]$
--

$[Gname] [sink_node_ID] [source_node_ID] [+input_node_ID] [-input_node_ID] [gain]$
--

$[Hname] [+output_node_ID] [-output_node_ID] [Vname] [gain]$
--

$[Fname] [sink_node_ID] [source_node_ID] [Vname] [gain]$
--

In each case, the *gain* value is the ratio of output to input, regardless of units (e.g. Volts output per Volt input for a type E source; Amperes output per Volt input for a type G source, etc.).


3.8.1 Example: voltage-controlled voltage source

- Name = 3
- Polarity = *input on nodes 3 (+) and 4 (-) ; output on nodes 1 (+) and 2 (-)*
- Gain = *0.5 Volts output per Volt input*

Spice element description

```
E3 1 2 3 4 0.5
```

Schematic representation

 


3.8.2 Example: voltage-controlled current source

- Name = 1
- Polarity = *input on nodes 4 (+) and 8 (-) ; output current enters node 5 and exits node 6*
- Gain = *2.3 Amperes output per Volt input*

Spice element description

```
G1 5 6 4 8 2.3
```

Schematic representation

 

3.9 Nonlinear dependent sources

While independent sources output a prescribed voltage or current, dependent sources output a voltage or current as a function of some other voltage or current signal in the circuit. A *nonlinear* source is able to implement a mathematical function relating one or more inputs to its output. While there is no real-world equivalent component for a dependent source, dependent sources are useful for modeling a variety of phenomena and are often used as portions of a SPICE model for some real-world component.

Note: these sources are not available in legacy versions of SPICE, but are supported in NGSPICE.

General format:

```
[Bname] [+output_node_ID] [-output_node_ID] [i= expression] [v= expression]
```

Supported mathematical functions include the arithmetic basic operations of addition (+), subtraction (-), multiplication (*), division (/), and powers (^) as well as many other functions. Exponential (**exp**) and logarithmic (both **ln** and **log**), trigonometric, hyperbolic, and other functions are supported too.


3.9.1 Example: multiplier

- Name = *2*
- Polarity = *output on nodes 4 (+) and 3 (-)*
- Function = *voltage v(1) times voltage v(2)*

Spice element description

```
B2 4 3 v=(v(1)*v(2))
```

Schematic representation

 

$$V_{\text{out}} = (V_1)(V_2)$$

3.10 Diodes

Semiconductor diodes, like other semiconductor components in SPICE, must be accompanied by a `.model` card somewhere in the netlist specifying the model name and parameters.

General format:

```
[Dname] [anode_node_ID] [cathode_node_ID] [model_name] [IC= initial_voltage]
[.MODEL] [model_name] [D] [Parameter1= value] [Parameter2= value] [...]
```

The following is a list of parameters, any of which may be included in the `.model` card:

- IS = Reverse saturation current (default = 1×10^{-14} Amperes)
- N = Emission coefficient (default = 1)
- RS = Ohmic resistance (default = 0 Ohms)
- TT = Transit time (default = 0 seconds)
- CJO = Zero-bias junction capacitance (default = 0 Farads)
- VJ = Junction potential (default = 1 Volt)
- M = Grading coefficient (default = 0.5)
- EG = Activation energy (default = 1.11 electron-Volts, representing Silicon)
- BV = Breakdown voltage (default = infinite Volts)
- IBV = Current at breakdown voltage (default = 1×10^{-3} Amperes)

3.10.1 Example: Generic diode

- Name = *2*
- Polarity = *anode on node 5 and cathode on node 8*
- Model = *acme*, generic diode

SPICE element description

```
D2 5 8 acme
.MODEL acme d
```

Schematic representation

```
D2
5 —▶— 8
```


3.10.2 Example: 1N4001

- Name = *d*
- Polarity = *anode on node 1 and cathode on node 0*
- Model = *1N4001* rectifying diode

SPICE element description

```
D4 1 0 1N4001
.MODEL 1N4001 d
+ IS=1.2e-8 RS=0.04
+ N=1.83 EG=0.6
+ BV=50 IBV=5e-8
+ CJO=1e-11 VJ=0.65
+ M=0.5 TT=1e-9
```

Schematic representation

 

3.11 Bipolar Junction Transistors (BJTs)

BJTs, like other semiconductor components in SPICE, must be accompanied by a `.model` card somewhere in the netlist specifying the model name and parameters. This is where the type of BJT (NPN or PNP) is specified.

General format:

```
[Qname] [collector_node_ID] [base_node_ID] [emitter_node_ID] [model_name]
[.MODEL] [model_name] [NPN or PNP] [Parameter1= value] [Parameter2= value] [...]
```

The following is a list of parameters, any of which may be included in the `.model` card:

- IS = Reverse saturation current (default = 1×10^{-14} Amperes)
- BF = Forward current gain (default = 100)
- BR = Reverse current gain (default = 1)
- NF = Forward emission coefficient (default = 1)
- NR = Reverse emission coefficient (default = 1)
- VAF = Forward Early voltage (default = infinite Volts)
- VAR = Reverse Early voltage (default = infinite Volts)
- RC = Collector ohmic resistance (default = 0 Ohms)
- RB = Base ohmic resistance (default = 0 Ohms)
- RE = Emitter ohmic resistance (default = 0 Ohms)
- TF = Forward transit time (default = 0 seconds)
- TR = Reverse transit time (default = 0 seconds)
- CJE = Zero-bias B-E junction capacitance (default = 0 Farads)
- CJC = Zero-bias B-C junction capacitance (default = 0 Farads)
- VJE = B-E junction potential (default = 0.75 Volt)
- VJC = B-C junction potential (default = 0.75 Volt)
- MJE = B-E grading coefficient (default = 0.33)
- MJC = B-C grading coefficient (default = 0.33)


3.11.1 Example: Generic NPN transistor

- Name = *3*
- Terminals = *collector on node 2 and base on node 7 and emitter on node 4*
- Model = *mynpn*, generic NPN

SPICE element description

```
Q3 2 7 4 mynpn
.MODEL mynpn npn
```

Schematic representation

 


3.11.2 Example: 2N2907

- Name = *8*
- Terminals = *collector on node 5 and base on node 2 and emitter on node 3*
- Model = *2N2907* small-signal PNP

SPICE element description

```
Q8 5 2 3 2N2907
.MODEL 2N2907 pnp
+ IS=3e-12 BF=395
+ NF=1.15 VAF=42
+ VJE=0.69 VJC=0.41
```

Schematic representation

 

3.12 Junction Field-Effect Transistors (JFETs)

JFETs, like other semiconductor components in SPICE, must be accompanied by a `.model` card somewhere in the netlist specifying the model name and parameters. The channel type is specified in the `.model` card: NJF for N-channel and PJF for P-channel.

General format:

```
[Jname] [drain_node_ID] [gate_node_ID] [source_node_ID] [model_name]
[.MODEL] [model_name] [NJF or PJF] [Parameter1= value] [Parameter2= value] [...]
```

The following is a list of parameters, any of which may be included in the `.model` card:

- VTO = Threshold pinch-off voltage (default = -2.0 Volts)
- BETA = Transconductance (default = 10^{-4} A/V²)
- LAMBDA = Channel length modulation (default = 0 V⁻¹)
- RD = Drain ohmic resistance (default = 0 Ohms)
- RS = Source ohmic resistance (default = 0 Ohms)
- CGS = Zero-bias G-S junction capacitance (default = 0 Farads)
- CGD = Zero-bias G-D junction capacitance (default = 0 Farads)
- IS = Gate junction saturation current (default = 1×10^{-14} Amperes)
- PB = Gate junction potential (default = 1.0 Volt)

The mathematical sign of the threshold pinch-off voltage (VTO) is important. Since JFETs are normally-on devices, and the gate-channel PN junction must be reverse-biased in order to turn the transistor off, the value for VTO is negative. Interestingly, this negative sign is true regardless of channel type (i.e. N-channel or P-channel) although the actual polarity necessary for reverse-biasing that junction is different for the two channel types.


3.12.1 Example: Generic N-channel JFET

- Name = *6*
- Terminals = *drain on node 4 and gate on node 2 and source on node 5*
- Model = *nchannel*, generic NJF

SPICE element description

```
J6 4 2 5 nchannel  
.MODEL nchannel njf
```

Schematic representation

 

3.13 Metal-Oxide Field-Effect Transistors (MOSFETs)

MOSFETs, like other semiconductor components in SPICE, must be accompanied by a `.model` card somewhere in the netlist specifying the model name and parameters. The channel type is specified in the `.model` card: NMOS for N-channel and PMOS for P-channel.

General format:

```
[Mname] [drain_node_ID] [gate_node_ID] [source_node_ID] [bulk_node_ID] [model_name]
[.MODEL] [model_name] [NMOS or PMOS] [Parameter1= value] [Parameter2= value]
[...]
```

Note: the “bulk” terminal describes the semiconductor substrate upon which the MOSFET is built, and is optional. The following is a list of parameters, any of which may be included in the `.model` card:

- VTO = Threshold pinch-off voltage (default = 0 Volts)
- KP = Transconductance (default = 2×10^{-5} A/V²)
- GAMMA = Bulk threshold (default = $0 \text{ V}^{\frac{1}{2}}$)
- LAMBDA = Channel length modulation (default = 0 V^{-1})
- RD = Drain ohmic resistance (default = 0 Ohms)
- RS = Source ohmic resistance (default = 0 Ohms)
- RSH = Drain and source diffusion sheet resistance (default = 0 Ohms)
- CBD = Zero-bias B-D junction capacitance (default = 0 Farads)
- CBS = Zero-bias B-S junction capacitance (default = 0 Farads)
- CJ = Zero-bias bulk junction bottom capacitance (default = 0 Farads)
- MJ = Bulk junction grading coefficient (default = 0.5)
- CJSW = Zero-bias bulk junction sidewall capacitance (default = 0 Farads)
- MJSW = Bulk junction sidewall grading coefficient (default = 0.33)
- IS = Bulk junction saturation current (default = 1×10^{-14} Amperes)
- PB = Bulk junction potential (default = 1.0 Volt)
- CGDO = G-D overlap capacitance per unit channel width (default = 0 Farads/meter)
- CGSO = G-S overlap capacitance per unit channel width (default = 0 Farads/meter)

- CGBO = G-B overlap capacitance per unit channel width (default = 0 Farads/meter)
- TOX = Oxide thickness (default = infinite meters)
- LD = Lateral diffusion (default = 0 meters)

The same device card is used for enhancement-mode as well as depletion-mode MOSFETs, the only difference being the value assigned to the threshold pinch-off voltage (V_{T0}). Enhancement-mode MOSFETs are normally-off devices and thus are “pinched off” at zero gate voltage, requiring V_{T0} to be a positive value for NMOS devices and a negative value for PMOS devices. Depletion-mode MOSFETs are normally-on devices and need a “reverse-bias” gate voltage to turn off, requiring V_{T0} to be a negative value for NMOS devices and a positive value for PMOS devices.


3.13.1 Example: Generic N-channel depletion-type MOSFET

- Name = 7
- Terminals = *drain on node 2 and gate on node 1 and source on node 4 (bulk connected to source)*
- Model = *ndmos*, generic depletion-type NMOS

SPICE element description

```
M7 2 1 4 4 ndmos
.MODEL ndmos VTO=-3
```

Schematic representation

 


3.13.2 Example: Generic N-channel enhancement-type MOSFET

- Name = 7
- Terminals = *drain on node 2 and gate on node 1 and source on node 4 (bulk connected to source)*
- Model = *nemos*, generic enhancement-type NMOS

SPICE element description

```
M7 2 1 4 4 nemos
.MODEL nemos VTO=2
```

Schematic representation

 


3.13.3 Example: Generic P-channel depletion-type MOSFET

- Name = 7
- Terminals = *drain on node 2 and gate on node 1 and source on node 4 (bulk connected to source)*
- Model = *pdmos*, generic depletion-type PMOS

SPICE element description

```
M7 2 1 4 4 pdmos
.MODEL pdmos VTO=3
```

Schematic representation

 


3.13.4 Example: Generic P-channel enhancement-type MOSFET

- Name = 7
- Terminals = *drain on node 2 and gate on node 1 and source on node 4 (bulk connected to source)*
- Model = *pemos*, generic enhancement-type PMOS

SPICE element description

```
M7 2 1 4 4 pemos
.MODEL pemos VTO=-2
```

Schematic representation

 

3.14 Subcircuits

Computer programming languages provide the means to perform *subroutines*, which consist of collections of code (instructions) separate from the main body of the program, but which may be “called” from the main program as many times as needed. This is used in applications where a particular algorithm or set of instructions must be repeatedly executed: rather than have those instructions appear repeated throughout the program, they are entered as a subroutine and that subroutine is called by name as many times as necessary.

SPICE has the ability to do the equivalent when simulating electric circuits. A collection of components that would otherwise need to be repeatedly entered in the netlist can be defined once as a *subcircuit*, and then that subcircuit may be called by name as often as desired elsewhere in the netlist. Subcircuits are useful when the overall circuit is comprised of multiple identical sub-networks, because it makes the netlist shorter and easier to understand to a human reader.

```
[X] [subcircuit_name] [node_1] [node_2] [...]  
[.SUBCKTname] [node_1] [node_2] [...]
```

All node numbers with the exception of node 0 used within the `.SUBCKT` card are “local” to that card and may be re-used for other purposes elsewhere in the netlist.


3.14.1 Example: resistor subnetwork

- Name = *rnet*
- Terminals = *first node is upper, second is lower*

SPICE subcircuit description

```
.SUBCKT rnet 1 4
R1 1 2 2200
R2 2 3 2200
R3 2 4 2200
R4 3 4 2200
.ENDS rnet
```


Schematic representation

 

SPICE subcircuit usage

```
X1 1 2 rnet
X2 2 3 rnet
X3 3 0 rnet
```

Schematic representation

 

3.14.2 Example: solar cell array


The simulation of a solar cell array is an excellent use of both subcircuits and semiconductor models in SPICE. Each individual solar cell outputs about the same amount of voltage as the forward drop of a silicon rectifying diode, because a solar cell *is* a silicon PN junction. The larger the cell's junction contact area, the greater its short-circuit current capacity. We may simulate each cell's short-circuit (maximum) current using a current source (I_{sc}) and its PN-junction characteristics using a diode element (D_1) with added resistors representing substrate and inter-cell connection resistances:

- Name = *pvcell*
- Terminals = *first node is positive, second is negative*

SPICE subcircuit description

```
.SUBCKT pvcell 1 3
RS 1 2 0.01
ISC 3 2 1.5
D1 2 3 pnjunc
RP 2 3 5
.MODEL pnjunc d
.ENDS pvcell
```


Schematic representation

 

SPICE subcircuit usage

```
X1 1 2 pvcell
X2 2 0 pvcell
X3 1 3 pvcell
X4 3 0 pvcell
```

Schematic representation

 

Chapter 4

SPICE analysis descriptions

To review, here are some of the “cardinal rules” for writing SPICE netlists:

- The first line (card) of the netlist is the Title. It cannot be omitted.
- The last line (card) of the netlist is the `.end` command. It cannot be omitted.
- Each and every unique connection point in the circuit must be assigned a number called a *node*. This is how you describe the “shape” of the circuit to SPICE: by describing which nodes each component connect to. Component terminals sharing common node numbers are electrically common (i.e. directly connected to each other). There *must* be a node 0, and this is the “Ground” node of the circuit.
- Comment lines (cards) must begin with an asterisk symbol (*). These are lines of text inserted into the netlist strictly for the benefit of human readers. SPICE skips over them.

Note that SPICE is case-insensitive. Any instances of capital letters in the following SPICE analysis descriptions are included solely for clarity and readability.

4.1 DC voltage/current “sweep” analysis

General format:

```
[.dc] [source_name] [start_value] [end_value] [increment]
```

The starting and ending values for the sweep will override any static values specified in the source’s line (card).

4.1.1 Example: sweep of voltage source

- Source = *voltage source “v1”*
- Starting value = *2 Volts*
- Ending value = *12 Volts*
- Increment value = *5 Volts*

SPICE analysis description: `.dc v1 2 12 5`

4.1.2 Example: sweep of voltage and current sources

- Source1 = *voltage source “vce”*
 Starting value = *0 Volts*
 Ending value = *20 Volts*
 Increment value = *0.5 Volt*
- Source2 = *current source “ib”*
 Starting value = *0 milliAmperes*
 Ending value = *0.6 milliAmperes*
 Increment value = *0.1 milliAmperes*

SPICE analysis description: `.dc vce 0 20 0.5 ib 0 0.6e-3 0.1e-3`

Multi-source sweeps are useful when plotting “families” of characteristic curves for semiconductor devices, where each curve plotted is at a different controlling signal value. In the example shown, V_{CE} is swept from 0 to 20 Volts at an I_B value of 0 milliAmperes, then swept again from 0 to 20 Volts at $I_B = 0.1$ mA, then swept again from 0 to 20 Volts at $I_B = 0.2$ mA, etc.

4.2 AC frequency “sweep” analysis

General format:

<code>[.ac] [linearity] [points] [start_frequency] [end_frequency]</code>

4.2.1 Example: linear frequency sweep

- Linearity type = *linear*
- Number of points = *100*
- Starting frequency = *400 Hz*
- Ending frequency = *900 Hz*

SPICE analysis description: `.ac lin 100 400 900`

4.2.2 Example: decade logarithmic frequency sweep

- Linearity type = *decade*
- Number of points = *5 per decade*
- Starting frequency = *1 kHz*
- Ending frequency = *100 kHz*

SPICE analysis description: `.ac dec 5 1k 100k`

4.2.3 Example: octave logarithmic frequency sweep

- Linearity type = *octave*
- Number of points = *12 per octave*
- Starting frequency = *440 Hz*
- Ending frequency = *3.52 kHz*

SPICE analysis description: `.ac oct 12 440 3.52e3`

Note: this particular analysis covers four octaves of the frequencies of the equal-tempered Western musical scale, beginning with 440 Hz (concert tuning pitch “A”).

4.3 Transient analysis

General format:

<code>[.tran] [interval_time] [end_time] [start_time] [uic] [end_frequency]</code>
--

This instructs SPICE to perform a time-domain analysis of the circuit, from time $t = 0$ to the specified end time, over intervals of specified length. The starting time is used only for analyses where the printed or plotted results do not begin at $t = 0$; if unspecified it is assumed that the starting time is zero. The UIC parameter is optional, instructing SPICE to honor any initial conditions (IC=) specified in the component descriptions.

4.3.1 Example: using initial conditions, beginning at time $t = 0$

- Time interval = *10 milliseconds*
- Ending time = *500 milliseconds*

SPICE analysis description: `.tran 10m 500m uic`

4.3.2 Example: using initial conditions, beginning at non-zero time

- Time interval = *30 microseconds*
- Ending time = *200 microseconds*
- Print/plot starting time = *100 microseconds*

SPICE analysis description: `.tran 30u 200u 100u uic`

4.4 Fourier analysis

General format:

<code>[.four] [fundamental_frequency] [variable] [variable] [variable ...]</code>

Fourier analysis provides a printed-text summary of the first ten harmonic frequencies of the specified variable(s). This analysis must always be used in conjunction with a *transient* (`.tran`) analysis in the same netlist, since the Fourier transform takes a time-domain function (i.e. transient data in SPICE) and converts it into a frequency-domain function.

4.4.1 Example: analysis of 60 Hz waveform

- Fundamental frequency = *60 Hz*
- Variable = *Voltage between nodes 3 and 1*

SPICE analysis description: `.four 60 v(3,1)`

4.5 Display option: print

General format:

```
[.print] [analysis_type] [variable] [variable] [variable ...]
```

In order for this display option to function, the netlist (deck) must also contain an analysis line (card).

4.5.1 Example: printing a DC analysis

- Analysis type = *DC* (netlist must contain a `.dc` analysis line)
- First variable = *Voltage between node 4 and Ground*
- Second variable = *Voltage between nodes 6 and 3*
- Third variable = *Current through voltage source “vsupply”*

SPICE analysis description: `.print dc v(4) v(6,3) i(vsupply)`

4.5.2 Example: printing an AC analysis

- Analysis type = *AC* (netlist must contain an `.ac` analysis line)
- First variable = *Voltage magnitude between node 4 and Ground*
- Second variable = *Voltage phase angle between node 4 and Ground*
- Third variable = *Current magnitude through voltage source “vsupply”*
- Fourth variable = *Current phase angle through voltage source “vsupply”*

SPICE analysis description: `.print ac vm(4) vp(4) im(vsupply) ip(vsupply)`

Note that SPICE version 2 defaults to *degrees* as the unit for phase angles, while SPICE version 3 defaults to *radians*. If degrees are desired while running newer versions of SPICE, you may include the following cards in the netlist deck to control units:

```
.control
set units=degrees
.endc
```

4.6 Display option: plot

General format:

```
[.plot] [analysis_type] [variable] [variable] [variable ...]
```

The `.plot` display accepts all the same parameters as the `.print` display, but instead of merely printing a list of numbers it plots a graph of the variables over the domain of the analysis type. In order for this display option to function, the netlist (deck) must also contain an analysis line (card).

Since the purpose of the `.plot` display is to produce a *graph*, the analysis line really needs to “sweep” over multiple points.

4.6.1 Example: plotting a DC analysis

- Analysis type = *DC* (netlist must contain a `.dc` analysis line)
- First variable = *Voltage between nodes 4 and 1*

SPICE analysis description: `.plot dc v(4,1)`

4.6.2 Example: plotting an AC analysis

- Analysis type = *AC* (netlist must contain an `.ac` analysis line)
- First variable = *Voltage magnitude between nodes 4 and 1*
- Second variable = *Voltage phase angle between nodes 4 and 1*

SPICE analysis description: `.plot ac vm(4,1) vp(4,1)`

Note that SPICE version 2 defaults to *degrees* as the unit for phase angles, while SPICE version 3 defaults to *radians*. If degrees are desired while running newer versions of SPICE, you may include the following cards in the netlist deck to control units:

```
.control
set units=degrees
.endc
```

It is important to note that an AC plot is in the frequency domain; that is to say, the *x* axis of the plot will represent frequency while the *y* axis will represent the variable(s) specified in the `.plot` line. This is useful for generating Bode plots. An AC analysis will *not* plot waveforms as a function of time. That feature is delivered by `plot` only when the netlist specifies a *transient* analysis rather than an *AC* analysis.

4.6.3 Example: plotting a transient analysis

- Analysis type = *transient* (netlist must contain a `.tran` analysis line)
- First variable = *Voltage between nodes 7 and 3*

SPICE analysis description: `.plot tran v(7,3)`

This plot will show the waveform as a function of time, with the plot's x axis expressed in units of time.

4.6.4 Example: plotting parametric functions

- Analysis type = *transient* (netlist must contain a `.tran` analysis line)
- First variable = *Voltage between nodes 1 and 0*
- First variable = *Voltage between nodes 5 and 8*

SPICE analysis description: `.plot tran v(1) vs v(5,8)`

Not all versions of SPICE support the “versus” option, but in those that do, this is useful for plotting one circuit parameter against another, rather than plot circuit parameter(s) over time. Use this option to create Lissajous figures, plotting one sinusoidal voltage against another at different frequencies and/or phase shifts.

4.7 Display option: width

General format:

```
[.width] [out= characters]
```

When SPICE outputs plain-text to the computer terminal, it assumes a 120-character display width, which is fitting for legacy teletype machines, but actually exceeds the standard electronic terminal display width of 80 characters. For this reason, especially when using the `.plot` output option, it is advisable to also use the `.width` option set to 80 characters to limit the width of the text display.

4.7.1 Example

- Display width = *80 characters*

SPICE analysis description: `.width out=80`


Chapter 5

Primitive circuit examples

“Primitive” circuits consist of the minimum number of components to demonstrate a concept. In most cases they consist of one source and one load directly connected together. They are presented here as a form of “Hello World” example to show how SPICE netlists and analyses are formatted.

 5.1 DC voltage source with .op analysis

Circuit schematic diagram (with node numbers listed). Note how the voltage source and the resistor are connected between the same pair of nodes: 1 and 0. This tells SPICE they are parallel to each other, because the upper terminals of each component are electrically common (node 1) and the lower terminals of each component are also electrically common (node 0). Note also how ground is defined in SPICE as node number *zero*, which must be included in every netlist:



SPICE netlist:

```
* SPICE circuit
v1 1 0 dc 12
r1 1 0 2200
.op
.end
```

SPICE version 2G6 analysis (edited for brevity):

```
node   voltage
(1)    12.0000

       voltage source currents

name   current
v1     -5.455E-03

total power dissipation  6.55E-02  watts
```

Just to show you what the raw output of SPICE version 2G6 looks like for this analysis, here it is in all its unedited glory (note that I had to shorten some of the lines that exceeded the page width):

```

1*****09/02/16 ***** spice 2g.6 3/15/83 *****12:04:38*****

0* spice circuit

0**** input listing temperature = 27.000 deg c

0*****

v1 1 0 dc 12
r1 1 0 2200
.op
.end
1*****09/02/16 ***** spice 2g.6 3/15/83 *****12:04:38*****

0* spice circuit
0**** small signal bias solution temperature = 27.000 deg c

0*****

node voltage

( 1) 12.0000

voltage source currents

name current

v1 -5.455E-03

total power dissipation 6.55E-02 watts
0
job concluded
0 total job time 0.00

```


NGSPICE version 26 is more verbose than the legacy SPICE version 2G6 running the “Operating Point” (.op) analysis, requiring more than a page to display:

Circuit: * spice circuit

Doing analysis at TEMP = 27.000000 and TNOM = 27.000000

No. of Data Rows : 1

Node	Voltage
----	-----

V(1)	1.200000e+01

Source Current

v1#branch	
	-5.45455e-03

Resistor models (Simple linear resistor)

model	R
rsh	0
narrow	0
short	0
tc1	0
tc2	0
defw	1e-05
l	1e-05
kf	0
af	0
r	0
bv_max	1e+99

Resistor: Simple linear resistor

device	r1
model	R
resistance	2200
ac	2200
dtemp	0
bv_max	1e+99
noisy	1
i	0.00545455
p	0.0654545

Vsource: Independent voltage source

device		v1
dc		12
acmag		0
pulse	-	
sine	-	
sin	-	
exp	-	
pwl	-	
sffm	-	
am	-	
trnoise	-	
ttrandom	-	
i		-0.00545455
p		0.0654545


CPU time since last call: 0.032 seconds.

Total CPU time: 0.032 seconds.

Total DRAM available = 489.546875 MB.
DRAM currently available = 152.234375 MB.
Total ngspice program size = 2.191406 MB.
Resident set size = 593.000 kB.
Shared ngspice pages = 464.000 kB.
Text (code) pages = 1.087891 MB.
Stack = 0 bytes.
Library pages = 164.000 kB.

 5.2 DC voltage source with single-point .dc sweep analysis

Circuit schematic diagram (with node numbers listed). Note how ground is defined in SPICE as node number *zero*. In this example we will maintain the voltage source at a constant value of 12 Volts DC. The “sweep” analysis is intended to cover a specified range of voltage values, but we are exploiting that analysis option here to perform an analysis at only a single voltage value:



SPICE netlist:

```
* SPICE circuit
v1 1 0 dc 12
r1 1 0 2200
.dc v1 12 12 1
.print dc v(1) i(v1)
.end
```

SPICE version 2G6 analysis (edited for brevity):

v1	v(1)	i(v1)
1.200E+01	1.200E+01	-5.455E-03

SPICE version 2G6 is slightly less verbose when performing the .dc analysis than when performing the .op analysis. Here is the “raw” output of SPICE version 2G6 for your perusal:

```

1*****09/02/16 ***** spice 2g.6 3/15/83 *****12:22:56*****

0* spice circuit

0**** input listing temperature = 27.000 deg c

0*****

v1 1 0 dc 12
r1 1 0 2200
.dc v1 12 12 1
.print dc v(1) i(v1)
.end
1*****09/02/16 ***** spice 2g.6 3/15/83 *****12:22:56*****

0* spice circuit
0**** dc transfer curves temperature = 27.000 deg c

0*****

v1          v(1)          i(v1)
x
1.200E+01   1.200E+01   -5.455E-03
y
0
          job concluded
0          total job time          0.00

```

NGSPICE version 26 is substantially less verbose when performing the `.dc` analysis. Here is the “raw” output of NGSPICE version 26 for your perusal:

Circuit: * spice circuit

Doing analysis at TEMP = 27.000000 and TNOM = 27.000000

No. of Data Rows : 1

```

* spice circuit
DC transfer characteristic  Fri Sep  2 12:28:41  2016
-----
Index  v-sweep      v(1)          v1#branch
-----
0      1.200000e+01  1.200000e+01  -5.45455e-03

```


CPU time since last call: 0.032 seconds.

Total CPU time: 0.032 seconds.

Total DRAM available = 489.546875 MB.
 DRAM currently available = 152.128906 MB.
 Total ngspice program size = 2.191406 MB.
 Resident set size = 595.000 kB.
 Shared ngspice pages = 466.000 kB.
 Text (code) pages = 1.087891 MB.
 Stack = 0 bytes.
 Library pages = 164.000 kB.

 5.3 DC current source with single-point .dc sweep analysis

Circuit schematic diagram (with node numbers listed). Note how ground is defined in SPICE as node number *zero*. In this example we will maintain the current source at a constant value of 4 milliAmperes DC. The “sweep” analysis is intended to cover a specified range of current values, but we are exploiting that analysis option here to perform an analysis at only a single current value:



SPICE netlist:


```
* SPICE circuit
i1 0 1 dc 4e-3
r1 1 0 2200
.dc i1 4e-3 4e-3 1
.print dc v(1)
.end
```

SPICE version 2G6 analysis (edited for brevity):

```
      i1          v(1)
4.000E-03      8.800E+00
```

 5.4 DC voltage source with multi-point .dc sweep analysis

Circuit schematic diagram (with node numbers listed). Note how ground is defined in SPICE as node number *zero*. In this example we will “sweep” the voltage source from 2 to 12 Volts DC in increments of 1 Volt:



First, showing the “printed” output option:

SPICE netlist:

```
* SPICE circuit
v1 1 0 dc 12
r1 1 0 2200
.dc v1 2 12 1
.print dc v(1) i(v1)
.end
```

SPICE version 2G6 analysis (edited for brevity):

v1	v(1)	i(v1)
2.000E+00	2.000E+00	-9.091E-04
3.000E+00	3.000E+00	-1.364E-03
4.000E+00	4.000E+00	-1.818E-03
5.000E+00	5.000E+00	-2.273E-03
6.000E+00	6.000E+00	-2.727E-03
7.000E+00	7.000E+00	-3.182E-03
8.000E+00	8.000E+00	-3.636E-03
9.000E+00	9.000E+00	-4.091E-03
1.000E+01	1.000E+01	-4.545E-03
1.100E+01	1.100E+01	-5.000E-03
1.200E+01	1.200E+01	-5.455E-03

Next, showing the “plotted” output option¹:

SPICE netlist:

```
* SPICE circuit
v1 1 0 dc 12
r1 1 0 2200
.dc v1 2 12 1
.plot dc v(1) i(v1)
.width out=80
.end
```

SPICE version 2G6 analysis (edited for brevity):


```
legend:
*: v(1)
+: i(v1)

      v1          v(1)

(*)----- 0.000E+00   5.000E+00   1.000E+01   1.500E+01   2.000E+01
-----
(+)----- -6.000E-03  -4.000E-03  -2.000E-03   0.000E+00   2.000E-03
-----
2.000E+00  2.000E+00 .      *      .      .      +      .      .
3.000E+00  3.000E+00 .      *      .      .      +      .      .
4.000E+00  4.000E+00 .      *      .      .      +      .      .
5.000E+00  5.000E+00 .      *      .      +      .      .      .
6.000E+00  6.000E+00 .      .      *      +      .      .      .
7.000E+00  7.000E+00 .      .      .      x      .      .      .
8.000E+00  8.000E+00 .      .      +      *      .      .      .
9.000E+00  9.000E+00 .      .      +      .      *      .      .
1.000E+01  1.000E+01 .      .      +      .      .      *      .      .
1.100E+01  1.100E+01 .      .      +      .      .      .      *      .      .
1.200E+01  1.200E+01 .      +      .      .      .      .      *      .      .
-----
```


¹SPICE assumes a 120-character width display, and so to fit the text output on a standard terminal the `.width` option must be invoked to set the display width at 80 characters

 NGSPICE version 26 analysis (using window-based interactive mode on Linux/X-Windows):



 5.5 AC voltage source with single-point .ac sweep analysis

Circuit schematic diagram (with node numbers listed). Note how the series connection between the “dummy” resistor and the inductor is specified by three nodes: 1, 2, and 0. The resistor connects between nodes 1 and 2, while the inductor connects between nodes 2 and 0. The one node common to both components (node 2) makes those two components share a common connection. Note as always how ground is defined in SPICE as node number *zero*. In this example we will “sweep” the source frequency from 1 kHz to 1 kHz with just one interval. The “dummy” resistance of 1 milli-Ohm is necessary in order to avoid a direct “loop” between the voltage source and the inductor, which SPICE cannot abide:



SPICE netlist:

```
* SPICE circuit
v1 1 0 ac 24
rdummy 1 2 1m
l1 2 0 200m
.ac lin 1 1k 1k
.print ac vm(1) vp(1) im(v1) ip(v1)
.end
```

SPICE version 2G6 analysis (edited for brevity):

freq	vm(1)	vp(1)	im(v1)	ip(v1)
1.000E+03	2.400E+01	0.000E+00	1.910E-02	9.000E+01


Early versions of SPICE such as 2G6 assumed phase angle unit of degrees, but many later versions assume *radians* when displaying phase angles. In order to specifically instruct modern versions of SPICE to display angles in degrees, the following “control” cards must be added to the netlist:

```
.control
set units=degrees
.endc
```

These cards may be added to the netlist “deck” anywhere between the first line (* SPICE circuit) and the last (.end).

 5.6 AC voltage source with multi-point .ac sweep analysis

Circuit schematic diagram (with node numbers listed). Note how ground is defined in SPICE as node number *zero*. In this example we will “sweep” the source frequency from 60 Hz to 6 kHz on a decade logarithmic scale with 5 points per decade:



First, showing the “printed” output option:

SPICE netlist:

```
* SPICE circuit
v1 1 0 ac 120
c1 1 0 4.7u
.ac dec 5 60 6k
.print ac vm(1) vp(1) im(v1) ip(v1)
.end
```

SPICE version 2G6 analysis (edited for brevity):

freq	vm(1)	vp(1)	im(v1)	ip(v1)
6.000E+01	1.200E+02	0.000E+00	2.126E-01	-9.000E+01
9.509E+01	1.200E+02	0.000E+00	3.370E-01	-9.000E+01
1.507E+02	1.200E+02	0.000E+00	5.341E-01	-9.000E+01
2.389E+02	1.200E+02	0.000E+00	8.465E-01	-9.000E+01
3.786E+02	1.200E+02	0.000E+00	1.342E+00	-9.000E+01
6.000E+02	1.200E+02	0.000E+00	2.126E+00	-9.000E+01
9.509E+02	1.200E+02	0.000E+00	3.370E+00	-9.000E+01
1.507E+03	1.200E+02	0.000E+00	5.341E+00	-9.000E+01
2.389E+03	1.200E+02	0.000E+00	8.465E+00	-9.000E+01
3.786E+03	1.200E+02	0.000E+00	1.342E+01	-9.000E+01
6.000E+03	1.200E+02	0.000E+00	2.126E+01	-9.000E+01

Next, showing the “plotted” output option²:

SPICE netlist:

```
* SPICE circuit
v1 1 0 ac 120
c1 1 0 4.7u
.ac dec 5 60 6k
.plot ac vm(1) vp(1) im(v1) ip(v1)
.width out=80
.end
```

²SPICE assumes a 120-character width display, and so to fit the text output on a standard terminal the `.width` option must be invoked to set the display width at 80 characters

SPICE version 2G6 analysis (edited for brevity):


```

legend:
*: vm(1)
+: vp(1)
=: im(v1)
$: ip(v1)

      freq      vm(1)
(*)-----  1.000E+01    1.000E+02    1.000E+03    1.000E+04    1.000E+05
-----
(+)-----  -1.000E-12   -5.000E-13    0.000E+00    5.000E-13    1.000E-12
-----
(=)-----  1.000E-01    1.000E+00    1.000E+01    1.000E+02    1.000E+03
-----
($)-----  -1.500E+02   -1.000E+02   -5.000E+01    0.000E+00    5.000E+01
-----
6.000E+01  1.200E+02 .    =    .* $    +    .    .
9.509E+01  1.200E+02 .    =    .* $    +    .    .
1.507E+02  1.200E+02 .    =    .* $    +    .    .
2.389E+02  1.200E+02 .    =    .* $    +    .    .
3.786E+02  1.200E+02 .    =    .* $    +    .    .
6.000E+02  1.200E+02 .    =    .* $    +    .    .
9.509E+02  1.200E+02 .    =    .* $    +    .    .
1.507E+03  1.200E+02 .    =    .* $    +    .    .
2.389E+03  1.200E+02 .    =    .* $    +    .    .
3.786E+03  1.200E+02 .    =    .* $    +    .    .
6.000E+03  1.200E+02 .    =    .* $    +    .    .
-----

```

 NGSPICE version 26 analysis (using window-based interactive mode on Linux/X-Windows):




It should be noted that early versions of SPICE such as 2G6 assumed phase angle unit of degrees, but many later versions assume *radians* when displaying phase angles. In order to specifically instruct modern versions of SPICE to display angles in degrees, the following “control” cards must be added to the netlist:

```
.control
set units=degrees
.endc
```

These cards may be added to the netlist “deck” anywhere between the first line (* SPICE circuit) and the last (.end).

 5.7 Additive AC voltage sources with single-point .ac sweep analysis

Circuit schematic diagram (with node numbers listed). Note the use of node numbers to specify the circuit's shape. Node 0 is the ground point, while nodes shared between different components specify direct connections between those components (i.e. all identically-numbered nodes are electrically common to each other). Nodes with different numbers are electrically distinct from each other:



SPICE netlist:

```
* SPICE circuit
v1 1 0 ac 4 0
v2 2 1 ac 3 0
v3 3 1 ac 3 180
v4 4 1 ac 3 90
r1 2 0 1k
r2 3 0 1k
r3 4 0 1k
.ac lin 1 60 60
.print ac vm(2) vm(3) vm(4)
.print ac vp(2) vp(3) vp(4)
.end
```

SPICE version 2G6 analysis (edited for brevity):

freq	vm(2)	vm(3)	vm(4)
6.000E+01	7.000E+00	1.000E+00	5.000E+00
freq	vp(2)	vp(3)	vp(4)
6.000E+01	0.000E+00	2.105E-14	3.687E+01

The voltage at node 2 (with respect to ground, 0) is the simple sum of 4 Volts and 3 Volts because V_1 and V_2 are perfectly in sync with each other, analogous to a pair of DC voltage sources connected in series with polarities additive. This also explains the zero phase shift of node 2's voltage: the sum of those two sources is in-phase with our reference source V_1 (at 0 degrees phase angle).

The voltage at node 3 is only 1 Volt (the difference between 4 Volts and 3 Volts) because V_1 and V_3 are perfectly *opposed* to one another, analogous to a pair of DC voltage sources connected in series with polarities subtractive. The phase shift of this voltage is practically zero, the only reason for the miniscule non-zero phase result being imperfections in SPICE's AC analysis.

The voltage at node 4 has no DC analogue because here the two sources V_1 and V_4 are neither directly in sync with each other nor perfectly opposed to each other – instead, these two sources are 90 degrees out of phase with each other. Their phasor sum is 5 Volts for the same reason that a right triangle with opposite and adjacent side lengths of 4 and 3 will have a hypotenuse length of 5. Note that the phase angle of this voltage is neither 0 degrees nor 90 degrees, but instead is 36.87 degrees: the same angle one would expect between the 4-length and 5-length sides of a right triangle (i.e. $\cos^{-1}(\frac{4}{5}) = 36.87^\circ$).


It should be noted that early versions of SPICE such as 2G6 assumed phase angle unit of degrees, but many later versions assume *radians* when displaying phase angles. In order to specifically instruct modern versions of SPICE to display angles in degrees, the following “control” cards must be added to the netlist:

```
.control
set units=degrees
.endc
```

These cards may be added to the netlist “deck” anywhere between the first line (* SPICE circuit) and the last (.end).

 5.8 Transient analysis of discharging RC circuit

Circuit schematic diagram (with node numbers listed). Note how ground is defined in SPICE as node number *zero*. In this example we will pre-charge the capacitor to 5 Volts and analyze its discharge over time. The time-span for analysis is from $t = 0$ to $t = 250$ milliseconds, in 10 millisecond intervals:



First, showing the “printed” output option:

SPICE netlist:

```
* SPICE circuit
r1 1 0 1k
c1 1 0 47u ic=5
.tran 10m 250m uic
.print tran v(1)
.end
```

SPICE version 2G6 analysis (edited for brevity):

time	v(1)
0.000E+00	5.000E+00
1.000E-02	4.046E+00
2.000E-02	3.270E+00
3.000E-02	2.643E+00
4.000E-02	2.136E+00
5.000E-02	1.726E+00
6.000E-02	1.395E+00
7.000E-02	1.127E+00
8.000E-02	9.112E-01
9.000E-02	7.364E-01
1.000E-01	5.951E-01
1.100E-01	4.810E-01
1.200E-01	3.887E-01
1.300E-01	3.142E-01
1.400E-01	2.539E-01
1.500E-01	2.052E-01
1.600E-01	1.658E-01
1.700E-01	1.340E-01
1.800E-01	1.083E-01
1.900E-01	8.754E-02
2.000E-01	7.075E-02
2.100E-01	5.718E-02
2.200E-01	4.621E-02
2.300E-01	3.735E-02
2.400E-01	3.018E-02
2.500E-01	2.437E-02

Next, showing the “plotted” output option³:

SPICE netlist:


```
* SPICE circuit
r1 1 0 1k
c1 1 0 47u ic=5
.tran 10m 250m uic
.plot tran v(1)
.width out=80
.end
```

³SPICE assumes a 120-character width display, and so to fit the text output on a standard terminal the `.width` option must be invoked to set the display width at 80 characters

SPICE version 2G6 analysis (edited for brevity):


time	v(1)					
	0.000E+00	2.000E+00	4.000E+00	6.000E+00	8.000E+00	
0.000E+00	5.000E+00	.	.	*	.	.
1.000E-02	4.046E+00	.	.	*	.	.
2.000E-02	3.270E+00	.	.	*	.	.
3.000E-02	2.643E+00	.	.	*	.	.
4.000E-02	2.136E+00	.	.	*	.	.
5.000E-02	1.726E+00	.	.	*	.	.
6.000E-02	1.395E+00	.	.	*	.	.
7.000E-02	1.127E+00	.	.	*	.	.
8.000E-02	9.112E-01	.	.	*	.	.
9.000E-02	7.364E-01	.	.	*	.	.
1.000E-01	5.951E-01	.	.	*	.	.
1.100E-01	4.810E-01	.	.	*	.	.
1.200E-01	3.887E-01	.	.	*	.	.
1.300E-01	3.142E-01	.	.	*	.	.
1.400E-01	2.539E-01	.	.	*	.	.
1.500E-01	2.052E-01	.	.	*	.	.
1.600E-01	1.658E-01	.	.	*	.	.
1.700E-01	1.340E-01	.	.	*	.	.
1.800E-01	1.083E-01	.	.	*	.	.
1.900E-01	8.754E-02	.	.	*	.	.
2.000E-01	7.075E-02	*
2.100E-01	5.718E-02	*
2.200E-01	4.621E-02	*
2.300E-01	3.735E-02	*
2.400E-01	3.018E-02	*
2.500E-01	2.437E-02	*

 NGSPICE version 26 analysis (using window-based interactive mode on Linux/X-Windows):



 5.9 Transient analysis of a steady sinusoidal voltage source

Circuit schematic diagram (with node numbers listed). Note how ground is defined in SPICE as node number *zero*. In this example we will define a voltage source with a sinusoidal waveform, no DC offset, 120 Volt peak amplitude, 60 Hz frequency, no start delay, and no decay (i.e. an undamped waveform). The time-span for analysis is from $t = 0$ to $t = 34$ milliseconds, in 1 millisecond intervals:




SPICE netlist:

```
* SPICE circuit
v1 1 0 sin (0 120 60 0 0)
r1 1 0 10e3
.tran 1m 34m
.plot tran v(1)
.width out=80
.end
```

SPICE version 2G6 analysis (edited for brevity):


time	v(1)	-2.000E+02	-1.000E+02	0.000E+00	1.000E+02	2.000E+02
0.000E+00	0.000E+00	.	.	*	.	.
1.000E-03	4.387E+01	.	.	.	*	.
2.000E-03	8.104E+01	.	.	.	*	.
3.000E-03	1.071E+02	*
4.000E-03	1.181E+02	*
5.000E-03	1.125E+02	*
6.000E-03	9.108E+01	.	.	.	*	.
7.000E-03	5.690E+01	.	.	.	*	.
8.000E-03	1.473E+01	.	.	.	*	.
9.000E-03	-2.951E+01	.	.	*	.	.
1.000E-02	-6.961E+01	.	*	.	.	.
1.100E-02	-9.993E+01	.	*	.	.	.
1.200E-02	-1.162E+02	.	*	.	.	.
1.300E-02	-1.162E+02	.	*	.	.	.
1.400E-02	-9.982E+01	.	*	.	.	.
1.500E-02	-6.945E+01	.	*	.	.	.
1.600E-02	-2.933E+01	.	.	*	.	.
1.700E-02	1.492E+01	.	.	.	*	.
1.800E-02	5.707E+01	.	.	.	*	.
1.900E-02	9.120E+01	*
2.000E-02	1.125E+02	*
2.100E-02	1.180E+02	*
2.200E-02	1.070E+02	*
2.300E-02	8.091E+01	.	.	.	*	.
2.400E-02	4.346E+01	.	.	.	*	.
2.500E-02	-9.465E-02	.	.	*	.	.
2.600E-02	-4.363E+01	.	.	*	.	.
2.700E-02	-8.104E+01	.	*	.	.	.
2.800E-02	-1.071E+02	.	*	.	.	.
2.900E-02	-1.181E+02	*
3.000E-02	-1.125E+02	*
3.100E-02	-9.108E+01	.	*	.	.	.
3.200E-02	-5.690E+01	.	.	*	.	.
3.300E-02	-1.473E+01	.	.	*	.	.
3.400E-02	2.951E+01	.	.	.	*	.

 NGSPICE version 26 analysis (using window-based interactive mode on Linux/X-Windows):



 5.10 Transient analysis of a sinusoidal capacitive circuit

Circuit schematic diagram (with node numbers listed). Note how ground is defined in SPICE as node number *zero*. In this example we will define a voltage source with a sinusoidal waveform, no DC offset, 120 Volt peak amplitude, 60 Hz frequency, no start delay, and no decay (i.e. an undamped waveform). The time-span for analysis is from $t = 0$ to $t = 30$ milliseconds, in 1 millisecond intervals:




SPICE netlist:

```
* SPICE circuit
v1 1 0 sin (0 120 60 0 0)
c1 2 0 1500u
vamm 1 2 0
.tran 1m 30m
.plot tran v(1) i(vamm)
.width out=80
.end
```

SPICE version 2G6 analysis (edited for brevity):


legend:						
*: v(1)						
+: i(vamm)						
time	v(1)					
(*)-----	-2.000E+02	-1.000E+02	0.000E+00	1.000E+02	2.000E+02	
(+)-----	-1.000E+02	-5.000E+01	0.000E+00	5.000E+01	1.000E+02	
0.000E+00	0.000E+00	.	.	x	.	.
1.000E-03	4.390E+01	.	.	*	.	+
2.000E-03	8.203E+01	.	.	.	*	+
3.000E-03	1.080E+02	.	.	.	+	.*
4.000E-03	1.190E+02	.	.	+	.	*
5.000E-03	1.140E+02	.	.	+	.	*
6.000E-03	9.197E+01	*
7.000E-03	5.747E+01	.	.	.	*	.
8.000E-03	1.503E+01	.	.	.	*	.
9.000E-03	-2.971E+01
1.000E-02	-7.010E+01
1.100E-02	-1.012E+02
1.200E-02	-1.173E+02
1.300E-02	-1.172E+02
1.400E-02	-1.012E+02
1.500E-02	-7.015E+01
1.600E-02	-2.967E+01
1.700E-02	1.501E+01
1.800E-02	5.753E+01
1.900E-02	9.189E+01
2.000E-02	1.140E+02
2.100E-02	1.191E+02
2.200E-02	1.079E+02
2.300E-02	8.205E+01
2.400E-02	4.393E+01
2.500E-02	1.243E-02
2.600E-02	-4.411E+01
2.700E-02	-8.174E+01
2.800E-02	-1.079E+02
2.900E-02	-1.196E+02
3.000E-02	-1.141E+02

 NGSPICE version 26 analysis (using window-based interactive mode on Linux/X-Windows):



 5.11 Transient analysis of a damped, offset sinusoidal voltage source

Circuit schematic diagram (with node numbers listed). Note how ground is defined in SPICE as node number *zero*. In this example we will define a voltage source with a sinusoidal waveform, an 80 Volt DC offset, 120 Volt peak amplitude, 60 Hz frequency, no start delay, and a damping factor of 40 s^{-1} . The time-span for analysis is from $t = 0$ to $t = 34$ milliseconds, in 1 millisecond intervals:



SPICE netlist:


```
* SPICE circuit
v1 1 0 sin (80 120 60 0 40)
r1 1 0 10e3
.tran 1m 34m
.plot tran v(1)
.width out=80
.end
```

SPICE version 2G6 analysis (edited for brevity):


time	v(1)				
	0.000E+00	5.000E+01	1.000E+02	1.500E+02	2.000E+02
0.000E+00	8.000E+01	.	.	*	.
1.000E-03	1.221E+02	.	.	.	*
2.000E-03	1.552E+02	.	.	.	*
3.000E-03	1.759E+02	.	.	.	*
4.000E-03	1.812E+02	.	.	.	*
5.000E-03	1.733E+02	.	.	.	*
6.000E-03	1.522E+02	.	.	.	*
7.000E-03	1.237E+02	.	.	*	.
8.000E-03	9.098E+01	.	.	*	.
9.000E-03	5.922E+01	.	.	*	.
1.000E-02	3.321E+01	.	*	.	.
1.100E-02	1.497E+01	.	*	.	.
1.200E-02	7.632E+00	.	*	.	.
1.300E-02	1.023E+01	.	*	.	.
1.400E-02	2.246E+01	.	*	.	.
1.500E-02	4.146E+01	.	*	.	.
1.600E-02	6.426E+01	.	*	.	.
1.700E-02	8.750E+01	.	*	.	.
1.800E-02	1.079E+02	.	*	.	.
1.900E-02	1.229E+02	.	*	.	.
2.000E-02	1.311E+02	.	*	.	.
2.100E-02	1.313E+02	.	*	.	.
2.200E-02	1.250E+02	.	*	.	.
2.300E-02	1.125E+02	.	*	.	.
2.400E-02	9.691E+01	.	*	.	.
2.500E-02	8.008E+01	.	*	.	.
2.600E-02	6.442E+01	.	*	.	.
2.700E-02	5.238E+01	.	*	.	.
2.800E-02	4.469E+01	.	*	.	.
2.900E-02	4.274E+01	.	*	.	.
3.000E-02	4.577E+01	.	*	.	.
3.100E-02	5.339E+01	.	*	.	.
3.200E-02	6.399E+01	.	*	.	.
3.300E-02	7.596E+01	.	*	.	.
3.400E-02	8.766E+01	.	*	.	.

 5.11. TRANSIENT ANALYSIS OF A DAMPED, OFFSET SINUSOIDAL VOLTAGE SOURCE97

NGSPICE version 26 analysis (using window-based interactive mode on Microsoft Windows 7):




 NGSPICE version 26 analysis (using window-based interactive mode on Linux/X-Windows):



 5.12 Additive AC voltage sources with transient analysis

Circuit schematic diagram (with node numbers listed):




SPICE netlist:

```
* SPICE circuit
v1 1 0 sin (0 4 1k 0 0)
v2 2 1 sin (0 3 1k 0 0)
v3 3 1 sin (0 3 1k -0.5m 0)
v4 4 1 sin (0 3 1k -0.25m 0)
r1 2 0 1k
r2 3 0 1k
r3 4 0 1k
.tran 0.05m 4m
.plot tran v(1) v(2,1) v(3,1) v(4,1)
.plot tran v(2) v(3) v(4)
.end
```

Here, the phase shift of each sinusoidal voltage source must be specified in terms of *start delay time*. A 1000 Hertz waveform has a period of 1 millisecond, and therefore 180 degrees of phase shift is equivalent to a start delay of 0.5 milliseconds (i.e. one-half of the 360° period) and 90 degrees of phase shift is equivalent to a start delay of 0.25 milliseconds (i.e. one-quarter of the 360° period). The start delay times are shown here as negative quantities because we want the phase shifts to be *leading* (e.g. the V_3 sinusoidal source with a start delay of -0.5 milliseconds is already at its 180 degree mark by the time our reference source V_1 begins at 0 degrees.).

An important note here is that SPICE version 2G6 does not handle negative start delay time values, but NGSPICE version 26 does. For this reason, a SPICE version 2G6 analysis is omitted.

 NGSPICE version 26 analysis (using window-based interactive mode on Linux/X-Windows):




The voltage at node 2 (with respect to ground, 0) is the simple sum of 4 Volts and 3 Volts because V_1 and V_2 are perfectly in sync with each other, analogous to a pair of DC voltage sources connected in series with polarities additive. The voltage at node 3 is only 1 Volt (the difference between 4 Volts and 3 Volts) because V_1 and V_3 are perfectly *opposed* to one another, analogous to a pair of DC voltage sources connected in series with polarities subtractive.

The voltage at node 4 has no DC analogue because here the two sources V_1 and V_4 are neither directly in sync with each other nor perfectly opposed to each other – instead, these two sources are 90 degrees out of phase with each other. Their phasor sum is 5 Volts for the same reason that a right triangle with opposite and adjacent side lengths of 4 and 3 will have a hypotenuse length of 5.

Note how the voltage at node 4 does not peak at the same times as the voltages at nodes 2 or 3 because its phase shift is not 0 degrees as with the others.

 5.13 Solar cell array simulation

This simulation uses both subcircuits and semiconductor models to represent a solar (photovoltaic) panel comprised of four individual cells. Each cell is modeled by the `pvcell` subcircuit, while the four-cell series-parallel array calls on that subcircuit four times. In order to plot the array's voltage-current characteristic curve, we use an external current source as a controlled load (I_{load}) and “sweep” the load current from zero to the full short-circuit rating of the array. In this case, with four cells connected in series-parallel fashion we would expect an open-circuit voltage approximately equal to two diode forward voltage drops and a short-circuit current approximately equal to two cells' parallel-total current:




SPICE netlist:⁴

```
* SPICE circuit
x1 1 2 pvcell
x2 2 0 pvcell
x3 1 3 pvcell
x4 3 0 pvcell
iload 1 0
.subckt pvcell 1 3
rs 1 2 0.01
isc 3 2 1.5
d1 2 3 pnjunc
rp 2 3 5
.model pnjunc d is=1e-9 vj=0.65
.ends pvcell
.dc iload 0 3 0.01
.plot dc v(1)
```

⁴.`plot dc` statement intended to display the array's voltage as a function of load current.

```
.end
```

 NGSPICE version 26 analysis (using window-based interactive mode on Linux/X-Windows):




In this analysis we see the open-circuit condition represented at the far left of the graph (maximum voltage, zero current) and the short-circuit condition represented at the far right (zero voltage⁵, maximum current).

The amount of open-circuit voltage for each cell is primarily a function of the cell subcircuit's diode model (v_j parameter defining its nominal forward-voltage drop, and i_s parameter defining its saturation current). The amount of short-circuit current for each cell is primarily a function of the cell's current source (I_{sc}). The slope of the voltage-current curve toward the right-hand side is primarily a function of the cell's internal parallel resistance (R_p).

⁵We actually see the voltage dip slightly below zero at a load current of 3 Amperes, because at this point I_{load} is actually behaving as a *source* rather than a load. This demonstrates that the array's short-circuit capability is actually slightly less than 3 Amperes.

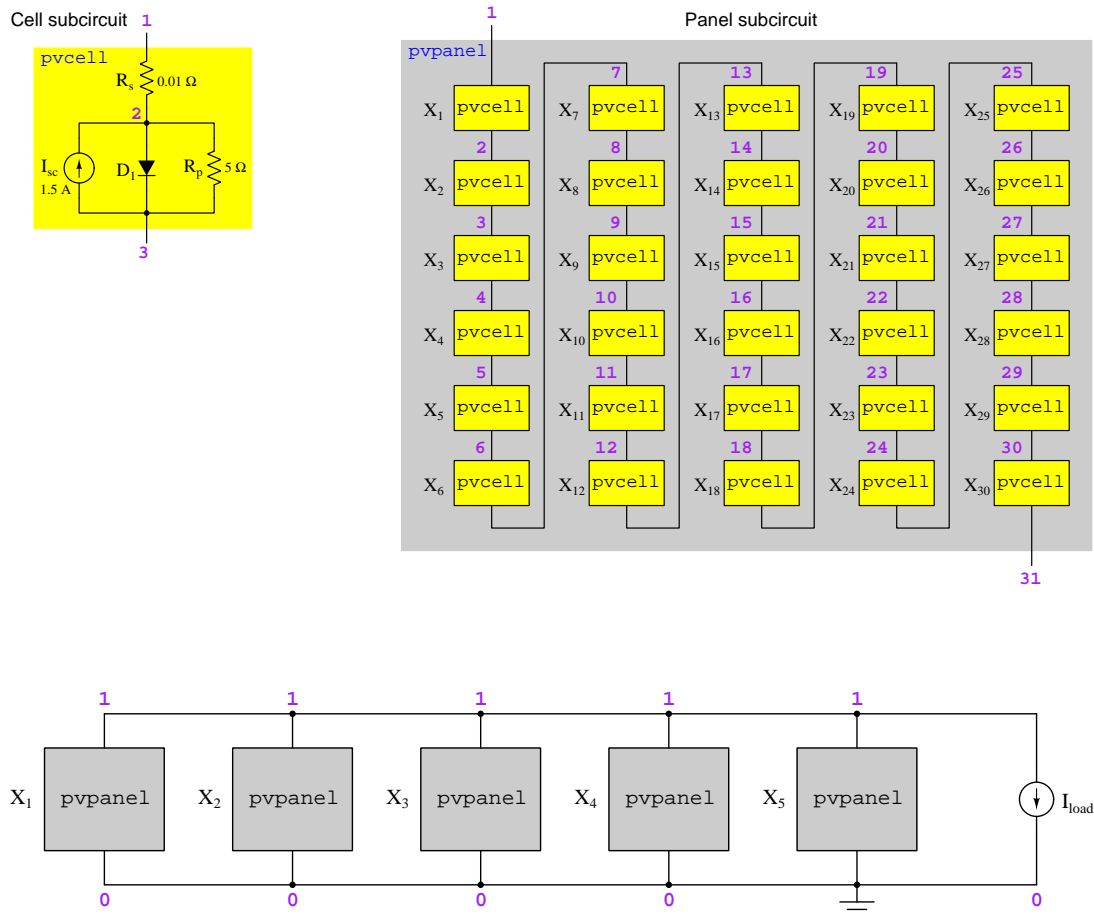5.14 Solar panel array simulation

This simulation uses nested subcircuits, the lowest-level subcircuit representing a single solar (photovoltaic) cell and the next-level subcircuit representing a single panel comprised of 30 of those cells. The top-level simulation uses five of those panels in parallel to power a test load.




SPICE netlist:⁶

```
* SPICE circuit
x1 1 0 pvpanel
x2 1 0 pvpanel
x3 1 0 pvpanel
x4 1 0 pvpanel
x5 1 0 pvpanel
iload 1 0
*
* Panel subcircuit
.subckt pvpanel 1 31
x1 1 2 pvcell
x2 2 3 pvcell
x3 3 4 pvcell
x4 4 5 pvcell
x5 5 6 pvcell
x6 6 7 pvcell
x7 7 8 pvcell
x8 8 9 pvcell
x9 9 10 pvcell
x10 10 11 pvcell
x11 11 12 pvcell
x12 12 13 pvcell
x13 13 14 pvcell
x14 14 15 pvcell
x15 15 16 pvcell
x16 16 17 pvcell
x17 17 18 pvcell
x18 18 19 pvcell
x19 19 20 pvcell
x20 20 21 pvcell
x21 21 22 pvcell
x22 22 23 pvcell
x23 23 24 pvcell
x24 24 25 pvcell
x25 25 26 pvcell
x26 26 27 pvcell
x27 27 28 pvcell
x28 28 29 pvcell
x29 29 30 pvcell
```

⁶.plot dc statement intended to display the array's voltage as a function of load current. Also note the addition comments (*) inserted to visually separate and clearly label the subcircuits, so as to distinguish them from the rest of the netlist code.

```
x30 30 31 pvcell
.ends pvpanel
*
* Cell subcircuit
.subckt pvcell 1 3
rs 1 2 0.01
Isc 3 2 1.5
d1 2 3 pnjunc
rp 2 3 5
.model pnjunc d is=1e-9 vj=0.65
.ends pvcell
*
.dc iload 0 7.5 0.01
.plot dc v(1)
.end
```

 NGSPICE version 26 analysis (using window-based interactive mode on Linux/X-Windows):



In this analysis we see the open-circuit condition represented at the far left of the graph (maximum voltage, zero current) and the short-circuit condition represented at the far right (zero voltage⁷, maximum current).

The amount of open-circuit voltage for each cell is primarily a function of the cell subcircuit's diode model (*vj* parameter defining its nominal forward-voltage drop, and *is* parameter defining its saturation current). The amount of short-circuit current for each cell is primarily a function of the cell's current source (I_{sc}). The slope of the voltage-current curve toward the right-hand side is primarily a function of the cell's internal parallel resistance (R_p).

One of the tremendous advantages of using subcircuits in SPICE netlists is also seen when using

⁷We actually see the voltage dip slightly below zero at a load current of 7.5 Amperes, because at this point I_{load} is actually behaving as a *source* rather than a load. This demonstrates that the array's short-circuit capability is actually slightly less than 7.5 Amperes.

subroutines in a computer programming language: by relegating the specific details of each solar cell to its own sub-set of the code, we may very easily make adjustments to that sub-set and watch the effects of those adjustments on the larger system. Imagine if we had to build a SPICE netlist without subcircuits, representing all 150 current sources, 150 diodes, 150 series resistors, and 150 parallel resistors! Not only would the netlist be enormous, but it would also be extremely tedious to alter any parameter(s) common to every cell.

Chapter 6

Gallery

All SPICE netlists showcased in this “Gallery” have been tested on two different versions of SPICE: SPICE version 2G6, and a modern variant of SPICE called NGSPICE (version 26 or newer). In most cases only one of these SPICE versions is used to generate the output.

When an analysis has been noted as “edited for brevity” it means that I have deleted unnecessary blank lines, unnecessary spaces, unnecessary characters, and all the statistical information typically output by SPICE in order to maximize the readability of the SPICE text output. This editing is especially important for those who wish to use the Gallery examples as practice problems (with answers provided by SPICE) for developing manual circuit analysis skills and do not care about the particulars of SPICE.

6.1 Using gallery examples for practice

Perhaps the most obvious use of the example netlists and analyses presented in this “Gallery” chapter is to learn how to write well-formed netlists for SPICE, and how to interpret the output generated by SPICE simulations. In other words, you may use these examples to help you learn how to use SPICE as a circuit simulation tool specific types of circuits.

However, this is not the only use of these examples. Students in quantitative fields of study such as electricity and electronics benefit from having sets of worked example problems to hone and test their burgeoning analytical skills. Textbooks commonly contain practice problems, followed by answers (at least for *some* of these problems!) located in an appendix against which students may self-check their own results. The SPICE example analyses presented in this “Gallery” chapter may serve as the same: sample problems complete with their own answer keys. Even more, once the basic syntax and netlist format of SPICE is mastered, students may use SPICE to generate answer keys for circuit problems of their own making, thus freeing them from the limitations of their textbooks’ problem sets.

Here are some suggestions for using the Gallery examples as practice problems:

1. Take the given information presented in the circuit schematic diagrams (also in the corresponding SPICE netlists) and use your analytical skills to calculate those same voltages and/or currents that SPICE is tasked with computing. When you think you have a complete analysis, turn to the SPICE analysis to check if your answers match.
2. Take the circuit schematic diagram and the results of the SPICE analysis as given parameters, and then use your analytical skills to “work backwards” to one or more of the specified component values in the SPICE netlist. For example, taking the schematic diagram and component voltage drops, and then calculating source voltage/current from that.
3. Modify component values within a SPICE netlist and re-run the analysis to make a new quantitative problem with different given conditions.
4. Use SPICE to predict the effects of *qualitative* changes by either increasing or decreasing any one component’s value and re-running the simulation, challenging yourself beforehand to predict all the effects of that qualitative change before letting SPICE tell you what will happen.
5. Use SPICE to predict the effects of *component faults* (e.g. opens and shorts) by altering resistance values to become very large (open) or very small (short), or by inserting high resistances in series with a component to simulate an “open” fault and low resistances in parallel to simulate a “short” fault. As with qualitative component value changes, you will challenge yourself beforehand to predict all the effects of that fault before letting SPICE tell you what will happen.


6.2 Three-phase AC direct-coupled circuits

In these circuits, a three-phase source directly connects to a three-phase load with no transformers in between.

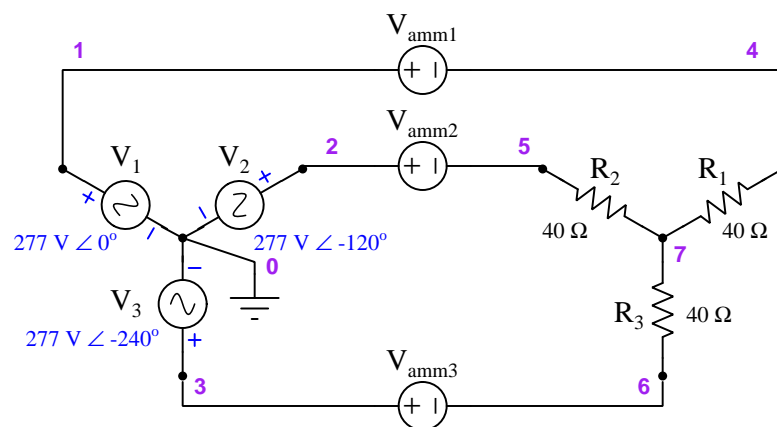6.2.1 Wye source, Wye load

Here we will analyze line and phase voltages as well as line currents in a balanced Wye-Wye system. The phase rotation is 1-2-3 as defined by the respective phase angles of the AC sources. Since this is a purely resistive circuit, frequency does not matter. The netlist will use 60 Hz as the single analysis frequency:

Circuit schematic diagram (with node numbers listed):



Note the use of DC voltage sources as line and phase ammeters. Early versions of SPICE were only able to display current values through voltage sources, and so here three DC voltage sources (with voltage values defaulting to zero, as will be unspecified in the netlist) are used as ammeters to sense current at different places in the circuit.

SPICE netlist:


```
* Wye source, Wye load
* 1-2-3 phase rotation, balanced source and load
v1 1 0 ac 277 0
v2 2 0 ac 277 -120
v3 3 0 ac 277 -240
r1 4 7 40
r2 5 7 40
r3 6 7 40
vamm1 1 4 0
vamm2 2 5 0
vamm3 3 6 0
.ac lin 1 60 60
.print ac vm(4,7) vp(4,7)
.print ac vm(5,7) vp(5,7)
.print ac vm(6,7) vp(6,7)
.print ac im(vamm1) ip(vamm1)
.print ac im(vamm2) ip(vamm2)
.print ac im(vamm3) ip(vamm3)
.print ac vm(4,5) vp(4,5)
.print ac vm(5,6) vp(5,6)
.print ac vm(6,4) vp(6,4)
.end
```

SPICE version 2G6 analysis (edited for brevity):

freq	vm(4,7)	vp(4,7)
6.000E+01	2.770E+02	7.349E-15
freq	vm(5,7)	vp(5,7)
6.000E+01	2.770E+02	-1.200E+02
freq	vm(6,7)	vp(6,7)
6.000E+01	2.770E+02	1.200E+02
freq	im(vamm1)	ip(vamm1)
6.000E+01	6.925E+00	7.349E-15
freq	im(vamm2)	ip(vamm2)
6.000E+01	6.925E+00	-1.200E+02
freq	im(vamm3)	ip(vamm3)
6.000E+01	6.925E+00	1.200E+02
freq	vm(4,5)	vp(4,5)
6.000E+01	4.798E+02	3.000E+01
freq	vm(5,6)	vp(5,6)
6.000E+01	4.798E+02	-9.000E+01
freq	vm(6,4)	vp(6,4)
6.000E+01	4.798E+02	1.500E+02

Note the symmetrical phase voltages: 277 Volts, at 0° (rounded from 7.349×10^{-15} degrees), -120° , and 120° for resistors 1, 2, and 3 respectively. Line currents are also symmetrical at 6.925 Amperes each, with the same phase angles. Line voltages are 479.8 Volts with phase angles displaced 30 degrees from the phase voltages, as is typical for balanced Wye-Delta translations.

 The following phasor diagram shows how phase and line voltages should relate between the nodes:




Note how the arrowhead of each vector contacts the node number first listed in parentheses in each `.print` card. This follows standard convention for polarity in SPICE: that first node number is the “+” pole and the second number is the “-” pole, just as polarity symbols and vector directions are commonly related to each other.

6.2.2 Wye source, Wye load with shunt resistors

As noted previously, legacy versions of SPICE were incapable of displaying current through any component except a voltage source, and so one work-around for measuring current at arbitrary points in a circuit was to insert 0 Volt DC sources to be used as ammeters. However, some modern versions of SPICE cannot display those current values in polar form (magnitude and phase angle), but only in rectangular form which is less relatable to meter and oscilloscope measurements.

An alternative method for measuring current via voltage is to insert a precision resistor (called a *shunt resistor*) in-line with the desired current, then use Ohm's Law to infer current from voltage. This technique, in fact, is commonly applied in real circuits where we must sense high values of current using nothing more than standard hand-held test equipment such as multimeters. To do this successfully, we must select shunt resistor sizes that will produce a high enough voltage drop to be easily measured yet not drop so much voltage that they interfere with the normal operation of the circuit. In SPICE simulations there is no such thing as a voltage too small to accurately measure, and so we may use extremely low-valued shunt resistors to infer current from voltage. A value I will use is 1 milliOhm, which is so small compared to the load resistance values as to be negligible. A 1 m Ω resistor, of course drops 1 milliVolt for every Ampere of current through it, and so the resulting voltage measurement values will need to be multiplied by a thousand (10^3) to reveal current magnitude. Phase shift will be the same for shunt resistor voltage and shunt resistor current because resistors have 0° impedance phase angles.

 Circuit schematic diagram (with node numbers listed):



SPICE netlist:

```
* Wye source, Wye load
* 1-2-3 phase rotation, balanced source and load
v1 1 0 ac 277 0
v2 2 0 ac 277 -120
v3 3 0 ac 277 -240
r1 4 7 90
r2 5 7 90
r3 6 7 90
rshunt1 1 4 1e-3
rshunt2 2 5 1e-3
rshunt3 3 6 1e-3
.ac lin 1 60 60
.control
set units=degrees
.endc
.print ac vm(4,7) vp(4,7)
.print ac vm(5,7) vp(5,7)
.print ac vm(6,7) vp(6,7)
.print ac vm(1,4) vp(1,4)
.print ac vm(2,5) vp(2,5)
.print ac vm(3,6) vp(3,6)
.print ac vm(4,5) vp(4,5)
.print ac vm(5,6) vp(5,6)
.print ac vm(6,4) vp(6,4)
.end
```

NGSPICE version 26 analysis (edited for brevity):

Index	frequency	mag(v(4)-v(7))	ph(v(4)-v(7))
0	6.000000e+01	2.769969e+02	0.000000e+00
Index	frequency	mag(v(5)-v(7))	ph(v(5)-v(7))
0	6.000000e+01	2.769969e+02	-1.20000e+02
Index	frequency	mag(v(6)-v(7))	ph(v(6)-v(7))
0	6.000000e+01	2.769969e+02	1.200000e+02
Index	frequency	mag(v(1)-v(4))	ph(v(1)-v(4))
0	6.000000e+01	3.077744e-03	0.000000e+00
Index	frequency	mag(v(2)-v(5))	ph(v(2)-v(5))
0	6.000000e+01	3.077744e-03	-1.20000e+02
Index	frequency	mag(v(3)-v(6))	ph(v(3)-v(6))
0	6.000000e+01	3.077744e-03	1.200000e+02

The voltage measurements taken across each of the shunt resistors read 3.077744×10^{-3} Volts, which of course is 1000 times smaller than the current value in Amperes due to the shunt resistors being $1 \text{ m}\Omega$ each. Therefore, line current in this three-phase circuit is 3.077744 Amperes. This simulated result is *very slightly less* than what theory would predict (3.077778 Amperes) due to the effect of the shunt resistors' added resistance to the circuit.


The remainder of the analysis is shown on the next page.

Index	frequency	mag(v(4)-v(5))	ph(v(4)-v(5))
0	6.000000e+01	4.797727e+02	3.000000e+01
Index	frequency	mag(v(5)-v(6))	ph(v(5)-v(6))
0	6.000000e+01	4.797727e+02	-9.000000e+01
Index	frequency	mag(v(6)-v(4))	ph(v(6)-v(4))
0	6.000000e+01	4.797727e+02	1.500000e+02

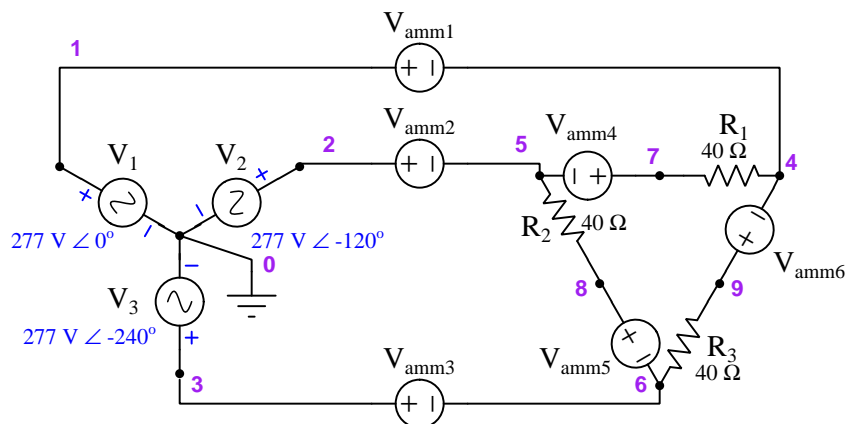6.2.3 Wye source, Delta load

Here we will analyze line and phase voltages as well as line currents in a balanced Wye-Delta system. The phase rotation is 1-2-3 as defined by the respective phase angles of the AC sources. Since this is a purely resistive circuit, frequency does not matter. The netlist will use 60 Hz as the single analysis frequency:

Circuit schematic diagram (with node numbers listed):



Note the use of DC voltage sources as line ammeters. Early versions of SPICE were only able to display current values through voltage sources, and so here three DC voltage sources (with voltage values defaulting to zero, as will be unspecified in the netlist) are used to connect the source to the load.

SPICE netlist:

```
* Wye source, Delta load
* 1-2-3 phase rotation, balanced source and load
v1 1 0 ac 277 0
v2 2 0 ac 277 -120
v3 3 0 ac 277 -240
vamm1 1 4 0
vamm2 2 5 0
vamm3 3 6 0
r1 4 7 40
r2 5 8 40
r3 6 9 40
vamm4 7 5 0
vamm5 8 6 0
vamm6 9 4 0
.ac lin 1 60 60
.control
set units=degrees
.endc
.print ac vm(1) vp(1)
.print ac vm(2) vp(2)
.print ac vm(3) vp(3)
.print ac i(vamm1)
.print ac i(vamm2)
.print ac i(vamm3)
.print ac i(vamm4)
.print ac i(vamm5)
.print ac i(vamm6)
.print ac vm(4,5) vp(4,5)
.print ac vm(5,6) vp(5,6)
.print ac vm(6,4) vp(6,4)
.end
```

NGSPICE version 26 analysis (edited for brevity):


Index	frequency	vm(1)	vp(1)
0	6.000000e+01	2.770000e+02	0.000000e+00
Index	frequency	vm(2)	vp(2)
0	6.000000e+01	2.770000e+02	-1.20000e+02
Index	frequency	vm(3)	vp(3)
0	6.000000e+01	2.770000e+02	1.200000e+02
Index	frequency	vamm1#branch	
0	6.000000e+01	2.077500e+01,	2.664535e-15
Index	frequency	vamm2#branch	
0	6.000000e+01	-1.03875e+01,	-1.79917e+01
Index	frequency	vamm3#branch	
0	6.000000e+01	-1.03875e+01,	1.799168e+01
Index	frequency	vamm4#branch	
0	6.000000e+01	1.038750e+01,	5.997226e+00
Index	frequency	vamm5#branch	
0	6.000000e+01	4.440892e-15,	-1.19945e+01

Index	frequency	vamm6#branch	
0	6.000000e+01	-1.03875e+01,	5.997226e+00
Index	frequency	mag(v(4)-v(5))	ph(v(4)-v(5))
0	6.000000e+01	4.797781e+02	3.000000e+01
Index	frequency	mag(v(5)-v(6))	ph(v(5)-v(6))
0	6.000000e+01	4.797781e+02	-9.00000e+01
Index	frequency	mag(v(6)-v(4))	ph(v(6)-v(4))
0	6.000000e+01	4.797781e+02	1.500000e+02

Sadly, NGSPICE does not yet (at least at the time of this writing in 2019) support polar representation of current values, but only for voltage values. The current in each case, measured through the “amm” voltage sources, is displayed as phasor numbers in *rectangular* form. For example, the reported current through vamm5 is $4.440892 \times 10^{-15} - j1.19945 \times 10^1$ Amperes, which is 11.9945 Amperes $\angle -90^\circ$; the reported current through vamm6 is $-1.03875 \times 10^1 + j5.997226 \times 10^0$ Amperes, which is 11.9945 Amperes $\angle 150^\circ$.

Note the symmetrical phase voltages for the Delta-connected load: 479.7781 Volts, at 30° , -90° , and 150° for resistors 1, 2, and 3 respectively. This magnitude for Delta phase voltage is precisely what we would expect for a balanced three-phase network powered by a Wye source having phase voltages of 277 Volts each, because $277\sqrt{3} = 479.7781$ Volts.

 The following phasor diagram shows how phase and line voltages should relate between the nodes:




Note how the arrowhead of each vector contacts the node number first listed in parentheses in each `.print` card. This follows standard convention for polarity in SPICE: that first node number is the “+” pole and the second number is the “-” pole, just as polarity symbols and vector directions are commonly related to each other.

6.2.4 Wye source, Delta load with shunt resistors

As noted previously, legacy versions of SPICE were incapable of displaying current through any component except a voltage source, and so one work-around for measuring current at arbitrary points in a circuit was to insert 0 Volt DC sources to be used as ammeters. However, some modern versions of SPICE cannot display those current values in polar form (magnitude and phase angle), but only in rectangular form which is less relatable to meter and oscilloscope measurements.

An alternative method for measuring current via voltage is to insert a precision resistor (called a *shunt resistor*) in-line with the desired current, then use Ohm's Law to infer current from voltage. This technique, in fact, is commonly applied in real circuits where we must sense high values of current using nothing more than standard hand-held test equipment such as multimeters. To do this successfully, we must select shunt resistor sizes that will produce a high enough voltage drop to be easily measured yet not drop so much voltage that they interfere with the normal operation of the circuit. In SPICE simulations there is no such thing as a voltage too small to accurately measure, and so we may use extremely low-valued shunt resistors to infer current from voltage. A value I will use is 1 milliOhm, which is so small compared to the load resistance values as to be negligible. A 1 m Ω resistor, of course drops 1 milliVolt for every Ampere of current through it, and so the resulting voltage measurement values will need to be multiplied by a thousand (10^3) to reveal current magnitude. Phase shift will be the same for shunt resistor voltage and shunt resistor current because resistors have 0° impedance phase angles.

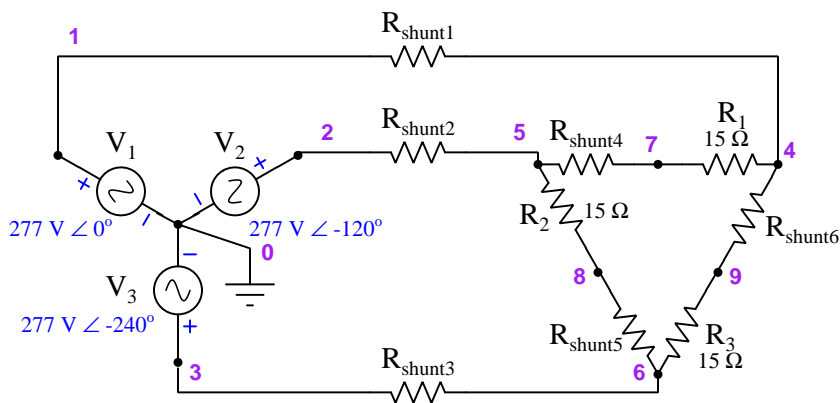Circuit schematic diagram (with node numbers listed):



SPICE netlist:

```
* Wye source, Delta load with shunt resistors
* 1-2-3 phase rotation, balanced source and load
v1 1 0 ac 277 0
v2 2 0 ac 277 -120
v3 3 0 ac 277 -240
rshunt1 1 4 1e-3
rshunt2 2 5 1e-3
rshunt3 3 6 1e-3
r1 4 7 15
r2 5 8 15
r3 6 9 15
rshunt4 7 5 1e-3
rshunt5 8 6 1e-3
rshunt6 9 4 1e-3
.ac lin 1 60 60
.control
set units=degrees
.endc
.print ac vm(1) vp(1)
.print ac vm(2) vp(2)
.print ac vm(3) vp(3)
.print ac vm(1,4) vp(1,4)
.print ac vm(2,5) vp(2,5)
.print ac vm(3,6) vp(3,6)
.print ac vm(7,5) vp(7,5)
.print ac vm(8,6) vp(8,6)
.print ac vm(9,4) vp(9,4)
.print ac vm(4,5) vp(4,5)
.print ac vm(5,6) vp(5,6)
.print ac vm(6,4) vp(6,4)
.end
```

NGSPICE version 26 analysis (edited for brevity):

Index	frequency	vm(1)	vp(1)
0	6.000000e+01	2.770000e+02	0.000000e+00
Index	frequency	vm(2)	vp(2)
0	6.000000e+01	2.770000e+02	-1.20000e+02
Index	frequency	vm(3)	vp(3)
0	6.000000e+01	2.770000e+02	1.200000e+02
Index	frequency	mag(v(1)-v(4))	ph(v(1)-v(4))
0	6.000000e+01	5.538523e-02	1.102433e-14
Index	frequency	mag(v(2)-v(5))	ph(v(2)-v(5))
0	6.000000e+01	5.538523e-02	-1.20000e+02
Index	frequency	mag(v(3)-v(6))	ph(v(3)-v(6))
0	6.000000e+01	5.538523e-02	1.200000e+02

The voltage measurements taken across each of the line shunt resistors read 5.538523×10^{-2} Volts, which of course is 1000 times smaller than the current value in Amperes due to the shunt resistors being $1 \text{ m}\Omega$ each. Therefore, line current in this three-phase circuit is 55.38523 Amperes.

The remainder of the analysis is shown on the next page.

Index	frequency	mag(v(7)-v(5))	ph(v(7)-v(5))
0	6.000000e+01	3.197668e-02	3.000000e+01
Index	frequency	mag(v(8)-v(6))	ph(v(8)-v(6))
0	6.000000e+01	3.197668e-02	-9.000000e+01
Index	frequency	mag(v(9)-v(4))	ph(v(9)-v(4))
0	6.000000e+01	3.197668e-02	1.500000e+02
Index	frequency	mag(v(4)-v(5))	ph(v(4)-v(5))
0	6.000000e+01	4.796821e+02	3.000000e+01
Index	frequency	mag(v(5)-v(6))	ph(v(5)-v(6))
0	6.000000e+01	4.796821e+02	-9.000000e+01
Index	frequency	mag(v(6)-v(4))	ph(v(6)-v(4))
0	6.000000e+01	4.796821e+02	1.500000e+02


The phase shunt resistors register 3.197668×10^{-2} Volts apiece, which again needs to be multiplied by 1000 to yield current in Amperes (31.97668 A).

It is worth noting that both sets of current measurements are *slightly* less than what theory would predict (55.400 Amperes for line current and 31.985 Amperes for Delta phase current). This is due to the influence of the shunt resistors' added resistance to the circuit. If more accurate results were necessary, we could make the shunt resistances smaller by orders of magnitude, perhaps $1 \mu\Omega$ instead of $1 \text{ m}\Omega$ apiece. Then we would need to remember to multiply the voltage values by a greater multiplier in order to calculate current.

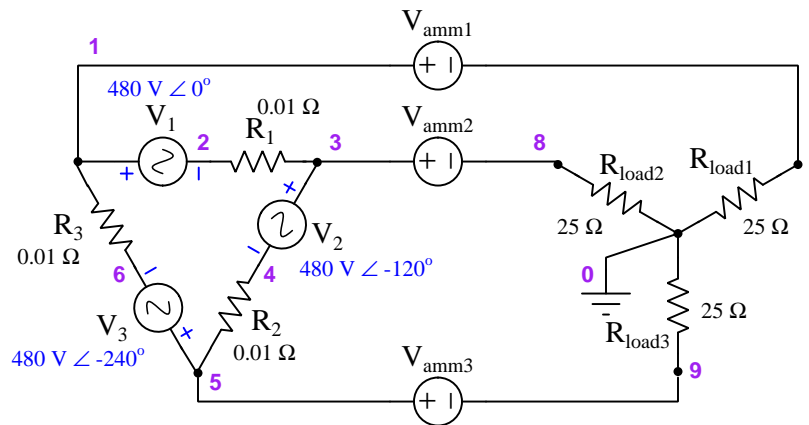6.2.5 Delta source, Wye load

Here we will analyze line and phase voltages as well as line currents in a balanced Delta-Wye system. The phase rotation is 1-2-3 as defined by the respective phase angles of the AC sources. Since this is a purely resistive circuit, frequency does not matter. The netlist will use 60 Hz as the single analysis frequency:

Circuit schematic diagram (with node numbers listed):



Note the use of DC voltage sources as line ammeters. Early versions of SPICE were only able to display current values through voltage sources, and so here three DC voltage sources (with voltage values defaulting to zero, as will be unspecified in the netlist) are used to connect the source to the load. Note also the inclusion of low-valued resistors in the Delta source, in order to break up what would otherwise be a “loop” of three voltage sources, which SPICE cannot tolerate.

SPICE netlist:

```
* Delta-connected three-phase source with Wye load
* 1-2-3 phase rotation
v1 1 2 ac 480 0
r1 2 3 0.01
v2 3 4 ac 480 -120
r2 4 5 0.01
v3 5 6 ac 480 -240
r3 6 1 0.01
vamm1 1 7 0
vamm2 3 8 0
vamm3 5 9 0
rload1 7 0 25
rload2 8 0 25
rload3 9 0 25
.ac lin 1 60 60
.print ac vm(7) vp(7)
.print ac vm(8) vp(8)
.print ac vm(9) vp(9)
.print ac im(vamm1) ip(vamm1)
.print ac im(vamm2) ip(vamm2)
.print ac im(vamm3) ip(vamm3)
.end
```


SPICE version 2G6 analysis (edited for brevity):

freq	vm(7)	vp(7)
6.000E+01	2.771E+02	-3.000E+01
freq	vm(8)	vp(8)
6.000E+01	2.771E+02	-1.500E+02
freq	vm(9)	vp(9)
6.000E+01	2.771E+02	9.000E+01
freq	im(vamm1)	ip(vamm1)
6.000E+01	1.108E+01	-3.000E+01
freq	im(vamm2)	ip(vamm2)
6.000E+01	1.108E+01	-1.500E+02
freq	im(vamm3)	ip(vamm3)
6.000E+01	1.108E+01	9.000E+01

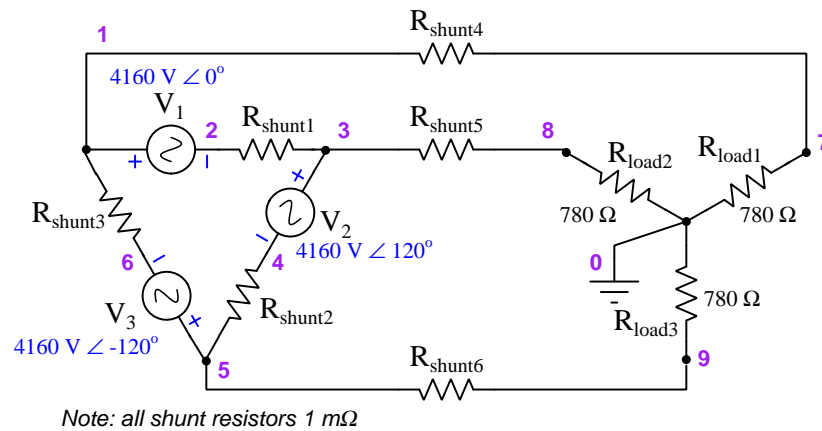6.2.6 Delta source, Wye load with shunt resistors

Here we will analyze line and phase voltages as well as line currents in a balanced Delta-Wye system. The phase rotation is 3-2-1 as defined by the respective phase angles of the AC sources. Since this is a purely resistive circuit, frequency does not matter. The netlist will use 60 Hz as the single analysis frequency:

Circuit schematic diagram (with node numbers listed):



Note the use of shunt resistors in the line for current measurement. This is an accommodation for certain versions of SPICE which cannot display current values through any component but a voltage source, or which cannot display current phase shifts and magnitudes. Here we will monitor the voltage across each shunt resistor and use those measurements to infer current. The inclusion of shunt resistors inside the Delta-connected source also serves the purpose of breaking up what would otherwise be a “loop” of three voltage sources, which SPICE cannot tolerate.

SPICE netlist:

```
* Delta-connected three-phase source with Wye load
* 3-2-1 phase rotation
v1 1 2 ac 4160 0
rshunt1 2 3 1m
v2 3 4 ac 4160 120
rshunt2 4 5 1m
v3 5 6 ac 4160 -120
rshunt3 6 1 1m
rshunt4 1 7 1m
rshunt5 3 8 1m
rshunt6 5 9 1m
rload1 7 0 780
rload2 8 0 780
rload3 9 0 780
.ac lin 1 60 60
.print ac vm(7) vp(7)
.print ac vm(8) vp(8)
.print ac vm(9) vp(9)
.print ac vm(1,7) vp(1,7)
.print ac vm(3,8) vp(3,8)
.print ac vm(5,9) vp(5,9)
.end
```


SPICE version 2G6 analysis (edited for brevity):

freq	vm(7)	vp(7)
6.000E+01	2.402E+03	3.000E+01
freq	vm(8)	vp(8)
6.000E+01	2.402E+03	1.500E+02
freq	vm(9)	vp(9)
6.000E+01	2.402E+03	-9.000E+01
freq	vm(1,7)	vp(1,7)
6.000E+01	3.119E-03	3.058E+01
freq	vm(3,8)	vp(3,8)
6.000E+01	3.119E-03	1.494E+02
freq	vm(5,9)	vp(5,9)
6.000E+01	3.174E-03	-9.000E+01

Current through the three line shunt resistors is inferred by Ohm's Law ($I = \frac{V}{R}$) where R is $1 \times 10^{-3} \Omega$ in each case. Thus, a voltage drop of 3.119E-03 Volts represents an inferred current of 3.119 Amperes. The phase angles of the shunt resistor voltages are equal to the phase angles of those currents, since resistance has an impedance angle of 0° (i.e. there is zero phase shift between the current through a resistor and the voltage dropped across that resistor).

This next netlist has been set up for a more modern version of SPICE, NGSPICE (version 26). This version of SPICE defaults to phase angles in units of *radians* rather than *degrees*, and so a few extra lines of code are necessary to command SPICE to display angles in degrees:

```
* Delta-connected three-phase source with Wye load
* 3-2-1 phase rotation
v1 1 2 ac 4160 0
rshunt1 2 3 1m
v2 3 4 ac 4160 120
rshunt2 4 5 1m
v3 5 6 ac 4160 -120
rshunt3 6 1 1m
rshunt4 1 7 1m
rshunt5 3 8 1m
rshunt6 5 9 1m
rload1 7 0 780
rload2 8 0 780
rload3 9 0 780
.ac lin 1 60 60
.control
set units=degrees
.endc
.print ac vm(7) vp(7)
.print ac vm(8) vp(8)
.print ac vm(9) vp(9)
.print ac vm(1,7) vp(1,7)
.print ac vm(3,8) vp(3,8)
.print ac vm(5,9) vp(5,9)
.end
```

NGSPICE version 26 analysis (edited for brevity):


Index	frequency	vm(7)	vp(7)
0	6.000000e+01	2.401773e+03	3.000000e+01
Index	frequency	vm(8)	vp(8)
0	6.000000e+01	2.401773e+03	1.500000e+02
Index	frequency	vm(9)	vp(9)
0	6.000000e+01	2.401773e+03	-9.00000e+01
Index	frequency	mag(v(1)-v(7))	ph(v(1)-v(7))
0	6.000000e+01	3.079196e-03	3.000000e+01
Index	frequency	mag(v(3)-v(8))	ph(v(3)-v(8))
0	6.000000e+01	3.079196e-03	1.500000e+02
Index	frequency	mag(v(5)-v(9))	ph(v(5)-v(9))
0	6.000000e+01	3.079196e-03	-9.00000e+01

It is interesting to note how the figures calculated by NGSPICE are more accurate than those calculated by SPICE version 2G6. Line current as shown by NGSPICE is much closer to the true value of 3.0792014 Amperes predicted by theory than the legacy SPICE. Regardless of the SPICE version used, none of the calculated values will be *perfect* because the inclusion of shunt resistors in the circuit slightly affects the outcome. This is why shunt resistor values were chosen to be arbitrarily small (only one milliOhm apiece), in order to skew the results as little as possible.

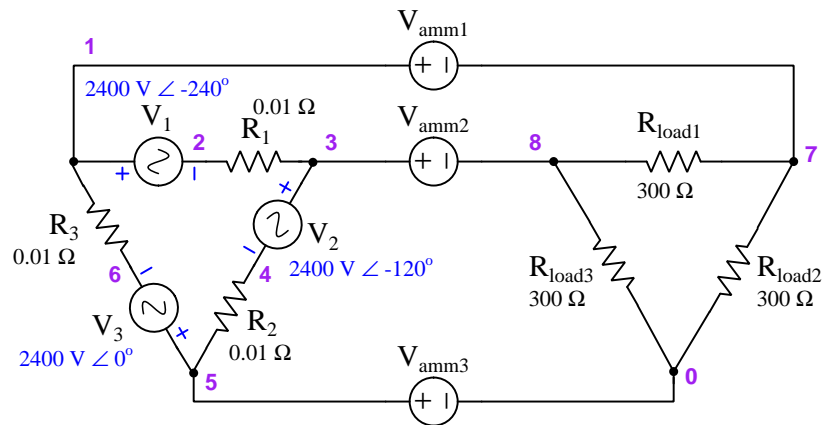6.2.7 Delta source, Delta load

Here we will analyze line and phase voltages as well as line currents in a balanced Delta-Delta system. The phase rotation is 3-2-1 as defined by the respective phase angles of the AC sources. Since this is a purely resistive circuit, frequency does not matter. The netlist will use 60 Hz as the single analysis frequency:

Circuit schematic diagram (with node numbers listed):



Note the use of DC voltage sources as line ammeters. Early versions of SPICE were only able to display current values through voltage sources, and so here three DC voltage sources (with voltage values defaulting to zero, as will be unspecified in the netlist) are used to connect the source to the load. Note also the inclusion of low-valued resistors in the Delta source, in order to break up what would otherwise be a “loop” of three voltage sources, which SPICE cannot tolerate.

SPICE netlist:

```
* Delta-connected three-phase source with Delta load
* 3-2-1 phase rotation
v1 1 2 ac 2.4k -240
r1 2 3 0.01
v2 3 4 ac 2.4k -120
r2 4 5 0.01
v3 5 6 ac 2.4k 0
r3 6 1 0.01
vamm1 1 7 0
vamm2 3 8 0
vamm3 5 0 0
rload1 7 8 300
rload2 7 0 300
rload3 8 0 300
.ac lin 1 60 60
.print ac vm(8,7) vp(8,7)
.print ac vm(7) vp(7)
.print ac vm(0,8) vp(0,8)
.print ac im(vamm1) ip(vamm1)
.print ac im(vamm2) ip(vamm2)
.print ac im(vamm3) ip(vamm3)
.end
```

SPICE version 2G6 analysis (edited for brevity):

freq	vm(8,7)	vp(8,7)
6.000E+01	2.400E+03	-6.000E+01
freq	vm(7)	vp(7)
6.000E+01	2.400E+03	-1.800E+02
freq	vm(0,8)	vp(0,8)
6.000E+01	2.400E+03	6.000E+01
freq	im(vamm1)	ip(vamm1)
6.000E+01	1.386E+01	1.500E+02
freq	im(vamm2)	ip(vamm2)
6.000E+01	1.386E+01	-9.000E+01
freq	im(vamm3)	ip(vamm3)
6.000E+01	1.386E+01	3.000E+01

NGSPICE version 26 does not support magnitude and phase (i.e. polar complex) analyses of current, only voltage. Furthermore, NGSPICE defaults to units of radians rather than degrees, and so some special cards must be added to the netlist deck in order to specify degrees as the unit of measurement for phase angle.

NGSPICE netlist:

```
* Delta-connected three-phase source with Delta load
* 3-2-1 phase rotation
* written for NGSPICE (setting units to degrees)
v1 1 2 ac 2.4k -240
r1 2 3 0.01
v2 3 4 ac 2.4k -120
r2 4 5 0.01
v3 5 6 ac 2.4k 0
r3 6 1 0.01
vamm1 1 7 0
vamm2 3 8 0
vamm3 5 0 0
rload1 7 8 300
rload2 7 0 300
rload3 8 0 300
.ac lin 1 60 60
.control
set units=degrees
.endc
.print ac vm(8,7) vp(8,7)
.print ac vm(7) vp(7)
.print ac vm(0,8) vp(0,8)
.print ac i(vamm1)
.print ac i(vamm2)
.print ac i(vamm3)
.end
```

NGSPICE version 26 analysis (edited for brevity):


-----	-----	-----	-----
Index	frequency	mag(v(8)-v(7))	ph(v(8)-v(7))
-----	-----	-----	-----
0	6.000000e+01	2.399920e+03	-6.000000e+01
-----	-----	-----	-----
Index	frequency	vm(7)	vp(7)
-----	-----	-----	-----
0	6.000000e+01	2.399920e+03	1.800000e+02
-----	-----	-----	-----
Index	frequency	mag(-v(8))	ph(-v(8))
-----	-----	-----	-----
0	6.000000e+01	2.399920e+03	6.000000e+01
-----	-----	-----	-----
Index	frequency	vamm1#branch	
-----	-----	-----	-----
0	6.000000e+01	-1.19996e+01,	6.927972e+00
-----	-----	-----	-----
Index	frequency	vamm2#branch	
-----	-----	-----	-----
0	6.000000e+01	4.547144e-15,	-1.38559e+01
-----	-----	-----	-----
Index	frequency	vamm3#branch	
-----	-----	-----	-----
0	6.000000e+01	1.199960e+01,	6.927972e+00
-----	-----	-----	-----

The current values shown here are in NGSPICE's default format of *rectangular* complex numbers. For example, the current through vamm1 is $-11.9996 + j6.927972$ Amperes AC.

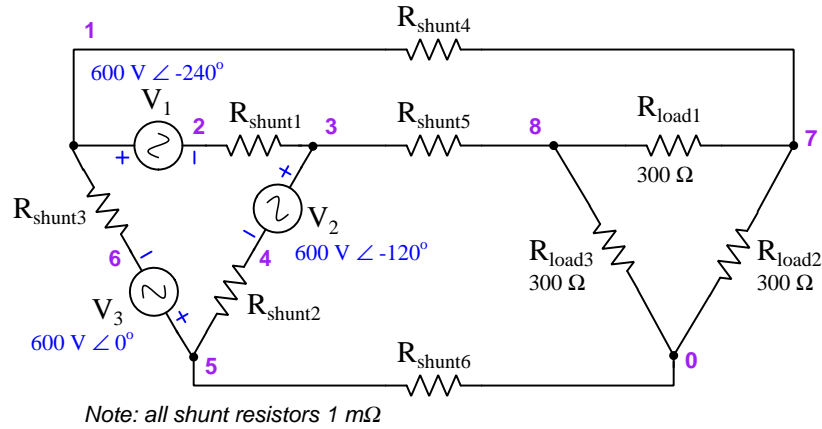6.2.8 Delta source, Delta load with shunt resistors

Here we will analyze line and phase voltages as well as line currents in a balanced Delta-Delta system. The phase rotation is 3-2-1 as defined by the respective phase angles of the AC sources. Since this is a purely resistive circuit, frequency does not matter. The netlist will use 60 Hz as the single analysis frequency:

Circuit schematic diagram (with node numbers listed):



Rather than 0-Volt DC sources used as ammeters, we will install low-valued shunt resistors wherever we wish to sense current in the circuit. These shunt resistors will be given arbitrarily low values (1 milliOhm each) so as to not adversely affect the circuit's operation by their presence, and yet be able to serve as tools for inferring current by virtue of their values being a simple power of ten. In other words, all we will need to do is multiply the voltage drop across each of these shunt resistors by 1000 (10^3) to infer current, because each shunt resistor's value is $\frac{1}{1000} \Omega$.

Shunt resistors are also useful in this circuit for an entirely different purpose, and that is to "break up" what would otherwise be a loop of voltage sources in the Delta source network. SPICE cannot handle loops comprised only of voltage sources, and so we must insert resistances in series with these voltage sources anyway to avoid this problem. Those resistances might as well be shunt resistors serving an additional purpose of easy current measurement.

SPICE netlist:

```
* Delta-connected three-phase source with Delta load
* 3-2-1 phase rotation
v1 1 2 ac 600 -240
rshunt1 2 3 1e-3
v2 3 4 ac 600 -120
rshunt2 4 5 1e-3
v3 5 6 ac 600 0
rshunt3 6 1 1e-3
rshunt4 1 7 1e-3
rshunt5 3 8 1e-3
rshunt6 5 0 1e-3
rload1 7 8 300
rload2 7 0 300
rload3 8 0 300
.ac lin 1 60 60
.print ac vm(3,2) vp(3,2)
.print ac vm(5,4) vp(5,4)
.print ac vm(1,6) vp(1,6)
.print ac vm(1,7) vp(1,7)
.print ac vm(3,8) vp(3,8)
.print ac vm(5) vp(5)
.end
```

SPICE version 2G6 analysis (edited for brevity):

freq	vm(3,2)	vp(3,2)
6.000E+01	2.036E-03	1.196E+02
freq	vm(5,4)	vp(5,4)
6.000E+01	2.000E-03	-1.200E+02
freq	vm(1,6)	vp(1,6)
6.000E+01	2.014E-03	0.000E+00
freq	vm(1,7)	vp(1,7)
6.000E+01	3.456E-03	1.499E+02
freq	vm(3,8)	vp(3,8)
6.000E+01	3.418E-03	-9.000E+01
freq	vm(5)	vp(5)
6.000E+01	3.464E-03	3.000E+01

As you can see, every `.print` instruction in our SPICE netlist is intended to show voltage dropped across a shunt resistor, and so each of these values reflects a current somewhere in the circuit. The first three are phase currents at the source, and the next three are line currents. Our values for phase voltage and phase current in this circuit are simple enough (600 Volts, and 300 Ohms) that the calculation for phase current is trivial (2 Amperes). Line current, being the phasor sum of phase currents at each corner of each Delta network, is simply $2\sqrt{3}$ or 3.4641 Amperes. Note how SPICE 2G6 struggles a bit to provide 100% accurate representations of these currents.

In our next simulation we will use NGSPICE rather than a legacy version of SPICE, and include a “control” statement in the netlist specifying the unit of angle measurement to be degrees rather than radians. SPICE version 2G6 assumed degrees, but many modern versions of SPICE such as NGSPICE default to radians instead of degrees.

NGSPICE version 26 netlist:

```
* Delta-connected three-phase source with Delta load
* 3-2-1 phase rotation
v1 1 2 ac 600 -240
rshunt1 2 3 1e-3
v2 3 4 ac 600 -120
rshunt2 4 5 1e-3
v3 5 6 ac 600 0
rshunt3 6 1 1e-3
rshunt4 1 7 1e-3
rshunt5 3 8 1e-3
rshunt6 5 0 1e-3
rload1 7 8 300
rload2 7 0 300
rload3 8 0 300
.ac lin 1 60 60
.control
set units = degrees
.endc
.print ac vm(3,2) vp(3,2)
.print ac vm(5,4) vp(5,4)
.print ac vm(1,6) vp(1,6)
.print ac vm(1,7) vp(1,7)
.print ac vm(3,8) vp(3,8)
.print ac vm(5) vp(5)
.end
```

NGSPICE version 26 analysis (edited for brevity):


-----	-----	-----	-----
Index	frequency	mag(v(3)-v(2))	ph(v(3)-v(2))
-----	-----	-----	-----
0	6.000000e+01	1.999973e-03	1.200000e+02
-----	-----	-----	-----
Index	frequency	mag(v(5)-v(4))	ph(v(5)-v(4))
-----	-----	-----	-----
0	6.000000e+01	1.999973e-03	-1.20000e+02
-----	-----	-----	-----
Index	frequency	mag(v(1)-v(6))	ph(v(1)-v(6))
-----	-----	-----	-----
0	6.000000e+01	1.999973e-03	-1.86133e-09
-----	-----	-----	-----
Index	frequency	mag(v(1)-v(7))	ph(v(1)-v(7))
-----	-----	-----	-----
0	6.000000e+01	3.464055e-03	1.500000e+02
-----	-----	-----	-----
Index	frequency	mag(v(3)-v(8))	ph(v(3)-v(8))
-----	-----	-----	-----
0	6.000000e+01	3.464055e-03	-9.00000e+01
-----	-----	-----	-----
Index	frequency	vm(5)	vp(5)
-----	-----	-----	-----
0	6.000000e+01	3.464055e-03	3.000000e+01

As you can see, NGSPICE does a more accurate job of calculating phase and line currents for this circuit than SPICE 2G6: all currents are balanced rather than slightly unbalanced as they were in the SPICE 2G6 analysis, and their values are closer to that predicted by theory. Theory tells us phase current should be 2 Amperes, and here NGSPICE tells us phase current is 1.999973 Amperes (1.999973×10^{-3} Volts divided by $1 \times 10^{-3} \Omega$). Theory tells us line current should be 3.464102 Amperes and NGSPICE tells us line current is 3.464055 Amperes. The disparity between NGSPICE's output and theoretical predictions is due to the inclusion of the 1 m Ω shunt resistors.

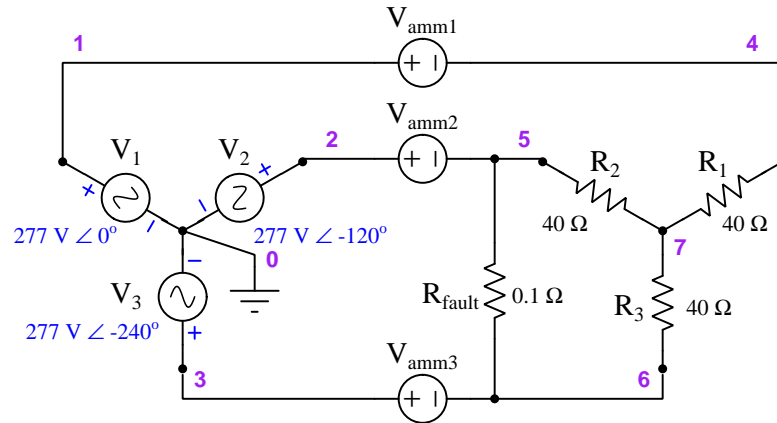6.2.9 Wye source with phase-to-phase fault

Here we will analyze line currents in a Wye-Wye system unbalanced by a phase-to-phase fault, represented by a very low resistance connected between two of the lines:

Circuit schematic diagram (with node numbers listed):



Note the use of DC voltage sources as line ammeters. Early versions of SPICE were only able to display current values through voltage sources, and so here three DC voltage sources (with voltage values defaulting to zero, as will be unspecified in the netlist) are used to connect the source to the load.


SPICE netlist:

```
* Wye source, Wye load
* 1-2-3 phase rotation, fault between nodes 5 and 6
v1 1 0 ac 277 0
v2 2 0 ac 277 -120
v3 3 0 ac 277 -240
r1 4 7 40
r2 5 7 40
r3 6 7 40
rfault 5 6 0.1
vamm1 1 4 0
vamm2 2 5 0
vamm3 3 6 0
.ac lin 1 60 60
.print ac im(vamm1) ip(vamm1)
.print ac im(vamm2) ip(vamm2)
.print ac im(vamm3) ip(vamm3)
.end
```

SPICE version 2G6 analysis (edited for brevity):

freq	im(vamm1)	ip(vamm1)
6.000E+01	6.925E+00	7.349E-15
freq	im(vamm2)	ip(vamm2)
6.000E+01	4.804E+03	-9.004E+01
freq	im(vamm3)	ip(vamm3)
6.000E+01	4.804E+03	9.004E+01

 Note how line 1's current is normal (6.925 Amperes $\angle 0^\circ$) while line 2 and line 3 are carrying very large amounts of current at strange phase angles (4804 Amperes at 90.04° and -90.04° , respectively). A phasor diagram of these lines currents would look something like this (with a greater disparity between long and short vector lengths than what is shown here):



This is why a phase-to-phase fault in a three-phase power system typically has the effect of making two of the line current phasors point in (nearly) opposite directions: the low fault resistance is effectively being powered by a single-phase voltage, and its large magnitude dominates line current which makes those two line current phasors seem as though they resemble that of a single-phase load rather than a three-phase load.


6.3 Three-phase AC transformer circuits

In these circuits, a three-phase source directly connects to a three-phase load with a bank of multiple transformers coupling power in between source and load.

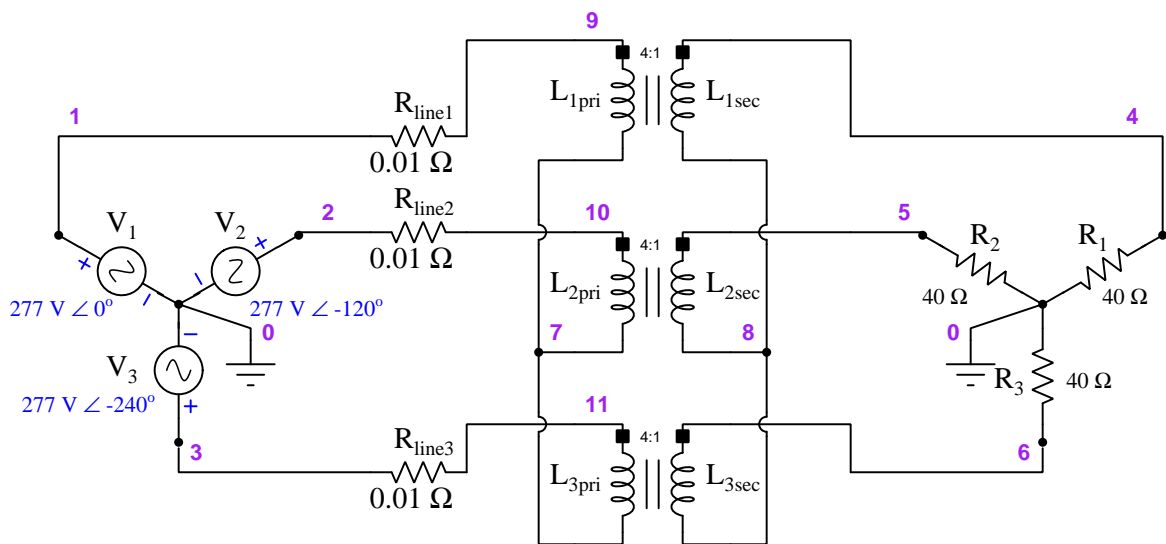6.3.1 Wye primary, Wye secondary

Here we will analyze load voltages for a transformer bank connected in a Wye-Wye configuration:

Circuit schematic diagram (with node numbers listed):



Note that transformers are modeled in SPICE as pairs of inductors with a coupling coefficient (k). Inductance values determine the ratio, with inductance ratio being the square of turns ratio (e.g. a 2:1 turns ratio requires a 4:1 ratio between primary and secondary inductance; a 4:1 turns ratio requires a 16:1 inductance ratio).

Note also how line resistances are necessary to insert into the circuit for the sake of avoiding a voltage source / inductor loop which will cause SPICE to abort with errors.

SPICE netlist:

```
* Wye-Wye transformer bank
* 4:1 turns ratio specified by 8:0.5 inductance ratio (16:1)
v1 1 0 ac 277 0
v2 2 0 ac 277 -120
v3 3 0 ac 277 -240
l1pri 9 7 8
l2pri 10 7 8
l3pri 11 7 8
l1sec 4 8 0.5
l2sec 5 8 0.5
l3sec 6 8 0.5
k1 l1pri l1sec 0.999
k2 l2pri l2sec 0.999
k3 l3pri l3sec 0.999
r1 4 0 40
r2 5 0 40
r3 6 0 40
rline1 1 9 0.01
rline2 2 10 0.01
rline3 3 11 0.01
.ac lin 1 60 60
.print ac vm(4) vp(4)
.print ac vm(5) vp(5)
.print ac vm(6) vp(6)
.end
```

SPICE version 2G6 analysis (edited for brevity):

freq	vm(4)	vp(4)
6.000E+01	6.918E+01	-5.395E-01
freq	vm(5)	vp(5)
6.000E+01	6.918E+01	-1.205E+02
freq	vm(6)	vp(6)
6.000E+01	6.918E+01	1.195E+02

In an ideal system, the 277 Volt phase source voltage gets stepped down by a precisely 4:1 ratio to deliver 69.25 Volts to each phase resistor at the load, with source phase angles perfectly preserved. The imperfect coupling between primary and secondary windings of each transformer and the finite inductance of the primary and secondary windings, however, conspire to skew the secondary voltage slightly down (to 69.18 Volts each), and to add a slight negative phase shift (-0.5395°) to all secondary voltages.

The less inductance possessed by the primary and secondary transformer windings, the closer the secondary phase angles approach ideal. The closer the coupling (k) values approach unity, the closer the secondary voltage values approach ideal. Here is a re-analysis of the circuit using 2 and 0.125 Henry inductance values instead of 8 and 0.5 Henry values, and transformer coupling factors of 0.9999 instead of 0.999:

SPICE version 2G6 analysis (edited for brevity):

freq	vm(4)	vp(4)
6.000E+01	6.924E+01	-1.274E-02
freq	vm(5)	vp(5)
6.000E+01	6.924E+01	-1.200E+02
freq	vm(6)	vp(6)
6.000E+01	6.924E+01	1.200E+02

6.3.2 Wye primary, Delta secondary

INCOMPLETE!

6.3.3 Delta primary, Wye secondary

INCOMPLETE!

6.3.4 Delta primary, Delta secondary

INCOMPLETE!

Appendix A

Problem-Solving Strategies

The ability to solve complex problems is arguably one of the most valuable skills one can possess, and this skill is particularly important in any science-based discipline.

- Study principles, not procedures. Don't be satisfied with merely knowing how to compute solutions – learn *why* those solutions work.
- Identify what it is you need to solve, identify all relevant data, identify all units of measurement, identify any general principles or formulae linking the given information to the solution, and then identify any “missing pieces” to a solution. Annotate all diagrams with this data.
- Sketch a diagram to help visualize the problem. When building a real system, always devise a plan for that system and analyze its function *before* constructing it.
- Follow the units of measurement and meaning of every calculation. If you are ever performing mathematical calculations as part of a problem-solving procedure, and you find yourself unable to apply each and every intermediate result to some aspect of the problem, it means you don't understand what you are doing. Properly done, every mathematical result should have practical meaning for the problem, and not just be an abstract number. You should be able to identify the proper units of measurement for each and every calculated result, and show where that result fits into the problem.
- Perform “thought experiments” to explore the effects of different conditions for theoretical problems. When troubleshooting real systems, perform *diagnostic tests* rather than visually inspecting for faults, the best diagnostic test being the one giving you the most information about the nature and/or location of the fault with the fewest steps.
- Simplify the problem until the solution becomes obvious, and then use that obvious case as a model to follow in solving the more complex version of the problem.
- Check for exceptions to see if your solution is incorrect or incomplete. A good solution will work for *all* known conditions and criteria. A good example of this is the process of testing scientific hypotheses: the task of a scientist is not to find support for a new idea, but rather to *challenge* that new idea to see if it holds up under a battery of tests. The philosophical

principle of *reductio ad absurdum* (i.e. disproving a general idea by finding a specific case where it fails) is useful here.

- Work “backward” from a hypothetical solution to a new set of given conditions.
- Add quantities to problems that are qualitative in nature, because sometimes a little math helps illuminate the scenario.
- Sketch graphs illustrating how variables relate to each other. These may be quantitative (i.e. with realistic number values) or qualitative (i.e. simply showing increases and decreases).
- Treat quantitative problems as qualitative in order to discern the relative magnitudes and/or directions of change of the relevant variables. For example, try determining what happens if a certain variable were to increase or decrease before attempting to precisely calculate quantities: how will each of the dependent variables respond, by increasing, decreasing, or remaining the same as before?
- Consider limiting cases. This works especially well for qualitative problems where you need to determine which direction a variable will change. Take the given condition and magnify that condition to an extreme degree as a way of simplifying the direction of the system’s response.
- Check your work. This means regularly testing your conclusions to see if they make sense. This does *not* mean repeating the same steps originally used to obtain the conclusion(s), but rather to use some other means to check validity. Simply repeating procedures often leads to *repeating the same errors* if any were made, which is why alternative paths are better.

Appendix B

Instructional philosophy

“The unexamined circuit is not worth energizing” – Socrates (if he had taught electricity)

These learning modules, although useful for self-study, were designed to be used in a formal learning environment where a subject-matter expert challenges students to digest the content and exercise their critical thinking abilities in the answering of questions and in the construction and testing of working circuits.

The following principles inform the instructional and assessment philosophies embodied in these learning modules:

- The first goal of education is to enhance clear and independent thought, in order that every student reach their fullest potential in a highly complex and inter-dependent world. Robust reasoning is *always* more important than particulars of any subject matter, because its application is universal.
- Literacy is fundamental to independent learning and thought because text continues to be the most efficient way to communicate complex ideas over space and time. Those who cannot read with ease are limited in their ability to acquire knowledge and perspective.
- Articulate communication is fundamental to work that is complex and interdisciplinary.
- Faulty assumptions and poor reasoning are best corrected through challenge, not presentation. The rhetorical technique of *reductio ad absurdum* (disproving an assertion by exposing an absurdity) works well to discipline student’s minds, not only to correct the problem at hand but also to learn how to detect and correct future errors.
- Important principles should be repeatedly explored and widely applied throughout a course of study, not only to reinforce their importance and help ensure their mastery, but also to showcase the interconnectedness and utility of knowledge.

These learning modules were expressly designed to be used in an “inverted” teaching environment¹ where students first read the introductory and tutorial chapters on their own, then individually attempt to answer the questions and construct working circuits according to the experiment and project guidelines. The instructor never lectures, but instead meets regularly with each individual student to review their progress, answer questions, identify misconceptions, and challenge the student to new depths of understanding through further questioning. Regular meetings between instructor and student should resemble a Socratic² dialogue, where questions serve as scalpels to dissect topics and expose assumptions. The student passes each module only after consistently demonstrating their ability to logically analyze and correctly apply all major concepts in each question or project/experiment. The instructor must be vigilant in probing each student’s understanding to ensure they are truly *reasoning* and not just *memorizing*. This is why “Challenge” points appear throughout, as prompts for students to think deeper about topics and as starting points for instructor queries. Sometimes these challenge points require additional knowledge that hasn’t been covered in the series to answer in full. This is okay, as the major purpose of the Challenges is to stimulate analysis and synthesis on the part of each student.

The instructor must possess enough mastery of the subject matter and awareness of students’ reasoning to generate their own follow-up questions to practically any student response. Even completely correct answers given by the student should be challenged by the instructor for the purpose of having students practice articulating their thoughts and defending their reasoning. Conceptual errors committed by the student should be exposed and corrected not by direct instruction, but rather by reducing the errors to an absurdity³ through well-chosen questions and thought experiments posed by the instructor. Becoming proficient at this style of instruction requires time and dedication, but the positive effects on critical thinking for both student and instructor are spectacular.

An inspection of these learning modules reveals certain unique characteristics. One of these is a bias toward thorough explanations in the tutorial chapters. Without a live instructor to explain concepts and applications to students, the text itself must fulfill this role. This philosophy results in lengthier explanations than what you might typically find in a textbook, each step of the reasoning process fully explained, including footnotes addressing common questions and concerns students raise while learning these concepts. Each tutorial seeks to not only explain each major concept in sufficient detail, but also to explain the logic of each concept and how each may be developed

¹In a traditional teaching environment, students first encounter new information via *lecture* from an expert, and then independently apply that information via *homework*. In an “inverted” course of study, students first encounter new information via *homework*, and then independently apply that information under the scrutiny of an expert. The expert’s role in lecture is to simply *explain*, but the expert’s role in an inverted session is to *challenge, critique*, and if necessary *explain* where gaps in understanding still exist.

²Socrates is a figure in ancient Greek philosophy famous for his unflinching style of questioning. Although he authored no texts, he appears as a character in Plato’s many writings. The essence of Socratic philosophy is to leave no question unexamined and no point of view unchallenged. While purists may argue a topic such as electric circuits is too narrow for a true Socratic-style dialogue, I would argue that the essential thought processes involved with scientific reasoning on *any* topic are not far removed from the Socratic ideal, and that students of electricity and electronics would do very well to challenge assumptions, pose thought experiments, identify fallacies, and otherwise employ the arsenal of critical thinking skills modeled by Socrates.

³This rhetorical technique is known by the Latin phrase *reductio ad absurdum*. The concept is to expose errors by counter-example, since only one solid counter-example is necessary to disprove a universal claim. As an example of this, consider the common misconception among beginning students of electricity that voltage cannot exist without current. One way to apply *reductio ad absurdum* to this statement is to ask how much current passes through a fully-charged battery connected to nothing (i.e. a clear example of voltage existing without current).

from “first principles”. Again, this reflects the goal of developing clear and independent thought in students’ minds, by showing how clear and logical thought was used to forge each concept. Students benefit from witnessing a model of clear thinking in action, and these tutorials strive to be just that.

Another characteristic of these learning modules is a lack of step-by-step instructions in the Project and Experiment chapters. Unlike many modern workbooks and laboratory guides where step-by-step instructions are prescribed for each experiment, these modules take the approach that students must learn to closely read the tutorials and apply their own reasoning to identify the appropriate experimental steps. Sometimes these steps are plainly declared in the text, just not as a set of enumerated points. At other times certain steps are implied, an example being assumed competence in test equipment use where the student should not need to be told *again* how to use their multimeter because that was thoroughly explained in previous lessons. In some circumstances no steps are given at all, leaving the entire procedure up to the student.

This lack of prescription is not a flaw, but rather a feature. Close reading and clear thinking are foundational principles of this learning series, and in keeping with this philosophy all activities are designed to *require* those behaviors. Some students may find the lack of prescription frustrating, because it demands more from them than what their previous educational experiences required. This frustration should be interpreted as an unfamiliarity with autonomous thinking, a problem which must be corrected if the student is ever to become a self-directed learner and effective problem-solver. Ultimately, the need for students to read closely and think clearly is more important both in the near-term and far-term than any specific facet of the subject matter at hand. If a student takes longer than expected to complete a module because they are forced to outline, digest, and reason on their own, so be it. The future gains enjoyed by developing this mental discipline will be well worth the additional effort and delay.

Another feature of these learning modules is that they do not treat topics in isolation. Rather, important concepts are introduced early in the series, and appear repeatedly as stepping-stones toward other concepts in subsequent modules. This helps to avoid the “compartmentalization” of knowledge, demonstrating the inter-connectedness of concepts and simultaneously reinforcing them. Each module is fairly complete in itself, reserving the beginning of its tutorial to a review of foundational concepts.

This methodology of assigning text-based modules to students for digestion and then using Socratic dialogue to assess progress and hone students’ thinking was developed over a period of several years by the author with his Electronics and Instrumentation students at the two-year college level. While decidedly unconventional and sometimes even unsettling for students accustomed to a more passive lecture environment, this instructional philosophy has proven its ability to convey conceptual mastery, foster careful analysis, and enhance employability so much better than lecture that the author refuses to ever teach by lecture again.

Problems which often go undiagnosed in a lecture environment are laid bare in this “inverted” format where students must articulate and logically defend their reasoning. This, too, may be unsettling for students accustomed to lecture sessions where the instructor cannot tell for sure who comprehends and who does not, and this vulnerability necessitates sensitivity on the part of the “inverted” session instructor in order that students never feel discouraged by having their errors exposed. *Everyone* makes mistakes from time to time, and learning is a lifelong process! Part of the instructor’s job is to build a culture of learning among the students where errors are not seen as shameful, but rather as opportunities for progress.

To this end, instructors managing courses based on these modules should adhere to the following principles:

- Student questions are always welcome and demand thorough, honest answers. The only type of question an instructor should refuse to answer is one the student should be able to easily answer on their own. Remember, *the fundamental goal of education is for each student to learn to think clearly and independently*. This requires hard work on the part of the student, which no instructor should ever circumvent. Anything done to bypass the student's responsibility to do that hard work ultimately limits that student's potential and thereby does real harm.
- It is not only permissible, but encouraged, to answer a student's question by asking questions in return, these follow-up questions designed to guide the student to reach a correct answer through their own reasoning.
- All student answers demand to be challenged by the instructor and/or by other students. This includes both correct and incorrect answers – the goal is to practice the articulation and defense of one's own reasoning.
- No reading assignment is deemed complete unless and until the student demonstrates their ability to accurately summarize the major points in their own terms. Recitation of the original text is unacceptable. This is why every module contains an "Outline and reflections" question as well as a "Foundational concepts" question in the Conceptual reasoning section, to prompt reflective reading.
- No assigned question is deemed answered unless and until the student demonstrates their ability to consistently and correctly apply the concepts to *variations* of that question. This is why module questions typically contain multiple "Challenges" suggesting different applications of the concept(s) as well as variations on the same theme(s). Instructors are encouraged to devise as many of their own "Challenges" as they are able, in order to have a multitude of ways ready to probe students' understanding.
- No assigned experiment or project is deemed complete unless and until the student demonstrates the task in action. If this cannot be done "live" before the instructor, video-recordings showing the demonstration are acceptable. All relevant safety precautions must be followed, all test equipment must be used correctly, and the student must be able to properly explain all results. The student must also successfully answer all Challenges presented by the instructor for that experiment or project.

Students learning from these modules would do well to abide by the following principles:

- No text should be considered fully and adequately read unless and until you can express every idea *in your own words, using your own examples*.
- You should always articulate your thoughts as you read the text, noting points of agreement, confusion, and epiphanies. Feel free to print the text on paper and then write your notes in the margins. Alternatively, keep a journal for your own reflections as you read. This is truly a helpful tool when digesting complicated concepts.
- Never take the easy path of highlighting or underlining important text. Instead, *summarize* and/or *comment* on the text using your own words. This actively engages your mind, allowing you to more clearly perceive points of confusion or misunderstanding on your own.
- A very helpful strategy when learning new concepts is to place yourself in the role of a teacher, if only as a mental exercise. Either explain what you have recently learned to someone else, or at least *imagine* yourself explaining what you have learned to someone else. The simple act of having to articulate new knowledge and skill forces you to take on a different perspective, and will help reveal weaknesses in your understanding.
- Perform each and every mathematical calculation and thought experiment shown in the text on your own, referring back to the text to see that your results agree. This may seem trivial and unnecessary, but it is critically important to ensuring you actually understand what is presented, especially when the concepts at hand are complicated and easy to misunderstand. Apply this same strategy to become proficient in the use of *circuit simulation software*, checking to see if your simulated results agree with the results shown in the text.
- Above all, recognize that learning is hard work, and that a certain level of frustration is unavoidable. There are times when you will struggle to grasp some of these concepts, and that struggle is a natural thing. Take heart that it will yield with persistent and varied⁴ effort, and never give up!

Students interested in using these modules for self-study will also find them beneficial, although the onus of responsibility for thoroughly reading and answering questions will of course lie with that individual alone. If a qualified instructor is not available to challenge students, a workable alternative is for students to form study groups where they challenge⁵ one another.

To high standards of education,

Tony R. Kuphaldt

⁴As the old saying goes, “Insanity is trying the same thing over and over again, expecting different results.” If you find yourself stumped by something in the text, you should attempt a different approach. Alter the thought experiment, change the mathematical parameters, do whatever you can to see the problem in a slightly different light, and then the solution will often present itself more readily.

⁵Avoid the temptation to simply share answers with study partners, as this is really counter-productive to learning. Always bear in mind that the answer to any question is far less important in the long run than the method(s) used to obtain that answer. The goal of education is to empower one’s life through the improvement of clear and independent thought, literacy, expression, and various practical skills.

Appendix C

Tools used

I am indebted to the developers of many open-source software applications in the creation of these learning modules. The following is a list of these applications with some commentary on each.

You will notice a theme common to many of these applications: a bias toward *code*. Although I am by no means an expert programmer in any computer language, I understand and appreciate the flexibility offered by code-based applications where the user (you) enters commands into a plain ASCII text file, which the software then reads and processes to create the final output. Code-based computer applications are by their very nature *extensible*, while WYSIWYG (What You See Is What You Get) applications are generally limited to whatever user interface the developer makes for you.

The GNU/Linux computer operating system

There is so much to be said about Linus Torvalds' `Linux` and Richard Stallman's `GNU` project. First, to credit just these two individuals is to fail to do justice to the *mob* of passionate volunteers who contributed to make this amazing software a reality. I first learned of `Linux` back in 1996, and have been using this operating system on my personal computers almost exclusively since then. It is *free*, it is completely *configurable*, and it permits the continued use of highly efficient `Unix` applications and scripting languages (e.g. shell scripts, Makefiles, `sed`, `awk`) developed over many decades. `Linux` not only provided me with a powerful computing platform, but its open design served to inspire my life's work of creating open-source educational resources.

Bram Moolenaar's Vim text editor

Writing code for any code-based computer application requires a *text editor*, which may be thought of as a word processor strictly limited to outputting plain-ASCII text files. Many good text editors exist, and one's choice of text editor seems to be a deeply personal matter within the programming world. I prefer `Vim` because it operates very similarly to `vi` which is ubiquitous on `Unix/Linux` operating systems, and because it may be entirely operated via keyboard (i.e. no mouse required) which makes it fast to use.

Donald Knuth's \TeX typesetting system

Developed in the late 1970's and early 1980's by computer scientist extraordinaire Donald Knuth to typeset his multi-volume magnum opus *The Art of Computer Programming*, this software allows the production of formatted text for screen-viewing or paper printing, all by writing plain-text code to describe how the formatted text is supposed to appear. \TeX is not just a markup language for documents, but it is also a Turing-complete programming language in and of itself, allowing useful algorithms to be created to control the production of documents. Simply put, *\TeX is a programmer's approach to word processing*. Since \TeX is controlled by code written in a plain-text file, this means anyone may read that plain-text file to see exactly how the document was created. This openness afforded by the code-based nature of \TeX makes it relatively easy to learn how other people have created their own \TeX documents. By contrast, examining a beautiful document created in a conventional WYSIWYG word processor such as Microsoft **Word** suggests nothing to the reader about *how* that document was created, or what the user might do to create something similar. As Mr. Knuth himself once quipped, conventional word processing applications should be called WYSIAYG (What You See Is *All* You Get).

Leslie Lamport's \LaTeX extensions to \TeX

Like all true programming languages, \TeX is inherently extensible. So, years after the release of \TeX to the public, Leslie Lamport decided to create a massive extension allowing easier compilation of book-length documents. The result was \LaTeX , which is the markup language used to create all ModEL module documents. You could say that \TeX is to \LaTeX as **C** is to **C++**. This means it is permissible to use any and all \TeX commands within \LaTeX source code, and it all still works. Some of the features offered by \LaTeX that would be challenging to implement in \TeX include automatic index and table-of-content creation.

Tim Edwards' **Xcircuit** drafting program

This wonderful program is what I use to create all the schematic diagrams and illustrations (but not photographic images or mathematical plots) throughout the ModEL project. It natively outputs PostScript format which is a true vector graphic format (this is why the images do not pixellate when you zoom in for a closer view), and it is so simple to use that I have never had to read the manual! Object libraries are easy to create for **Xcircuit**, being plain-text files using PostScript programming conventions. Over the years I have collected a large set of object libraries useful for drawing electrical and electronic schematics, pictorial diagrams, and other technical illustrations.

Gimp graphic image manipulation program

Essentially an open-source clone of Adobe's **PhotoShop**, I use **Gimp** to resize, crop, and convert file formats for all of the photographic images appearing in the **MODEL** modules. Although **Gimp** does offer its own scripting language (called **Script-Fu**), I have never had occasion to use it. Thus, my utilization of **Gimp** to merely crop, resize, and convert graphic images is akin to using a sword to slice bread.

SPICE circuit simulation program

SPICE is to circuit analysis as **T_EX** is to document creation: it is a form of markup language designed to describe a certain object to be processed in plain-ASCII text. When the plain-text "source file" is compiled by the software, it outputs the final result. More modern circuit analysis tools certainly exist, but I prefer **SPICE** for the following reasons: it is *free*, it is *fast*, it is *reliable*, and it is a fantastic tool for *teaching* students of electricity and electronics how to write simple code. I happen to use rather old versions of **SPICE**, version 2g6 being my "go to" application when I only require text-based output. **NGSPICE** (version 26), which is based on Berkeley **SPICE** version 3f5, is used when I require graphical output for such things as time-domain waveforms and Bode plots. In all **SPICE** example netlists I strive to use coding conventions compatible with all **SPICE** versions.

Andrew D. Hwang's ePiX mathematical visualization programming library

This amazing project is a **C++** library you may link to any **C/C++** code for the purpose of generating PostScript graphic images of mathematical functions. As a completely free and open-source project, it does all the plotting I would otherwise use a Computer Algebra System (CAS) such as **Mathematica** or **Maple** to do. It should be said that **ePiX** is *not* a Computer Algebra System like **Mathematica** or **Maple**, but merely a mathematical *visualization* tool. In other words, it won't determine integrals for you (you'll have to implement that in your own **C/C++** code!), but it can graph the results, and it does so beautifully. What I really admire about **ePiX** is that it is a **C++** programming library, which means it builds on the existing power and toolset available with that programming language. Mr. Hwang could have probably developed his own stand-alone application for mathematical plotting, but by creating a **C++** library to do the same thing he accomplished something much greater.

gnuplot mathematical visualization software

Another open-source tool for mathematical visualization is `gnuplot`. Interestingly, this tool is *not* part of Richard Stallman’s GNU project, its name being a coincidence. For this reason the authors prefer “gnu” *not* be capitalized at all to avoid confusion. This is a much “lighter-weight” alternative to a spreadsheet for plotting tabular data, and the fact that it easily outputs directly to an X11 console or a file in a number of different graphical formats (including PostScript) is very helpful. I typically set my `gnuplot` output format to default (X11 on my Linux PC) for quick viewing while I’m developing a visualization, then switch to PostScript file export once the visual is ready to include in the document(s) I’m writing. As with my use of `Gimp` to do rudimentary image editing, my use of `gnuplot` only scratches the surface of its capabilities, but the important points are that it’s *free* and that it *works well*.

Python programming language

Both Python and C++ find extensive use in these modules as instructional aids and exercises, but I’m listing Python here as a *tool* for myself because I use it almost daily as a *calculator*. If you open a Python interpreter console and type `from math import *` you can type mathematical expressions and have it return results just as you would on a hand calculator. Complex-number (i.e. *phasor*) arithmetic is similarly supported if you include the complex-math library (`from cmath import *`). Examples of this are shown in the Programming References chapter (if included) in each module. Of course, being a fully-featured programming language, Python also supports conditionals, loops, and other structures useful for calculation of quantities. Also, running in a console environment where all entries and returned values show as text in a chronologically-ordered list makes it easy to copy-and-paste those calculations to document exactly how they were performed.

Appendix D

Creative Commons License

Creative Commons Attribution 4.0 International Public License

By exercising the Licensed Rights (defined below), You accept and agree to be bound by the terms and conditions of this Creative Commons Attribution 4.0 International Public License (“Public License”). To the extent this Public License may be interpreted as a contract, You are granted the Licensed Rights in consideration of Your acceptance of these terms and conditions, and the Licensor grants You such rights in consideration of benefits the Licensor receives from making the Licensed Material available under these terms and conditions.

Section 1 – Definitions.

a. **Adapted Material** means material subject to Copyright and Similar Rights that is derived from or based upon the Licensed Material and in which the Licensed Material is translated, altered, arranged, transformed, or otherwise modified in a manner requiring permission under the Copyright and Similar Rights held by the Licensor. For purposes of this Public License, where the Licensed Material is a musical work, performance, or sound recording, Adapted Material is always produced where the Licensed Material is synched in timed relation with a moving image.

b. **Adapter’s License** means the license You apply to Your Copyright and Similar Rights in Your contributions to Adapted Material in accordance with the terms and conditions of this Public License.

c. **Copyright and Similar Rights** means copyright and/or similar rights closely related to copyright including, without limitation, performance, broadcast, sound recording, and Sui Generis Database Rights, without regard to how the rights are labeled or categorized. For purposes of this Public License, the rights specified in Section 2(b)(1)-(2) are not Copyright and Similar Rights.

d. **Effective Technological Measures** means those measures that, in the absence of proper authority, may not be circumvented under laws fulfilling obligations under Article 11 of the WIPO Copyright Treaty adopted on December 20, 1996, and/or similar international agreements.

e. **Exceptions and Limitations** means fair use, fair dealing, and/or any other exception or

limitation to Copyright and Similar Rights that applies to Your use of the Licensed Material.

f. **Licensed Material** means the artistic or literary work, database, or other material to which the Licensor applied this Public License.

g. **Licensed Rights** means the rights granted to You subject to the terms and conditions of this Public License, which are limited to all Copyright and Similar Rights that apply to Your use of the Licensed Material and that the Licensor has authority to license.

h. **Licensor** means the individual(s) or entity(ies) granting rights under this Public License.

i. **Share** means to provide material to the public by any means or process that requires permission under the Licensed Rights, such as reproduction, public display, public performance, distribution, dissemination, communication, or importation, and to make material available to the public including in ways that members of the public may access the material from a place and at a time individually chosen by them.

j. **Sui Generis Database Rights** means rights other than copyright resulting from Directive 96/9/EC of the European Parliament and of the Council of 11 March 1996 on the legal protection of databases, as amended and/or succeeded, as well as other essentially equivalent rights anywhere in the world.

k. **You** means the individual or entity exercising the Licensed Rights under this Public License. **Your** has a corresponding meaning.

Section 2 – Scope.

a. License grant.

1. Subject to the terms and conditions of this Public License, the Licensor hereby grants You a worldwide, royalty-free, non-sublicensable, non-exclusive, irrevocable license to exercise the Licensed Rights in the Licensed Material to:

A. reproduce and Share the Licensed Material, in whole or in part; and

B. produce, reproduce, and Share Adapted Material.

2. Exceptions and Limitations. For the avoidance of doubt, where Exceptions and Limitations apply to Your use, this Public License does not apply, and You do not need to comply with its terms and conditions.

3. Term. The term of this Public License is specified in Section 6(a).

4. Media and formats; technical modifications allowed. The Licensor authorizes You to exercise the Licensed Rights in all media and formats whether now known or hereafter created, and to make technical modifications necessary to do so. The Licensor waives and/or agrees not to assert any right or authority to forbid You from making technical modifications necessary to exercise the Licensed Rights, including technical modifications necessary to circumvent Effective Technological Measures.

For purposes of this Public License, simply making modifications authorized by this Section 2(a)(4) never produces Adapted Material.

5. Downstream recipients.

A. Offer from the Licensor – Licensed Material. Every recipient of the Licensed Material automatically receives an offer from the Licensor to exercise the Licensed Rights under the terms and conditions of this Public License.

B. No downstream restrictions. You may not offer or impose any additional or different terms or conditions on, or apply any Effective Technological Measures to, the Licensed Material if doing so restricts exercise of the Licensed Rights by any recipient of the Licensed Material.

6. No endorsement. Nothing in this Public License constitutes or may be construed as permission to assert or imply that You are, or that Your use of the Licensed Material is, connected with, or sponsored, endorsed, or granted official status by, the Licensor or others designated to receive attribution as provided in Section 3(a)(1)(A)(i).

b. Other rights.

1. Moral rights, such as the right of integrity, are not licensed under this Public License, nor are publicity, privacy, and/or other similar personality rights; however, to the extent possible, the Licensor waives and/or agrees not to assert any such rights held by the Licensor to the limited extent necessary to allow You to exercise the Licensed Rights, but not otherwise.

2. Patent and trademark rights are not licensed under this Public License.

3. To the extent possible, the Licensor waives any right to collect royalties from You for the exercise of the Licensed Rights, whether directly or through a collecting society under any voluntary or waivable statutory or compulsory licensing scheme. In all other cases the Licensor expressly reserves any right to collect such royalties.

Section 3 – License Conditions.

Your exercise of the Licensed Rights is expressly made subject to the following conditions.

a. Attribution.

1. If You Share the Licensed Material (including in modified form), You must:

A. retain the following if it is supplied by the Licensor with the Licensed Material:

i. identification of the creator(s) of the Licensed Material and any others designated to receive attribution, in any reasonable manner requested by the Licensor (including by pseudonym if designated);

ii. a copyright notice;

- iii. a notice that refers to this Public License;
- iv. a notice that refers to the disclaimer of warranties;
- v. a URI or hyperlink to the Licensed Material to the extent reasonably practicable;

B. indicate if You modified the Licensed Material and retain an indication of any previous modifications; and

C. indicate the Licensed Material is licensed under this Public License, and include the text of, or the URI or hyperlink to, this Public License.

2. You may satisfy the conditions in Section 3(a)(1) in any reasonable manner based on the medium, means, and context in which You Share the Licensed Material. For example, it may be reasonable to satisfy the conditions by providing a URI or hyperlink to a resource that includes the required information.

3. If requested by the Licensor, You must remove any of the information required by Section 3(a)(1)(A) to the extent reasonably practicable.

4. If You Share Adapted Material You produce, the Adapter's License You apply must not prevent recipients of the Adapted Material from complying with this Public License.

Section 4 – Sui Generis Database Rights.

Where the Licensed Rights include Sui Generis Database Rights that apply to Your use of the Licensed Material:

- a. for the avoidance of doubt, Section 2(a)(1) grants You the right to extract, reuse, reproduce, and Share all or a substantial portion of the contents of the database;
- b. if You include all or a substantial portion of the database contents in a database in which You have Sui Generis Database Rights, then the database in which You have Sui Generis Database Rights (but not its individual contents) is Adapted Material; and
- c. You must comply with the conditions in Section 3(a) if You Share all or a substantial portion of the contents of the database.

For the avoidance of doubt, this Section 4 supplements and does not replace Your obligations under this Public License where the Licensed Rights include other Copyright and Similar Rights.

Section 5 – Disclaimer of Warranties and Limitation of Liability.

a. Unless otherwise separately undertaken by the Licensor, to the extent possible, the Licensor offers the Licensed Material as-is and as-available, and makes no representations or warranties of any kind concerning the Licensed Material, whether express, implied, statutory, or other. This includes, without limitation, warranties of title, merchantability, fitness for a particular purpose, non-infringement, absence of latent or other defects, accuracy, or the presence or absence of errors,

whether or not known or discoverable. Where disclaimers of warranties are not allowed in full or in part, this disclaimer may not apply to You.

b. To the extent possible, in no event will the Licensor be liable to You on any legal theory (including, without limitation, negligence) or otherwise for any direct, special, indirect, incidental, consequential, punitive, exemplary, or other losses, costs, expenses, or damages arising out of this Public License or use of the Licensed Material, even if the Licensor has been advised of the possibility of such losses, costs, expenses, or damages. Where a limitation of liability is not allowed in full or in part, this limitation may not apply to You.

c. The disclaimer of warranties and limitation of liability provided above shall be interpreted in a manner that, to the extent possible, most closely approximates an absolute disclaimer and waiver of all liability.

Section 6 – Term and Termination.

a. This Public License applies for the term of the Copyright and Similar Rights licensed here. However, if You fail to comply with this Public License, then Your rights under this Public License terminate automatically.

b. Where Your right to use the Licensed Material has terminated under Section 6(a), it reinstates:

1. automatically as of the date the violation is cured, provided it is cured within 30 days of Your discovery of the violation; or

2. upon express reinstatement by the Licensor.

For the avoidance of doubt, this Section 6(b) does not affect any right the Licensor may have to seek remedies for Your violations of this Public License.

c. For the avoidance of doubt, the Licensor may also offer the Licensed Material under separate terms or conditions or stop distributing the Licensed Material at any time; however, doing so will not terminate this Public License.

d. Sections 1, 5, 6, 7, and 8 survive termination of this Public License.

Section 7 – Other Terms and Conditions.

a. The Licensor shall not be bound by any additional or different terms or conditions communicated by You unless expressly agreed.

b. Any arrangements, understandings, or agreements regarding the Licensed Material not stated herein are separate from and independent of the terms and conditions of this Public License.

Section 8 – Interpretation.

a. For the avoidance of doubt, this Public License does not, and shall not be interpreted to, reduce, limit, restrict, or impose conditions on any use of the Licensed Material that could lawfully

be made without permission under this Public License.

b. To the extent possible, if any provision of this Public License is deemed unenforceable, it shall be automatically reformed to the minimum extent necessary to make it enforceable. If the provision cannot be reformed, it shall be severed from this Public License without affecting the enforceability of the remaining terms and conditions.

c. No term or condition of this Public License will be waived and no failure to comply consented to unless expressly agreed to by the Licensor.

d. Nothing in this Public License constitutes or may be interpreted as a limitation upon, or waiver of, any privileges and immunities that apply to the Licensor or You, including from the legal processes of any jurisdiction or authority.

Creative Commons is not a party to its public licenses. Notwithstanding, Creative Commons may elect to apply one of its public licenses to material it publishes and in those instances will be considered the “Licensor.” Except for the limited purpose of indicating that material is shared under a Creative Commons public license or as otherwise permitted by the Creative Commons policies published at creativecommons.org/policies, Creative Commons does not authorize the use of the trademark “Creative Commons” or any other trademark or logo of Creative Commons without its prior written consent including, without limitation, in connection with any unauthorized modifications to any of its public licenses or any other arrangements, understandings, or agreements concerning use of licensed material. For the avoidance of doubt, this paragraph does not form part of the public licenses.

Creative Commons may be contacted at creativecommons.org.

Appendix E

References

Vladimirescu, Andrei, *The Spice Book*, John Wiley & Sons, New York, 1994.

Appendix F

Version history

This is a list showing all significant additions, corrections, and other edits made to this learning module. Each entry is referenced by calendar date in reverse chronological order (newest version first), which appears on the front cover of every learning module for easy reference. Any contributors to this open-source document are listed here as well.

6 September 2024 – re-named the “Introduction” chapter to be called “What is SPICE?”, so that later I may add an “Introduction” chapter more aligned with other modules’ Introduction chapters.

9 July 2021 – replaced some TeX-style italicizing markup with LaTeX-style.

3 September 2020 – added zero voltage values to all the “vamm” dummy voltage sources, as NGSPICE complains about voltage sources having no specified value, while SPICE 2G6 accepts this just fine.

6 May 2019 – typographical error corrections in some of the 3-phase SPICE netlists: four netlists were incorrectly named, and one of them had no resistance values given for shunt resistors.

30 April 2019 – added another three-phase circuit analysis example to the Gallery chapter.

20 April 2019 – added more three-phase circuit analysis examples to the Gallery chapter.

19 April 2019 – added more three-phase circuit analysis examples to the Gallery chapter.

7 April 2019 – added introductory section to the Gallery chapter discussing the use of SPICE as a tool for generating answers for practice problem sets.

2 April 2019 – added more three-phase examples to the Gallery chapter.

July 2017 – added references to *electrically common* and *electrically distinct* points when describing the function of node numbers in a SPICE netlist. Also, corrected a node-numbering error on one schematic diagram and improved the node numbering on other diagrams.

October 2016 – created changelog for future use.

September 2016 – document first published.

Index

- .end, [27](#), [55](#)
- Adding quantities to a qualitative problem, [154](#)
- Annotating diagrams, [153](#)
- Bode plot, [61](#)
- Buffer components, [25](#)
- Card, [27](#), [55](#)
- Checking for exceptions, [154](#)
- Checking your work, [154](#)
- Code, computer, [161](#)
- Comments, [27](#), [55](#)
- Components, buffer, [25](#)
- Dimensional analysis, [153](#)
- Edwards, Tim, [162](#)
- Electrically common points, [7](#), [55](#), [66](#), [82](#)
- Electrically distinct points, [7](#), [9](#), [14](#), [82](#)
- Frequency-domain plot, [61](#)
- Graph values to solve a problem, [154](#)
- Ground, [23](#), [27](#), [55](#)
- How to teach with these modules, [156](#)
- Hwang, Andrew D., [163](#)
- Identify given data, [153](#)
- Identify relevant principles, [153](#)
- Instructions for projects and experiments, [157](#)
- Intermediate results, [153](#)
- Inverted instruction, [156](#)
- Knuth, Donald, [162](#)
- Lamport, Leslie, [162](#)
- Limiting cases, [154](#)
- Lissajous figure, [62](#)
- Load, [23](#)
- Moolenaar, Bram, [161](#)
- Netlist, [27](#), [55](#)
- Node, [27](#), [55](#)
- Open, [24](#)
- Open-source, [161](#)
- Parametric plot, [62](#)
- Problem-solving: annotate diagrams, [153](#)
- Problem-solving: check for exceptions, [154](#)
- Problem-solving: checking work, [154](#)
- Problem-solving: dimensional analysis, [153](#)
- Problem-solving: graph values, [154](#)
- Problem-solving: identify given data, [153](#)
- Problem-solving: identify relevant principles, [153](#)
- Problem-solving: interpret intermediate results, [153](#)
- Problem-solving: limiting cases, [154](#)
- Problem-solving: qualitative to quantitative, [154](#)
- Problem-solving: quantitative to qualitative, [154](#)
- Problem-solving: reductio ad absurdum, [154](#)
- Problem-solving: simplify the system, [153](#)
- Problem-solving: thought experiment, [153](#)
- Problem-solving: track units of measurement, [153](#)
- Problem-solving: visually represent the system, [153](#)
- Problem-solving: work in reverse, [154](#)
- Qualitatively approaching a quantitative problem, [154](#)
- Reductio ad absurdum, [154–156](#)

Short, 24
Shunt resistor, 115, 123
Simplifying a system, 153
Socrates, 155
Socratic dialogue, 156
Source, 23
SPICE, 3
Stallman, Richard, 161

Thought experiment, 153
Time-domain plot, 62
Title, 27, 55
Torvalds, Linus, 161

Units of measurement, 153

Visualizing a system, 153

Work in reverse to solve a problem, 154
WYSIWYG, 3, 5, 161, 162