

Block I

Apollo Guidance Computer (AGC)

How to build one in your basement

Part 2: Control (CTL) Module

John Pultorak
December, 2004

Abstract

This report describes my successful project to build a working reproduction of the 1964 prototype for the Block I Apollo Guidance Computer. The AGC is the flight computer for the Apollo moon landings, and is the world's first integrated circuit computer.

I built it in my basement. It took me 4 years.

If you like, you can build one too. It will take you less time, and yours will be better than mine.

I documented my project in 9 separate .pdf files:

- Part 1 Overview: Introduces the project.
- Part 2 CTL Module: Design and construction of the control module.
- Part 3 PROC Module: Design and construction of the processing (CPU) module.
- Part 4 MEM Module: Design and construction of the memory module.
- Part 5 IO Module: Design and construction of the display/keyboard (DSKY) module.
- Part 6 Assembler: A cross-assembler for AGC software development.
- Part 7 C++ Simulator: A low-level simulator that runs assembled AGC code.
- Part 8 Flight Software: My translation of portions of the COLOSSUS 249 flight software.
- Part 9 Test & Checkout: A suite of test programs in AGC assembly language.

Overview

The Control Module (CTL) has 9 subsystems: CMI, MON, CLK, SCL, TPG, SEQ, CPM-A, CPM-B, CPM-C

CMI (Control Module external Interface)

The CMI interfaces the other control module subsystems (described below) to external AGC modules. 40-pin IDE connectors interface to the PROC, MEM, and IO modules. Inputs from those modules are buffered to 1 LSTTL load.

MON (AGC Monitor)

The monitor subsystem has the front-panel switches that control AGC operation, and also implements the power-up reset circuit.

CLK (Clock)

The AGC is controlled by a 2.048 MHz crystal clock. The clock is divided to produce a 2-phase, non-overlapping 1.024 MHz AGC system clock for nominal operation. For test purposes, a low-frequency RC clock can also be selected, or the clock can be single-stepped.

SCL (Scaler)

The 1.024 MHz AGC clock is divided by two to produce a 512 kHz signal called the MASTER FREQUENCY; this signal is further divided through a SCALER, first by five to produce a 102.4 kHz signal. This is then divided by two through 17 successive stages called F1 (51.2 kHz) through F17 (0.78125 Hz).


The F10 stage (100 Hz) is fed back into the AGC to increment the real-time clock and other priority counters in the PROC module. The F17 stage is used to intermittently run the AGC when it operates in the STANDBY mode.

TPG (Time Pulse Generator)

AGC instructions are implemented in groups of 12 steps, called timing pulses. The timing pulses, named TP1 through TP12, are produced by the Time Pulse Generator (TPG). Each set of 12 timing pulses is called an instruction subsequence. Simple instructions, such as TC, execute in a single subsequence of 12 pulses. More complex instructions require several subsequences.

SEQ (Sequence Generator)

 The sequence generator has the SQ register, which holds the next op-code, and the CTR




register--a counter used to count instruction subsequences during multiplication. The sequence generator also has the branch register (BR) which controls conditional processing during instruction execution, and the STAGE registers (STA and STB) which select the instruction subsequences for complex instructions that have more than one subsequence.

CPM-A (Control Pulse Matrix A)
 The CPM-A is the combinational logic matrix that implements most of the control logic. It is driven by inputs from the SQ register (which selects the instruction), the STB stage register (which selects the instruction subsequence), and the BR branch register (which selects conditional steps in a subsequence).


CPM-B (Control Pulse Matrix B)
 The CPM-B decodes read and write control signals for special memory location associated with input/output registers, central registers (A, Q, Z, and LP), and the editing registers used for rotation and shifting.

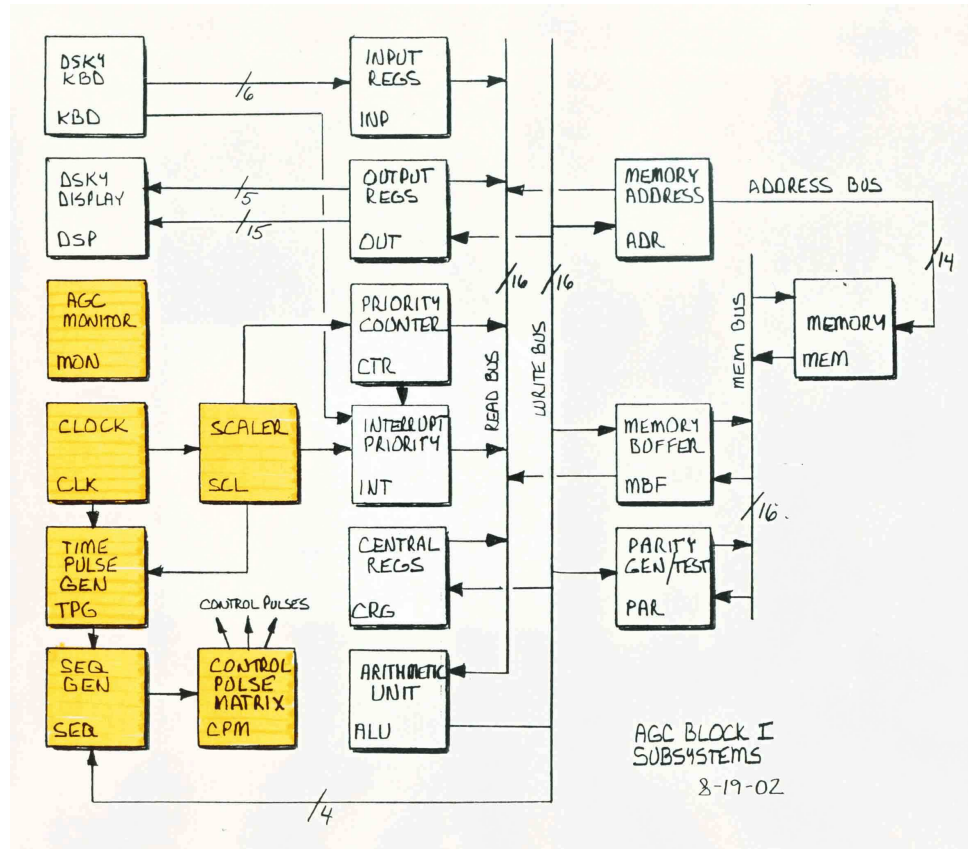CPM-C (Control Pulse Matrix C)
 The CPM-C decodes control signals primarily associated with interrupts, the memory cycle, and the selection of new instructions and instruction subsequences.



This is a functional diagram showing the interrelationships between the Time Pulse Generator (TPG), the Control Pulse Matrix (CPM-A, B, and C), and the registers that are in the Sequence Generator (SEQ).

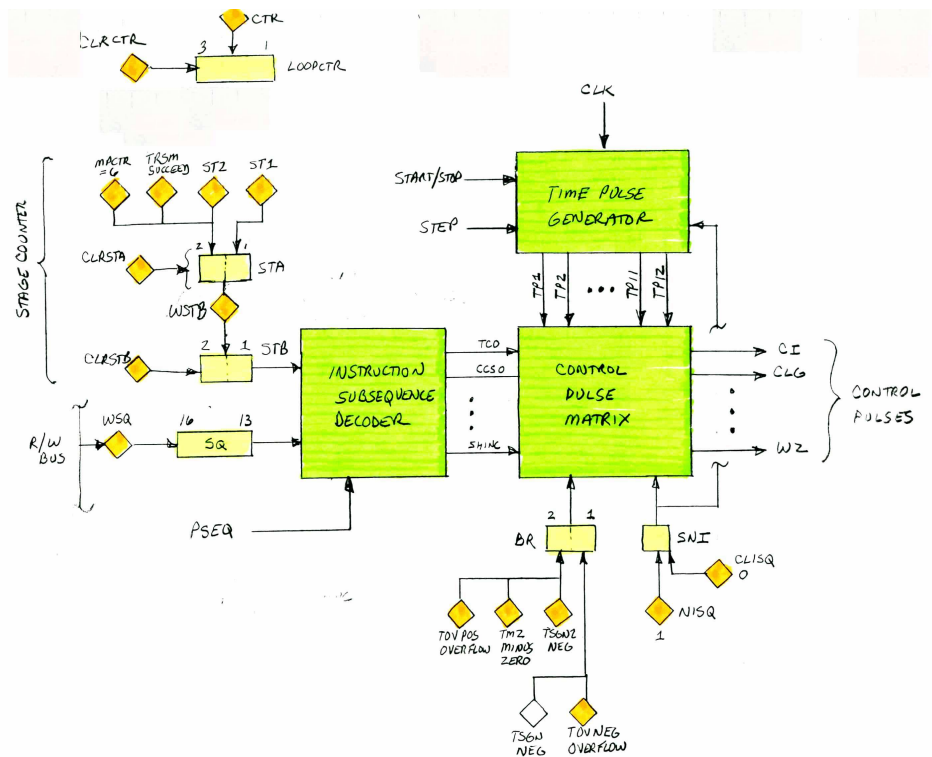The diagram is mine, but the style is borrowed from original AGC documentation: control signals are represented by diamonds. The arrows show the direction of data flow. When a control signal is asserted, data is allowed to flow through the diamond. For example, when WSA is asserted, the opcode is written from the Read/Write bus into the SQ register.




Registers (**LOOPCTR**, **STA**, **STB**, **SQ**, **BR**, and **SNI**) are represented by rectangles. The lower bit of the 2-bit **STA** register is set by **ST1**. The upper bit is set by any one of the 3 control signals flowing into it. The **STA** register is cleared by **CLRSTA**.

When **WSTB** is asserted, the **STA** register is copied to **STB**. **STB** and the **SQ** register select the instruction subsequence.


The instruction subsequence, time pulse generator, **BR** register, and **SNI** all feed into the **Control Pulse Matrix** to select the active control pulses.

The diagram was developed by analyzing the R-393 document. It was one of my first diagrams; a sort-of conceptual breakthrough that became my gateway for understanding the AGC control module.

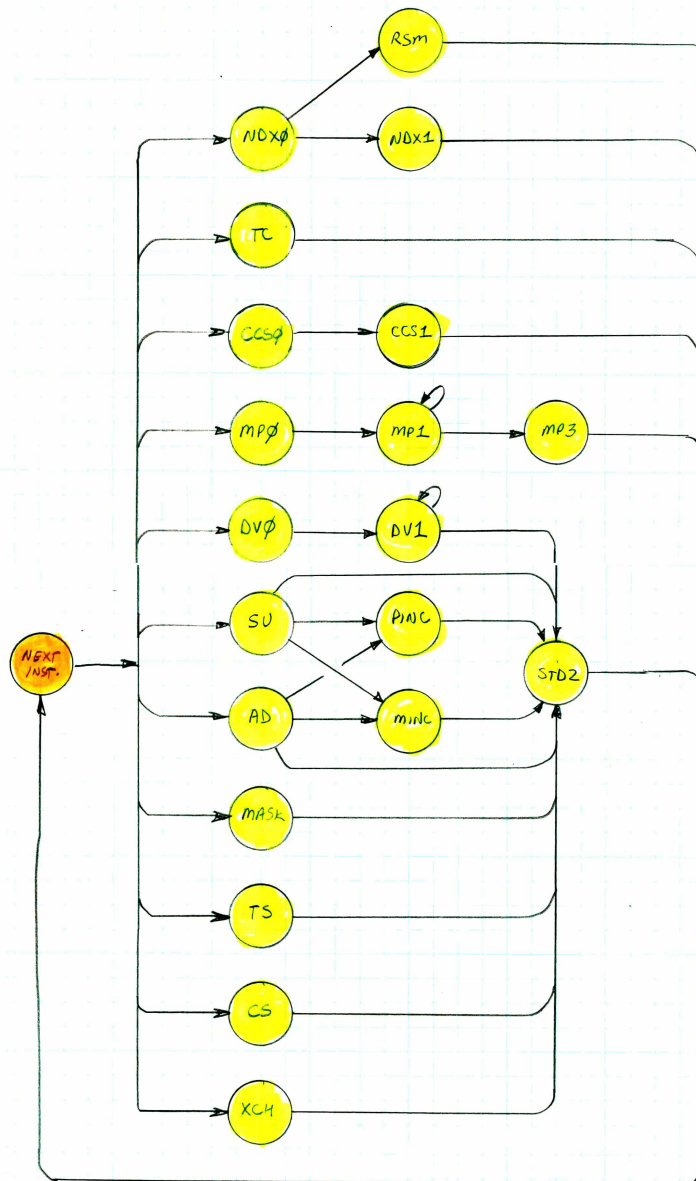The instruction subsequences executed by the AGC are shown in this diagram. Each yellow circle is a subsequence; a set of 12 steps, with each step generating 0-5 control pulses. Eleven steps (TP1-TP11) are in the yellow circle; the 12th step, which selects the next subsequence (TP12), is in the orange circle. This is discussed in more detail in the TPG, SEQ, and CPM-A subsystems.



 
(3-1)
INST IN \underline{L}
 $C(z) = L+1$



ST2 } also TRSM's succeed
ST1 } mpcnt = 0
} STAGE COUNTER
0 0 NORMAL } 0 START
0 1 INTERRUPT }
1 0
1 1
SUBSEQUENCE


The counter is incremented during the memory cycle and transferred to \underline{L} for output in T12. (2-9)

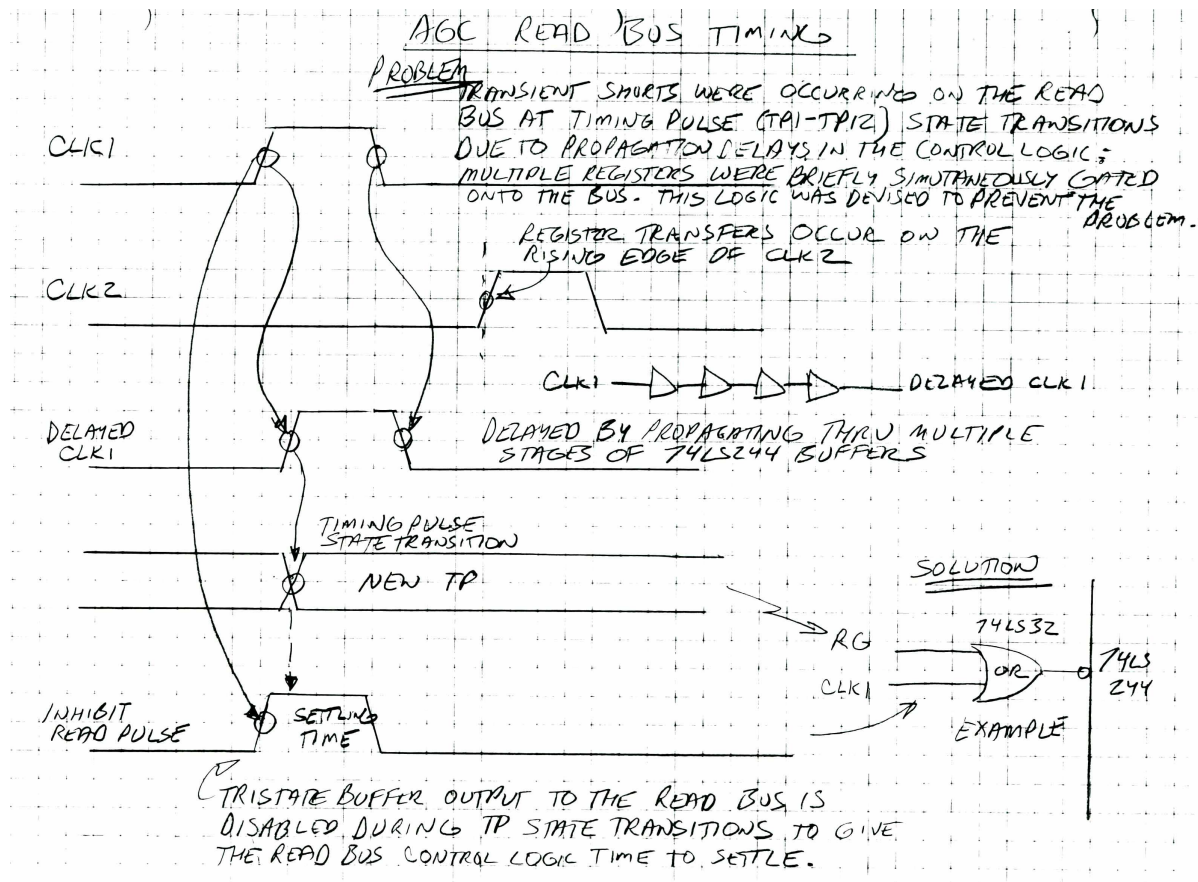A late addition to the CTL design fixed a problem with the read bus logic. Due to propagation delays (and some poor design on my part), the tri-state buffers from multiple registers were simultaneously enabled for brief periods causing some transients. I "kludged" in a design change that suppressed output to the read bus during CLK1, thereby giving the bus control logic time to settle.




CTL Internal Subsystem Interconnections

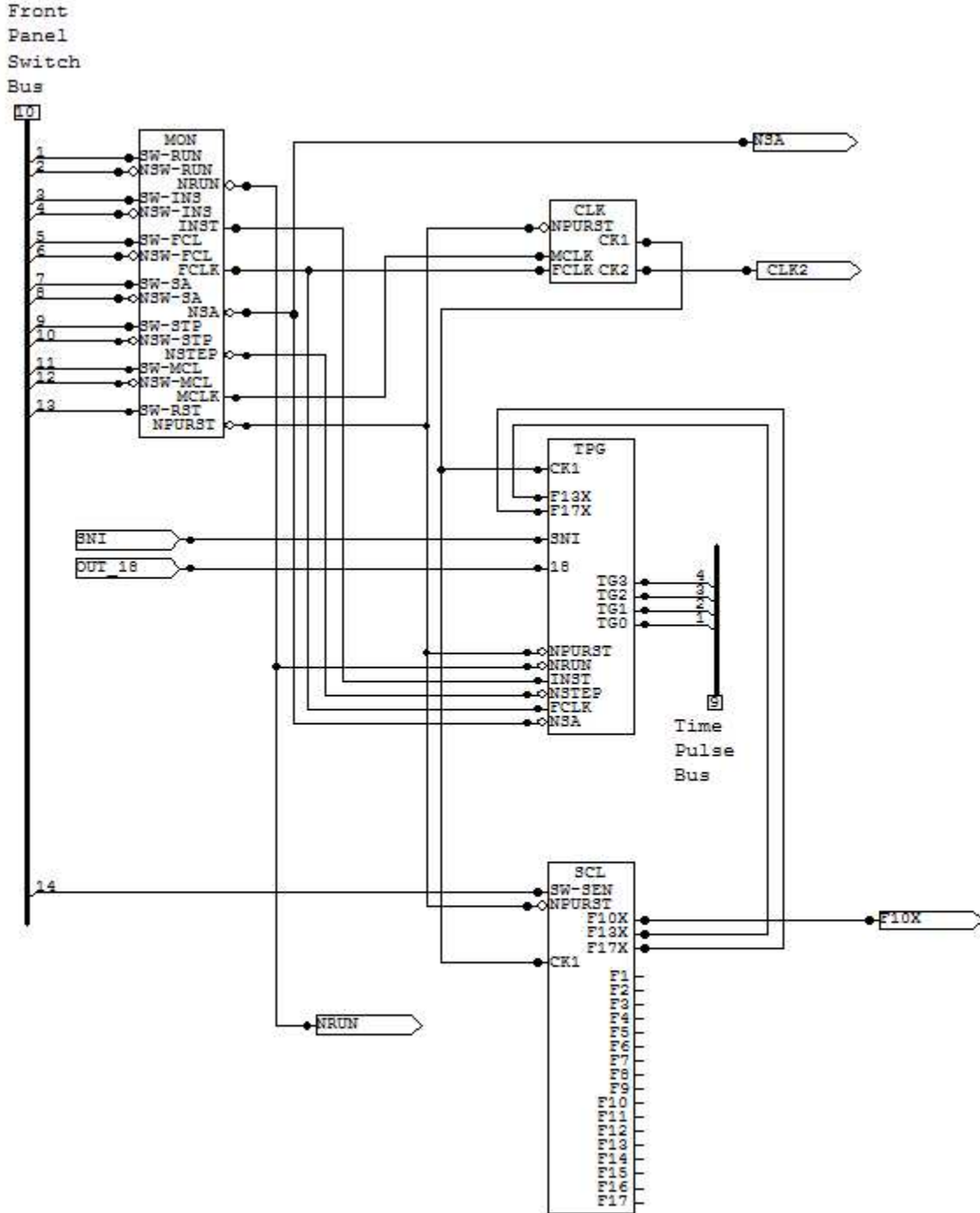This diagram shows internal interconnections for the subsystems in the CTL module.



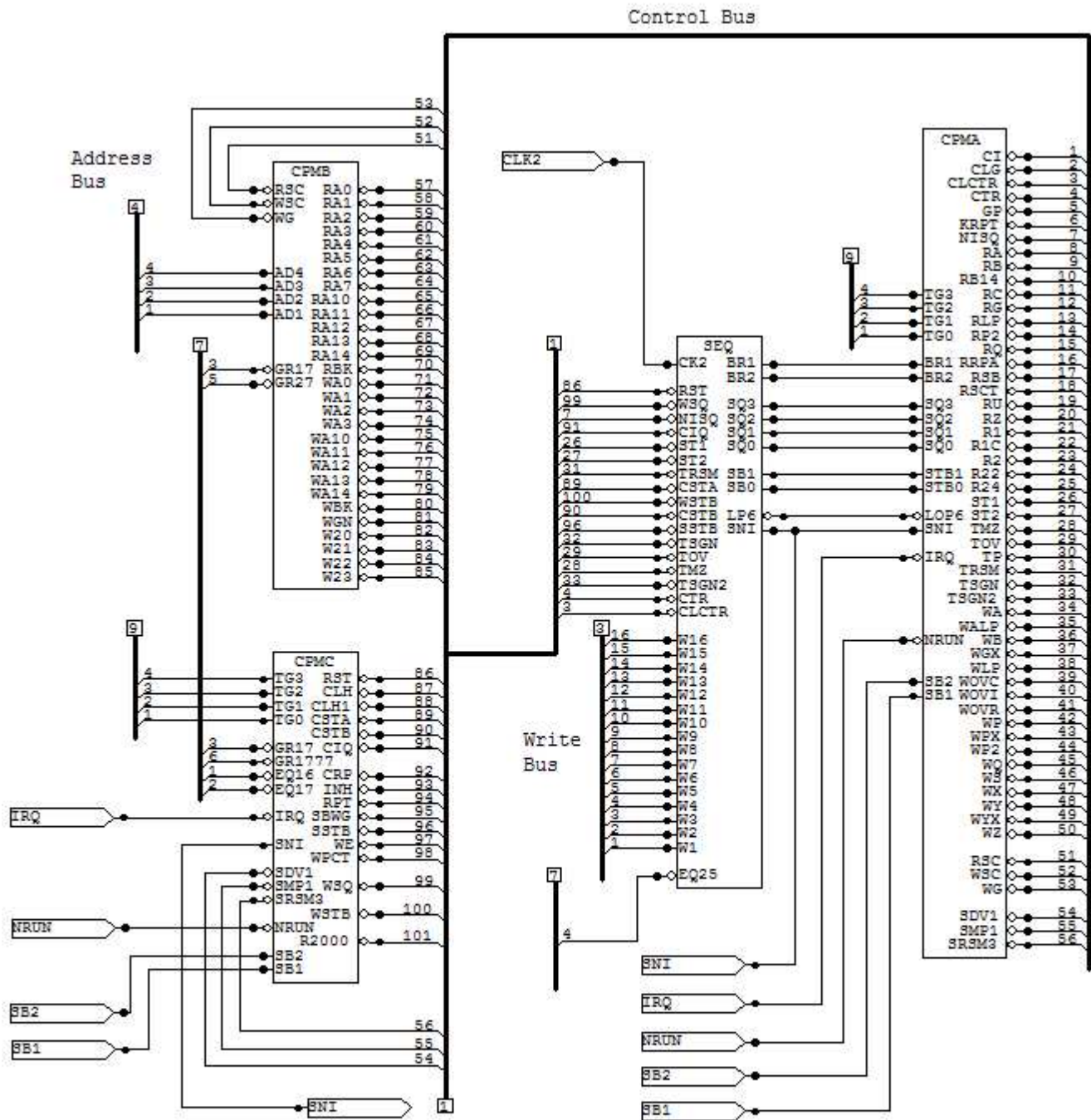
APOLLO GUIDANCE COMPUTER
AGC4 REPLICA
CONTROL MODULE (CTL)
9/8/2003



APOLLO GUIDANCE COMPUTER
 AGC4 REPLICA
 CONTROL MODULE (CTL)
 9/8/2003

CTL Module External Interfaces

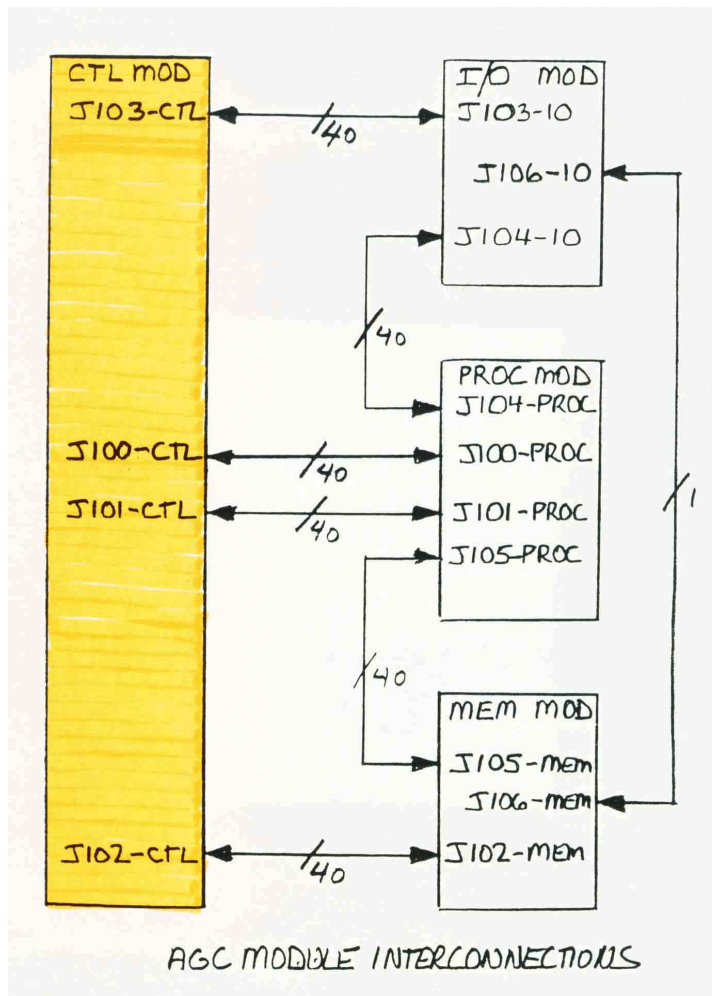The CTL module interfaces to the PROC, MEM, and IO modules through 40-pin IDE ribbon cables.



J100-CTL: CTL-to-PROC I/F

J100 is a 40-pin IDE ribbon cable that connects the CTL module to the PROC module.

OUTPUTS (from CTL):

<u>PIN</u>	<u>signal</u>	<u>full name</u>	<u>state definition</u>
1	WA3	WRITE ADDR 3 (74)	0=Write reg at address 3 (LP)
2	WA2	WRITE ADDR 2 (73)	0=Write reg at address 2 (Z)
3	WA1	WRITE ADDR 1 (72)	0=Write reg at address 1 (Q)
4	WA0	WRITE ADDR 0 (71)	0=Write reg at address 0 (A)
5	RA3	READ ADDR 3 (60)	0=Read reg at address 3 (LP)
6	RA2	READ ADDR 2 (59)	0=Read reg at address 2 (Z)
7	RA1	READ ADDR 1 (58)	0=Read reg at address 1 (Q)
8	RA0	READ ADDR 0 (57)	0=Read reg at address 0 (A)
9	WZ	WRITE Z (50)	0=Write Z
10	WYx	WRITE Y NO RESET (49)	0=Write Y (do not reset)
11	WY	WRITE Y (48)	0=Write Y
12	WX	WRITE X (47)	0=Write X
13	WQ	WRITE Q (45)	0=Write Q
14	WOVR	WRITE OVF (41)	0=Write overflow
15	WOVI	WRITE OVF RUPT INH (40)	0=Write overflow RUPT inhibit
16	WOVC	WRITE OVF CNTR (39)	0=Write overflow counter
17	WLP	WRITE LP (38)	0=Write LP
18	WB	WRITE B (36)	0=Write B
19	WALP	WRITE A/LP (35)	0=Write A and LP
20	WA	WRITE A (34)	0=Write A
21	F10X	F10 SCALER ONESHOT	1=timed out (100.0 Hz)
23	R24	READ 24 (25)	0=Read 24
24	R22	READ 22 (24)	0=Read 22
25	R2	READ 2 (23)	0=Read 2
26	R1C	READ 1 COMP (22)	0=Read 1 complimented
27	R1	READ 1 (21)	0=Read 1
28	RZ	READ Z (20)	0=Read Z
29	RU	READ U (19)	0=Read sum
30	RSCT	READ CNTR ADDR (18)	0=Read selected counter address
31	RSB	READ SIGN (17)	0=Read sign bit
32	RRPA	READ RUPT ADDR (16)	0=Read RUPT address
33	RQ	READ Q (15)	0=Read Q
34	RLP	READ LP (13)	0=Read LP
35	RC	READ C (11)	0=Read C
36	RB14	READ BIT 14 (10)	0=Read bit 14
37	RB	READ B (9)	0=Read B
38	RA	READ A (8)	0=Read A
39	KRPT	KNOCK DOWN RUPT (6)	0=Knock down Rupt priority
40	CI	SET CARRY IN (1)	0=Carry in

J101-CTL: CTL-to-PROC I/F

J101 is a 40-pin IDE ribbon cable that connects the CTL module to the PROC module.

INPUTS (to CTL):

<u>PIN</u>	<u>signal</u>	<u>full name</u>	<u>state definition</u>
21	SB_01	SUB SEL 01	SB_01 is LSB; SB_02 is MSB
22	SB_02	SUB SEL 02	00=no counter; 01=PINC; 10=MINC
23	IRQ	INT RQST	0=interrupt requested.
25	WB_01	WRITE BUS 01	(lsb)
26	WB_02	WRITE BUS 02	
27	WB_03	WRITE BUS 03	
28	WB_04	WRITE BUS 04	
29	WB_05	WRITE BUS 05	
30	WB_06	WRITE BUS 06	
31	WB_07	WRITE BUS 07	
32	WB_08	WRITE BUS 08	
33	WB_09	WRITE BUS 09	
34	WB_10	WRITE BUS 10	
35	WB_11	WRITE BUS 11	
36	WB_12	WRITE BUS 12	
37	WB_13	WRITE BUS 13	
38	WB_14	WRITE BUS 14	
39	WB_15	WRITE BUS 15	US (overflow) bit
40	WB_16	WRITE BUS 16	SG (sign) bit

OUTPUTS (from CTL):

<u>PIN</u>	<u>signal</u>	<u>full name</u>	<u>state definition</u>
1	R2000	READ 2000 (101)	0=Read 2000
2	WPCTR	WRITE PCTR (98)	0=Write PCTR (latch priority counter sequence)
3	RPT	READ RUPT (94)	0=Read RUPT opcode
4	INH	SET INHINT (93)	0=Set INHINT
5	CLRP	CLEAR RPCELL (92)	0=Clear RPCELL
6	CLINH1	CLEAR INHINT1 (88)	0=Clear INHINT1
7	CLINH	CLEAR INHINT (87)	0=Clear INHINT
8	GENRST	GENERAL RESET (86)	0=General Reset
19	CLK1	CLOCK1	1.024 MHz AGC clock 1 (normally low)
20	CLK2	CLOCK2	1.024 MHz AGC clock 2 (normally low)

J102-CTL: CTL-to-MEM I/F

J102 is a 40-pin IDE ribbon cable that connects the CTL module to the MEM module.

INPUTS (to CTL):

<u>PIN</u>	<u>signal</u>	<u>full name</u>	<u>state definition</u>
31	EQU_16	ADDRESS = 016 (1)	0=CADR in register S = 016
32	EQU_17	ADDRESS = 017 (2)	0=CADR in register S = 017
33	GTR_17	ADDRESS > 017 (3)	0=CADR in register S > 017
34	EQU_25	ADDRESS = 025 (4)	0=CADR in register S = 025
35	GTR_27	ADDRESS > 027 (5)	0=CADR in register S > 027
36	GTR_1777	ADDRESS > 01777 (6)	0=CADR in register S > 01777
37	AD_1	ADDRESS (1)	where AD_4 is MSB, AD_1 is LSB:
38	AD_2	ADDRESS (2)	(low-order bits of address)
38	AD_3	ADDRESS (3)	
40	AD_4	ADDRESS (4)	

OUTPUTS (from CTL):

<u>PIN</u>	<u>signal</u>	<u>full name</u>	<u>state definition</u>
1	WE	WRITE EMEM (97)	0=Write E-MEM from G
2	SBWG	WRITE G (95)	0=Write G from memory
3	GENRST	GENERAL RESET (86)	0=General Reset
4	W23	WRITE ADDR 23 (85)	0=Write into SL
5	W22	WRITE ADDR 22 (84)	0=Write into CYL
6	W21	WRITE ADDR 21 (83)	0=Write into SR
7	W20	WRITE ADDR 20 (82)	0=Write into CYR
8	WGn	WRITE G NORMAL (81)	0=Write G (normal gates)
9	WBK	WRITE BNK (80)	0=Write BNK reg
10	RBK	READ BNK (70)	0=Read BNK reg
11	WS	WRITE S (46)	0=Write S
12	WP2	WRITE P2 (44)	0=Write P2
13	WPx	WRITE P NO RESET (43)	0=Write P (do not reset)
14	WP	WRITE P (42)	0=Write P
15	WGx	WRITE G NO RESET (37)	0=Write G (do not reset)
16	TP	TEST PARITY (30)	0=Test parity
17	RP2	READ PARITY 2 (14)	0=Read parity 2
18	RG	READ G (12)	0=Read G
19	GP	GEN PARITY (5)	0=Generate Parity
20	CLG	CLR G (2)	0=Clear G
21	CLK2	CLOCK2	1.024 MHz AGC clock 2 (normally low)
22	CLK1	CLOCK1	1.024 MHz AGC clock 1 (normally low)
23	NPURST	POWER UP RESET	0=reset, 1=normal operation.
24	SWCLK	DEBOUNCE CLOCK	low freq clk for switch debounce
25	FCLK	CLOCK MODE	1=free-running clk mode; 0=single clk mode

J103-CTL: CTL-to-I/O I/F



J100 is a 40-pin IDE ribbon cable that connects the CTL module to the I/O module.

INPUTS (to CTL):


<u>PIN</u>	<u>signal</u>	<u>full name</u>	<u>state definition</u>
40	OUT1_8	STANDBY ENABLED	1=standby enabled; works with STANDBY ALLOWED switch


OUTPUTS (from CTL):

<u>PIN</u>	<u>signal</u>	<u>full name</u>	<u>state definition</u>
1	CLK1	CLOCK1	1.024 MHz AGC clock 1 (normally low)
2	CLK2	CLOCK2	1.024 MHz AGC clock 2 (normally low)
3	NSA	STANDBY ALLOWED	0=standby allowed
5	GENRST	GENERAL RESET (86)	0=clear the DSKY, OUT1, and OUT2.
6	WA11	WRITE OUT1 (76)	0=write into OUT1 from write bus
7	WA10	WRITE OUT0 (75)	0=write into OUT0 (DSKY) from write bus
8	RA11	READ OUT1 (66)	0=output OUT1 register to read bus
9	RA4	READ IN0 (61)	0=output IN0 register to read bus
20	STBY	STANDBY	0=AGC is in the standby state

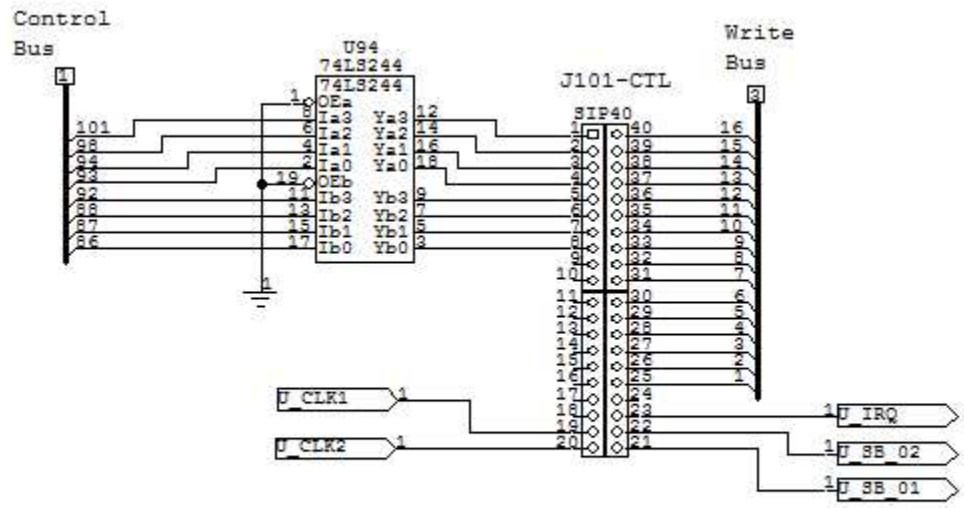 

CTL side of
CTL/PROC I/F

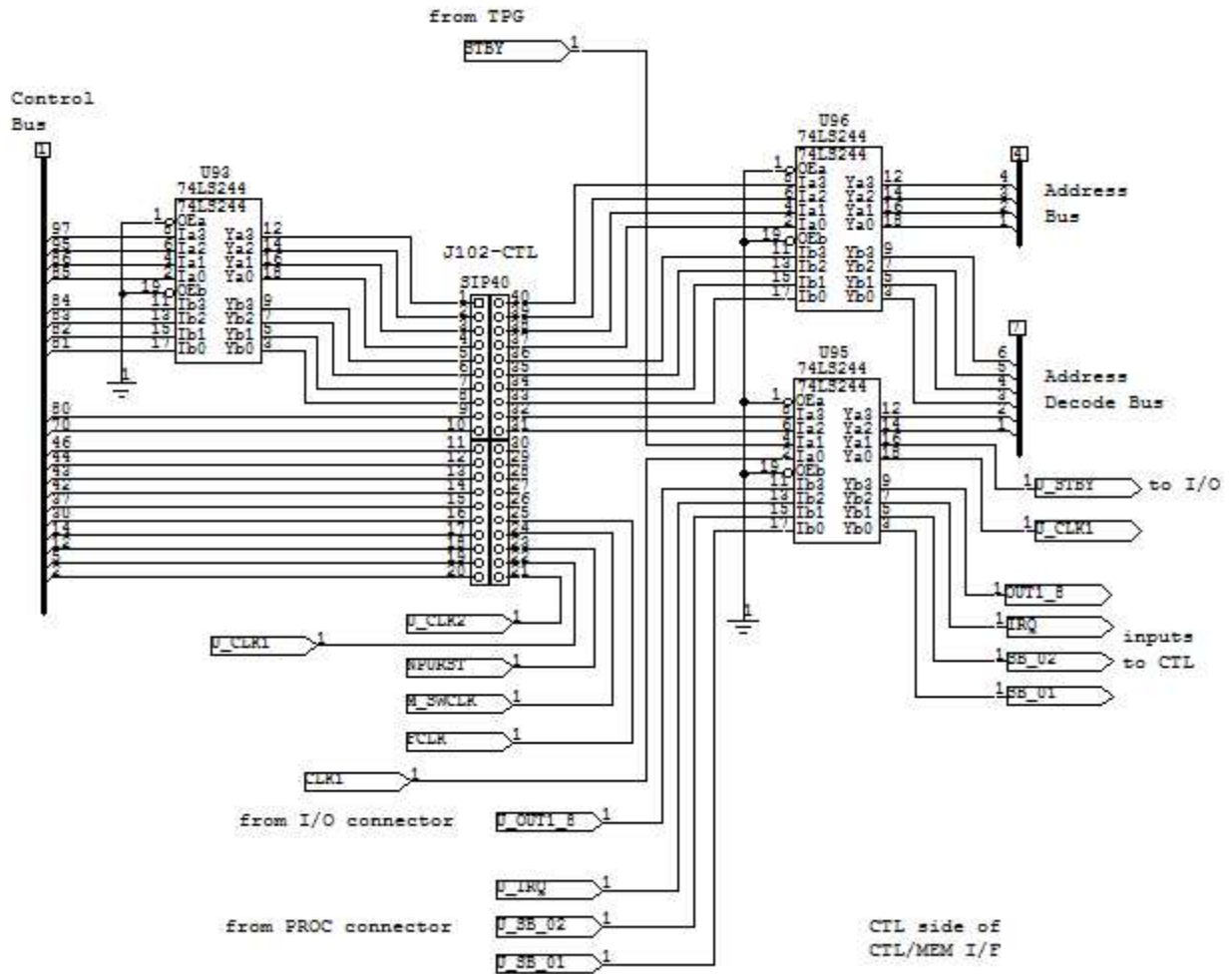


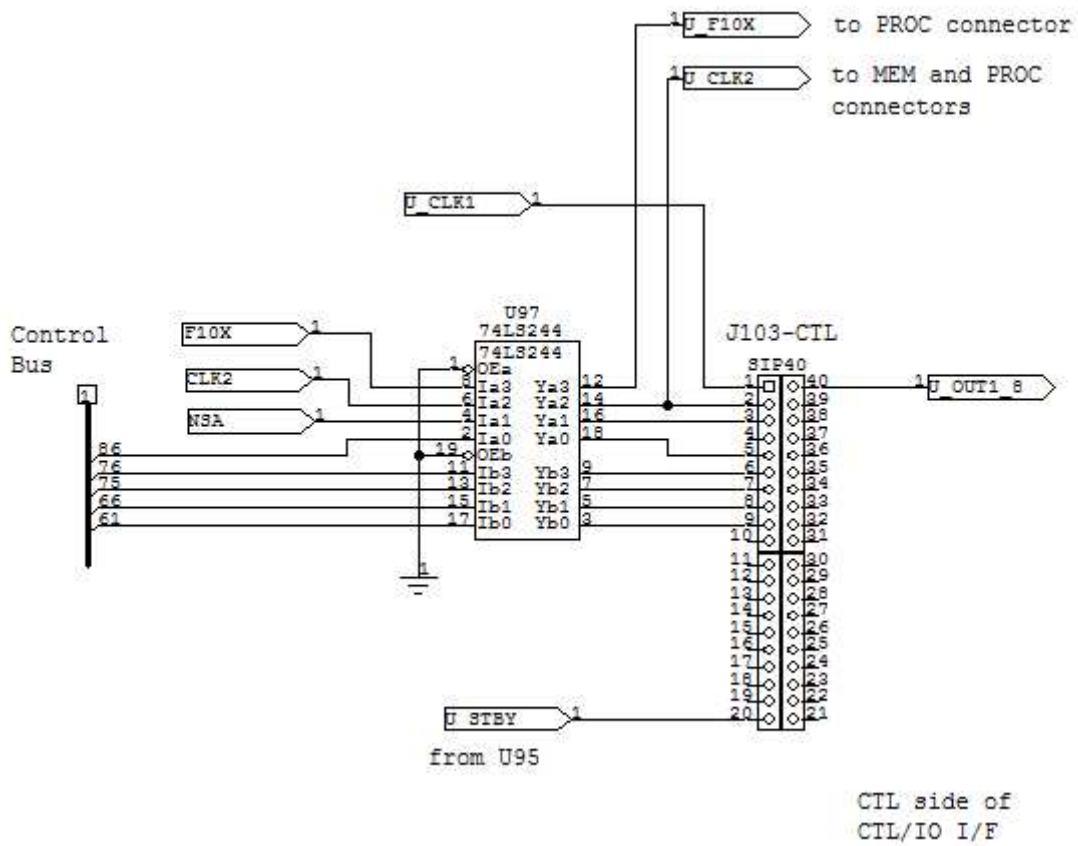

MON (AGC Monitor)

MON INPUTS:

<u>I/F</u>	<u>signal</u>	<u>full name</u>	<u>state definition</u>
	SW-RUN NSW-RUN	RUN/STEP SELECT SW	
	SW-INS NSW-INS	STEP MODE SW	
	SW-FCL NSW-FCL	CLOCK MODE SW	
	SW-SA NSW-SA	STANDBY ALLOWED SW	
	SW-STP NSW-STP	INST STEP SW	
	SW-MCL NSW-MCL	CLOCK STEP SW	
	SW-RST	MASTER RESET SW	

 

MON OUTPUTS:

<u>signal</u>	<u>full name</u>	<u>state definition</u>
NRUN	RUN/HALT	0=run, 1=step
INST	INST STEP MODE	1=instruction step, 0=sequence step
NSTEP	SINGLE STEP	0=step (momentary)
NSA	STANDBY ALLOWED	0=standby allowed
MCLK	CLOCK STEP	1=step (momentary); triggers a single clock pulse. Ignored if FCLK is 1.
FCLK	CLOCK MODE	1=continuous clock output at 1.024 MHz, 0=single clock
NPURST	POWER UP RESET	0=reset, 1=normal operation.
SENAB	SCALER ENABLE	1=enable counting; 0=hold

CTL CONTROL PANEL SWITCHES



Clock Control:

- RATE** Controls the slow clock rate when the 1MHZ/SLOW switch is in the SLOW position.
- 1MHZ/SLOW** Selects the free-running clock rate when the RUN/STEP switch is in the RUN position. The 1MHZ position gates a 2MHz signal into the 2-phased clock which produces a 1MHz 2-phased clock rate. The SLOW position gates a low frequency clock; the frequency is controlled by RATE.
- RUN/STEP** Selects a free-running (RUN) or a single-stepped (STEP) clock. In the RUN position, the rate is controlled by the 1MHZ/SLOW switch. In the STEP position, the clock steps each time the STEP button is depressed.
- STEP** Manually steps the clock when the RUN/STEP switch is in the STEP position. The clock is 2-phased, so each press steps an alternate phase.

Scaler:

- ENAB/DISAB** Enables or disables the SCALER.
- F10** Manually triggers the F10 stage of the SCALER.
- F13** Manually triggers the F13 stage of the SCALER.
- F17** Manually triggers the F17 stage of the SCALER.

Execution Control:

RUN/STEP	In the RUN position, the AGC free-runs at a rate determined by the clock controls. In the STEP position, the AGC single-steps to the next instruction or next sequence when the STEP button is depressed; the rate is determined by the clock controls.
INST/SEQ	Selects whether the AGC single-steps all the way to the next instruction (INST) or just to the next sequence (SEQ). Some instructions, such as TC, have a single sequence; on these instructions, the switch has the same effect in either position.
STEP	Single-steps the AGC when the RUN/STEP switch is in the STEP position.
RESET	Reset the entire AGC. Puts the TPG into the standby state.

Standby:

ALLOW/DISA	The ALLOWED position authorizes the AGC software to put the AGC in standby mode. The AGC is released from standby mode by a signal from F17 in the SCALER. If the scaler switch is in the DISAB position, the scaler is disabled, and the AGC will remain in the standby state. When the standby switch is in the DISAB position, the standby mode is inhibited.
------------	--


Normal Operation:

Set the following switch positions for nominal operation:



<u>switch</u>	<u>position</u>
1MHZ/SLOW	1MHZ
RUN/STEP	RUN (clock control)
ENAB/DISAB	ENAB (scaler)
RUN/STEP	RUN (execution control)
ALLOW/DISA	ALLOWED (standby)




CTL CONTROL SWITCH CONNECTIONS

<u>PIN</u>	<u>signal</u>	<u>state definition</u>
1	BUS# 10, line 1	Execution control: RUN/STEP
2	BUS# 10, line 2	
3	BUS# 10, line 3	Execution control: INST/SEQ
4	BUS# 10, line 4	
5	BUS# 10, line 5	Clock control: RUN/STEP
6	BUS# 10, line 6	
7	BUS# 10, line 7	STANDBY ALLOWED/DISABLED
8	BUS# 10, line 8	
9	BUS# 10, line 9	Execution control: STEP
10	BUS# 10, line 10	
11	BUS# 10, line 11	Clock control: STEP
12	BUS# 10, line 12	
13	BUS# 10, line 13	RESET
14	BUS# 10, line 14	SCALER DISAB
15	RATE	(SLOW) CLOCK CONTROL RATE
16	1MHZ	Clock control: 1MHZ/SLOW
17	SLOW	
18	F10	MANUAL TRIGGER F10
19	F13	MANUAL TRIGGER F13
20	F17	MANUAL TRIGGER F17

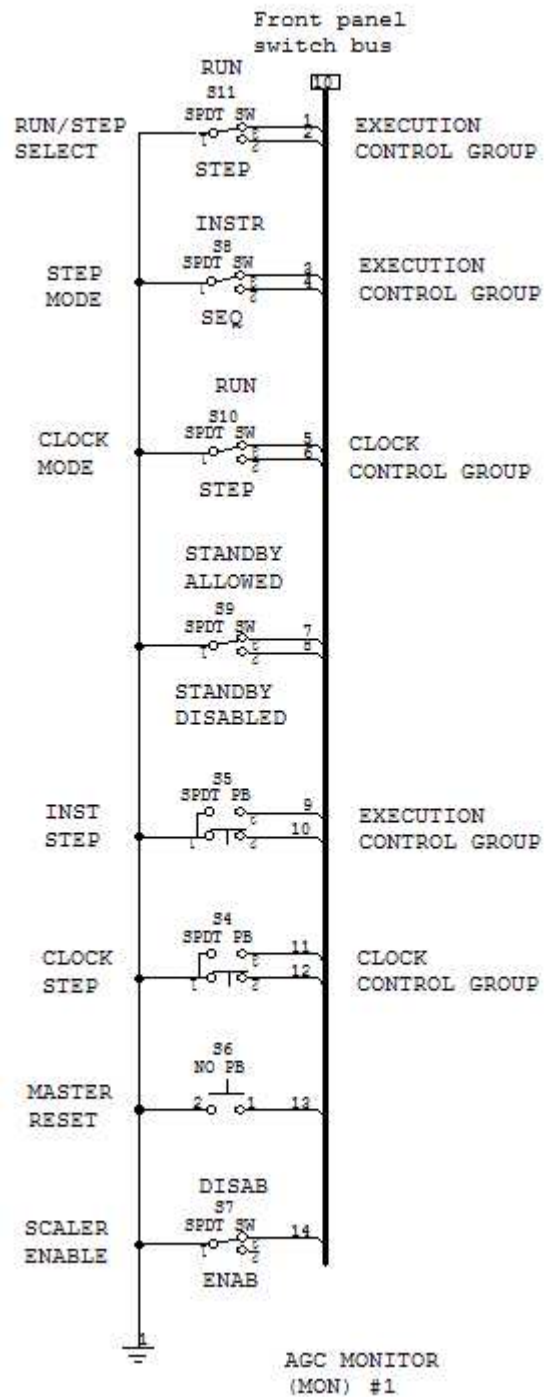

AGC MONITOR
SWITCH DEBOUNCE CLOCK

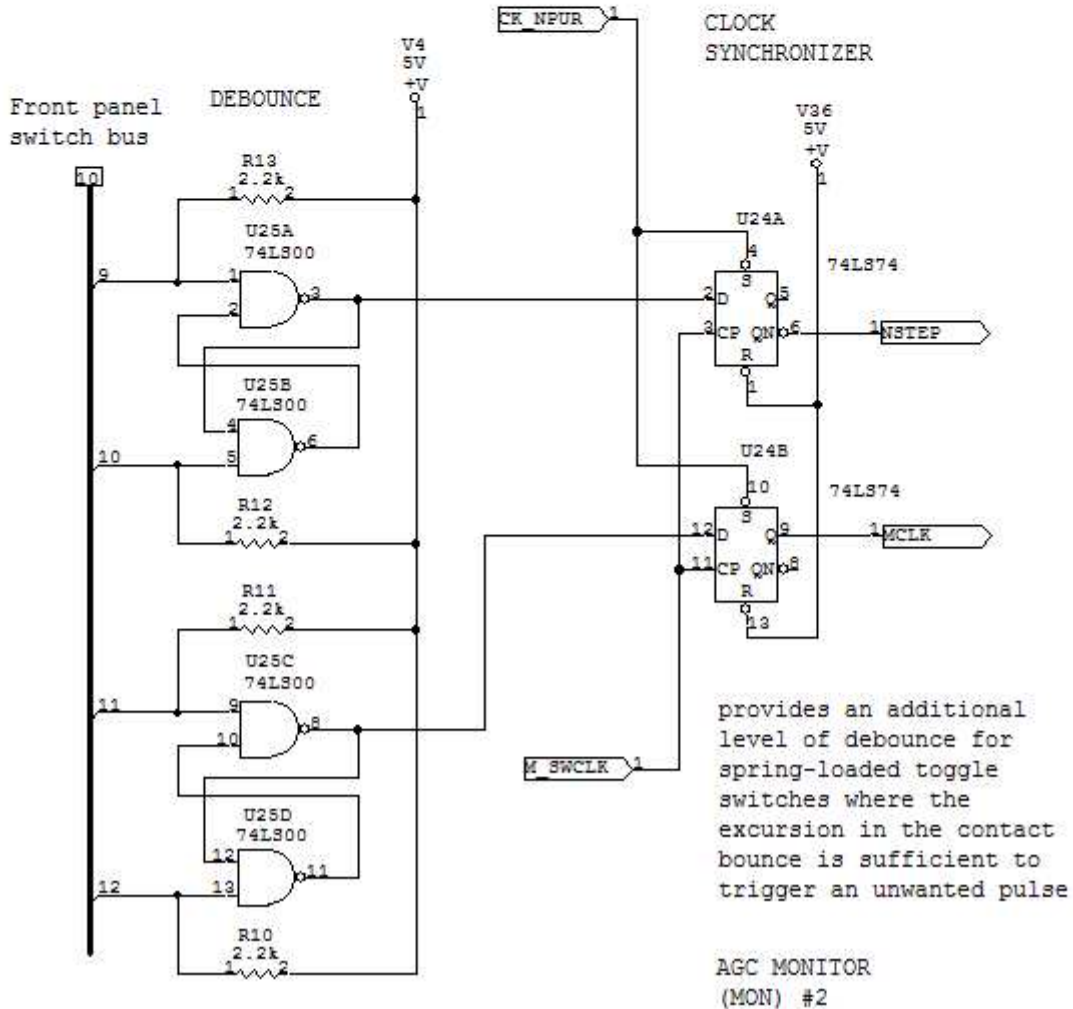 


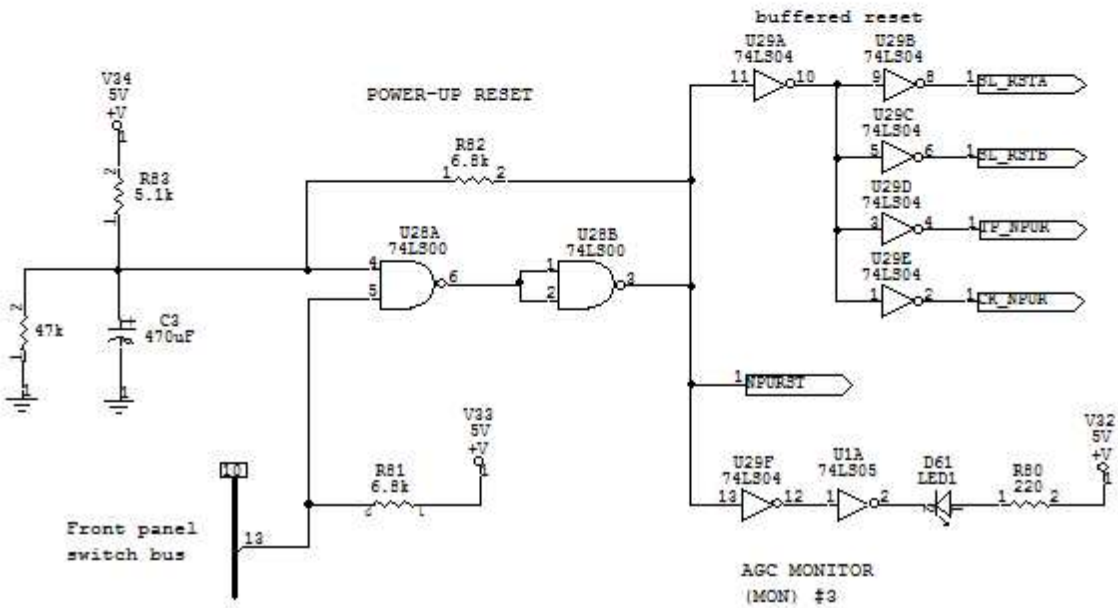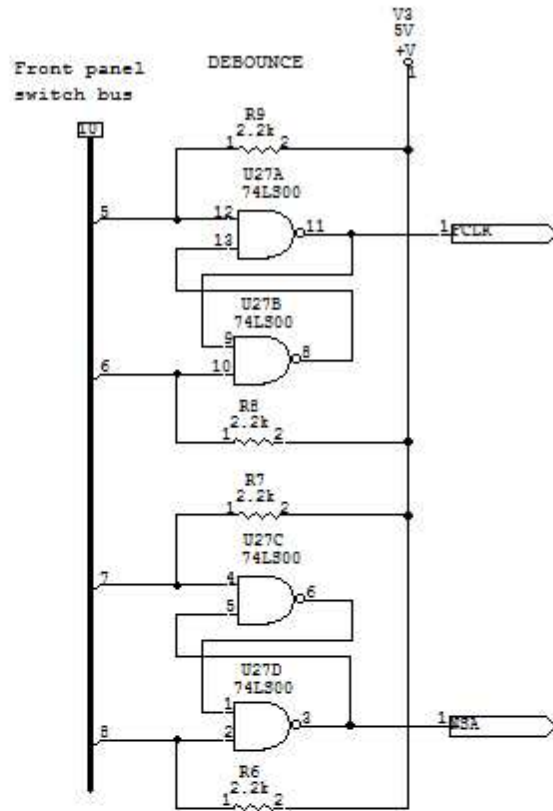
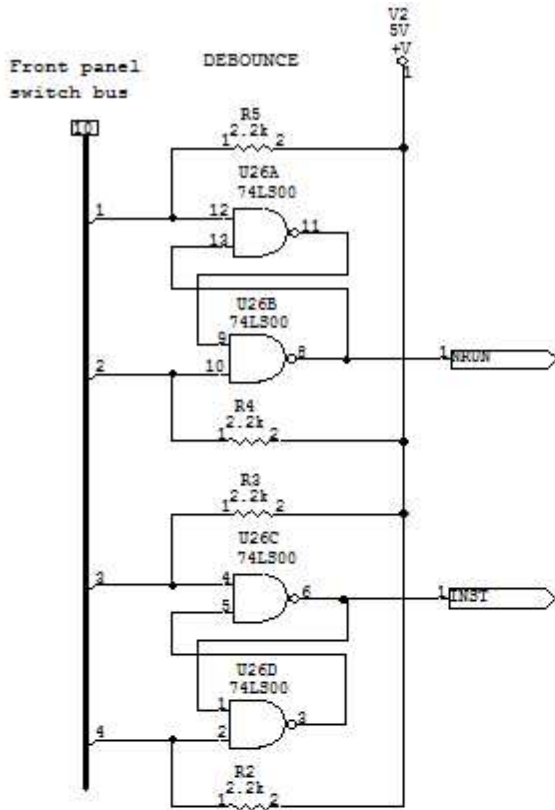


CTL INDICATORS


The CTL module has a panel of indicator lamps (LEDs) to show the state of CTL registers and critical logic signals.

These indicator lamps show the current state of all registers and some additional, important logic signals produced by the CTL module. The matrix of lamps in the lower portion show active subsequences. Much of the control logic is negative (active low) where an illuminated lamp means that the signal is NOT asserted. At the time the photo was taken the AGC was running the COLOSSUS 249 flight software load, executing Verb 16, Noun 36: a monitor verb which displays the AGC real time clock.


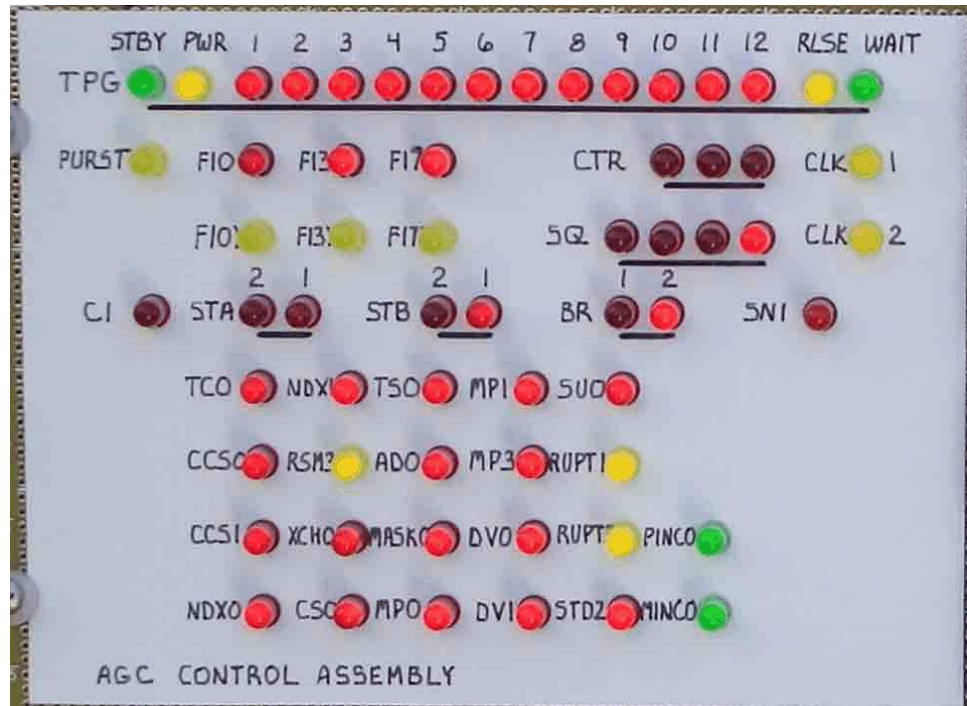


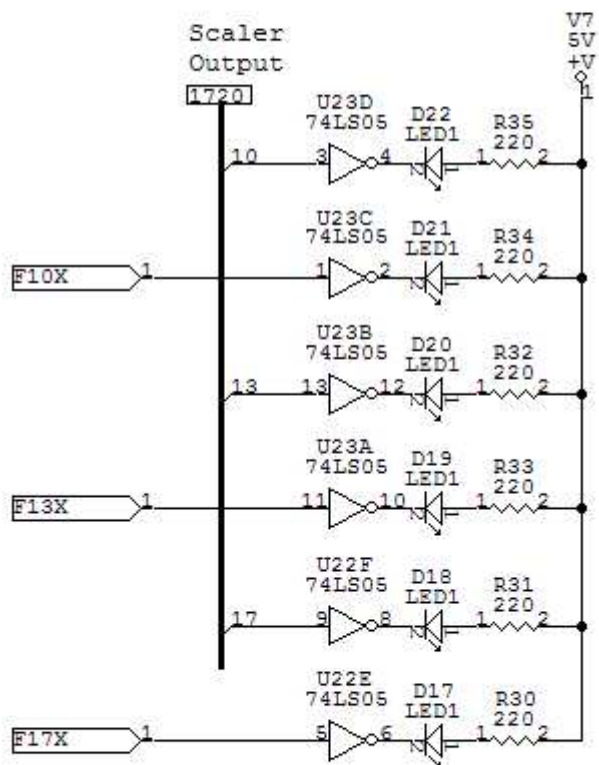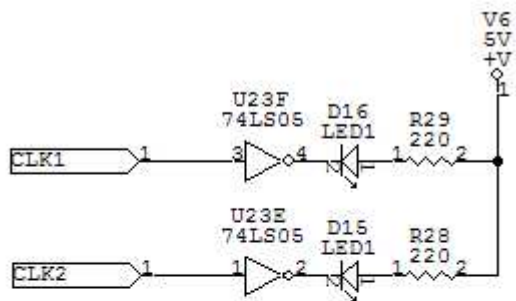

AGC MONITOR
 (MON) #4

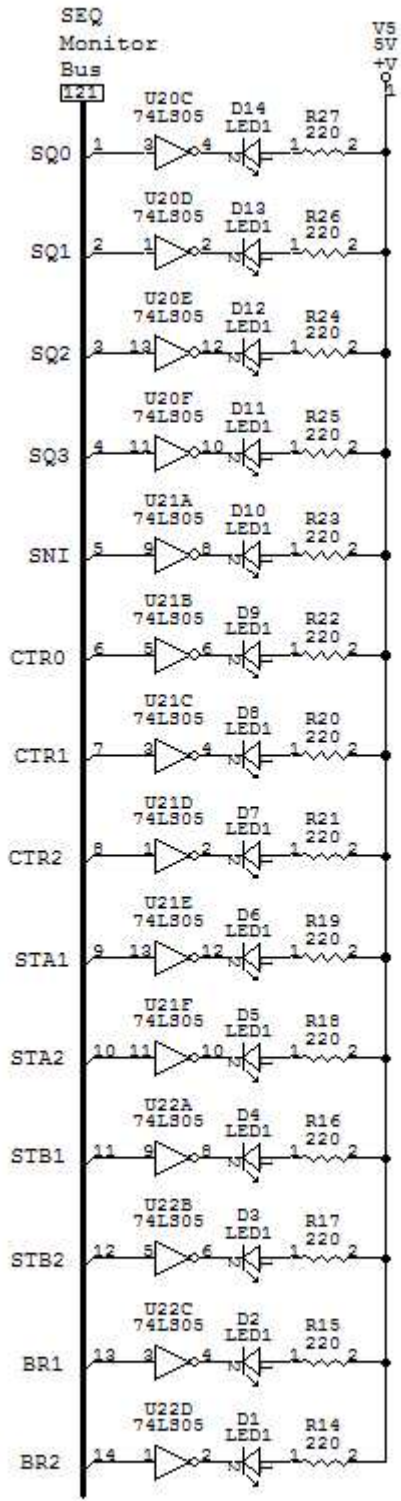

AGC MONITOR
 (MON) #5

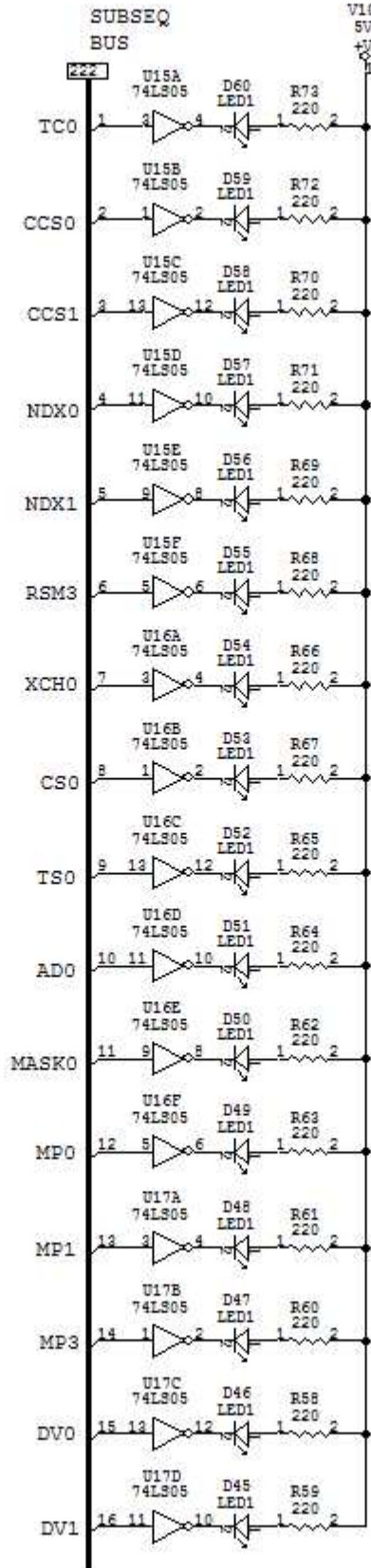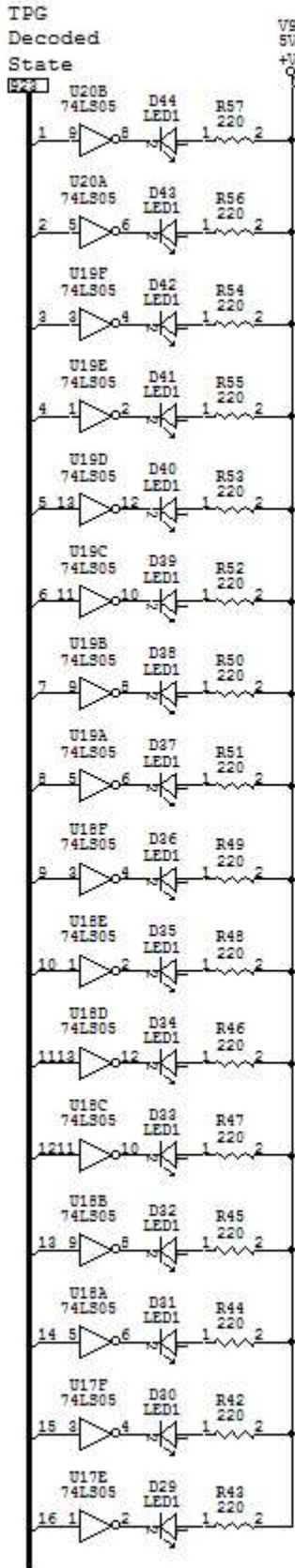


AGC MONITOR (MON) #6

CLK (Clock)

The original AGC used asynchronous logic driven by a 4-phase clock. This recreation uses synchronous logic driven by a 2-phase non-overlapping clock. The synchronous clock logic was designed to produce the following state transitions:

FFA	FFB	
0	0	idle state
0	1	decoded for phase 1
1	1	
1	0	decoded for phase 2

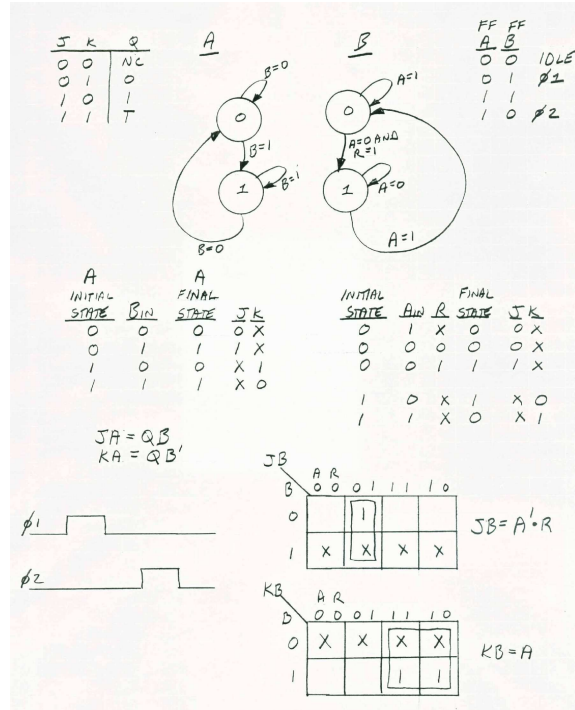The outputs of FFA and FFB are decoded by combinational logic to produce the non-overlapping phase 1 and phase 2 clock signals. The sequence is arranged so there is a single logic level transition for each state transition to prevent transients.




CLK INPUTS:


<u>I/F</u>	<u>signal</u>	<u>full name</u>	<u>state definition</u>
MON:	MCLK	CLOCK STEP	1=step (momentary); triggers a single clock pulse. Ignored if FCLK is 1.
	FCLK	CLOCK MODE	1=continuous clock output at 1.024 MHz, 0=single clock whenever MCLK is 1.
	NPURST	POWER UP RESET	0=power up reset

OUTPUTS:


<u>signal</u>	<u>full name</u>	<u>state definition</u>
CLK1	CLOCK1	1.024 MHz AGC clock 1 (normally low)
CLK2	CLOCK2	1.024 MHz AGC clock 2 (normally low)

 


AGC CLOCK

 

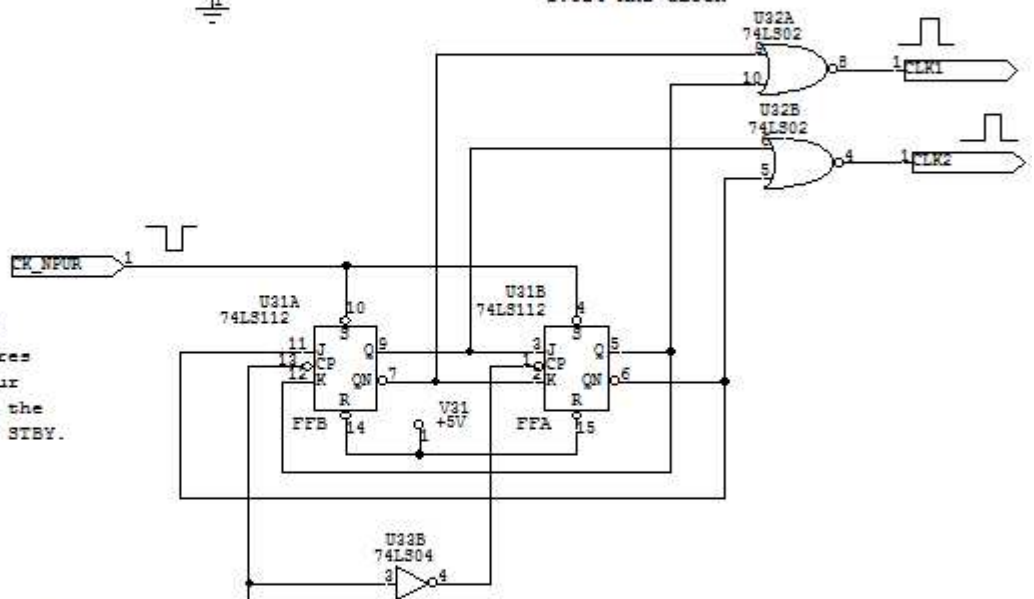TWO PHASE NON-OVERLAPPING
1.024 MHZ CLOCK



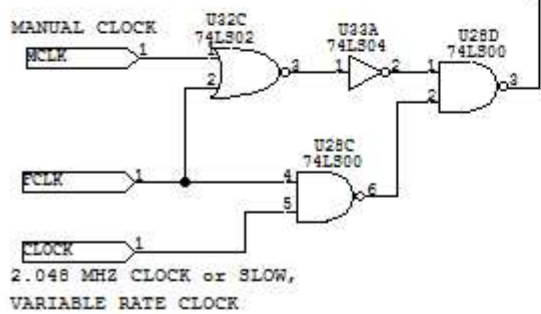Initialize so CLK2
occurs first; ensures
that CLK2 will occur
at least once when the
time pulse code is STBY.




2.048 MHZ CLOCK or SLOW,
VARIABLE RATE CLOCK

FCLK=1: free-running
clock;
FCLK=0: manually-
stepped clock

AGC CLOCK
(CLK) #1

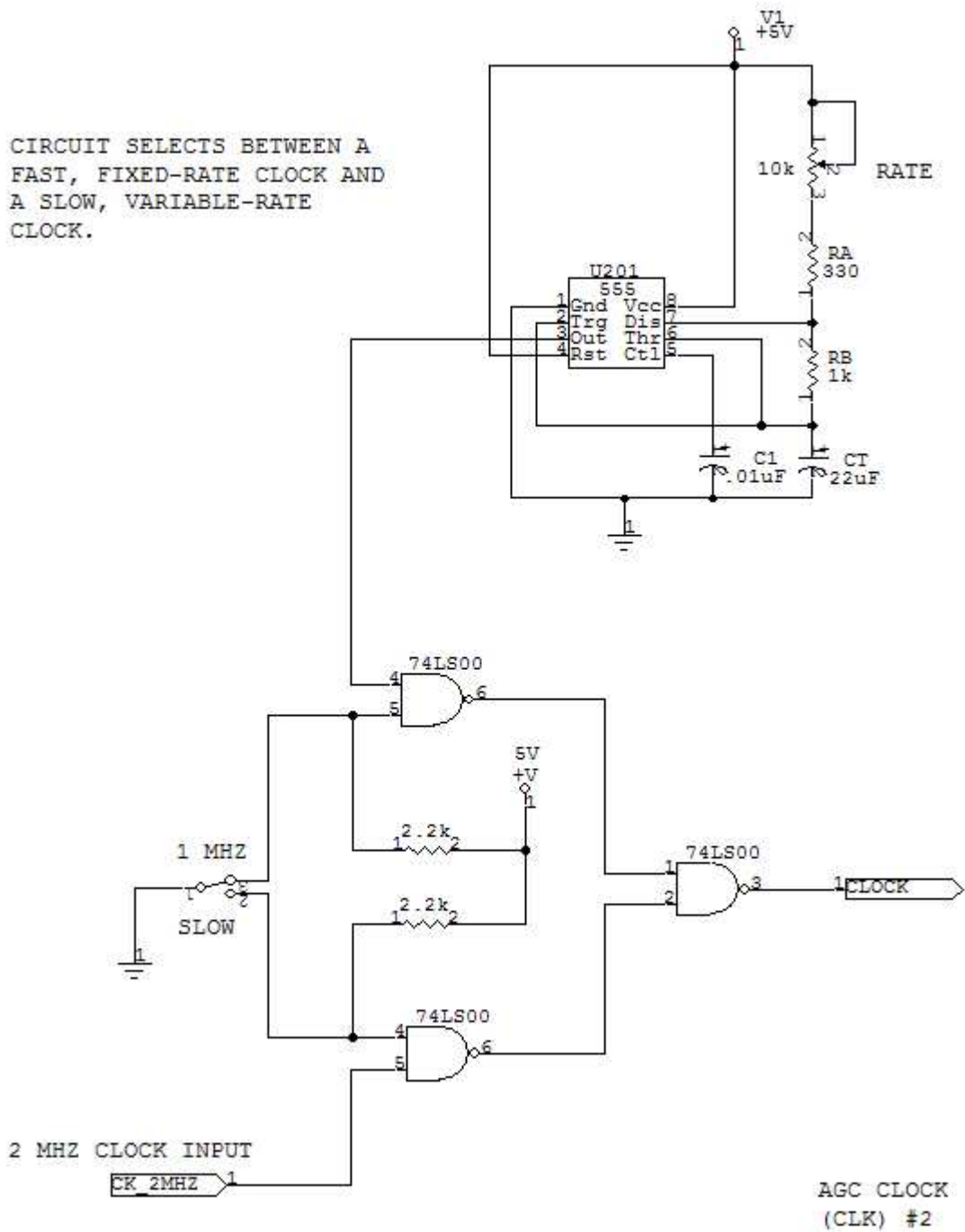
CIRCUIT SELECTS BETWEEN A FAST, FIXED-RATE CLOCK AND A SLOW, VARIABLE-RATE CLOCK.



SCL (Scaler)

The 1.024 MHz AGC clock is divided by two to produce a 512 kHz signal called the MASTER FREQUENCY; this signal is further divided through a SCALER, first by five to produce a 102.4 kHz signal. This is then divided by two through 17 successive stages called F1 (51.2 kHz) through F17 (0.78125 Hz). The F10 stage (100 Hz) is fed back into the AGC to increment the real-time clock and other priority counters in the PROC module. The F17 stage is used to intermittently run the AGC when it operates in the STANDBY mode.

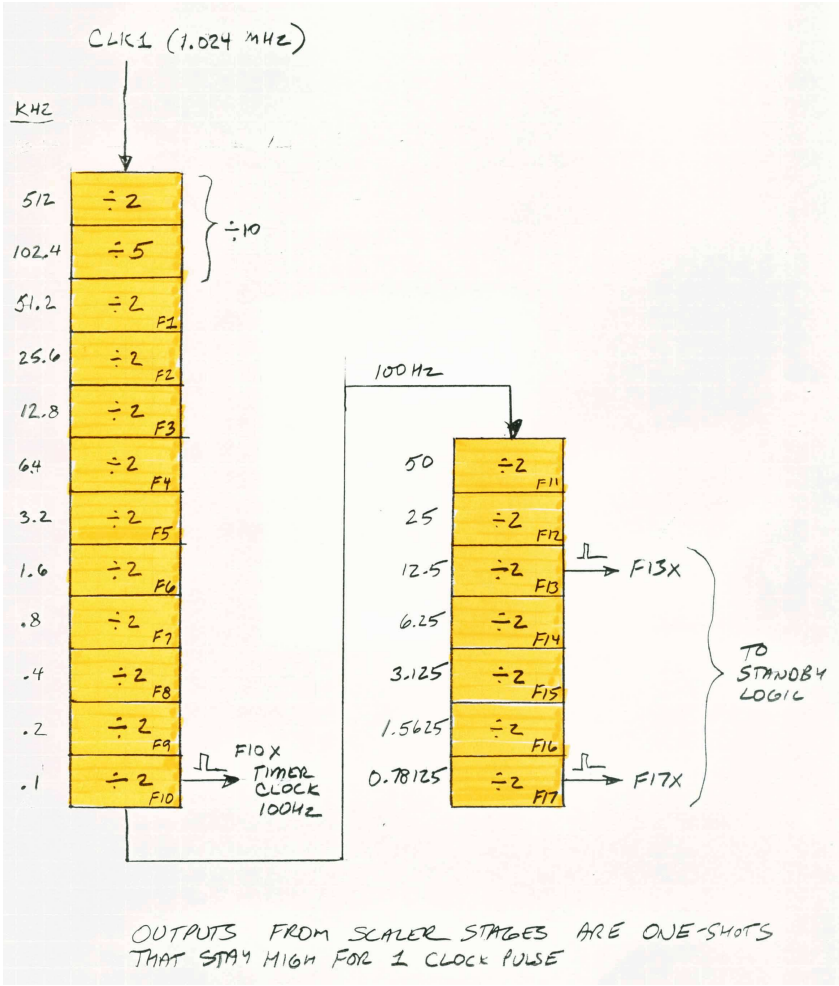The F10, F13, and F17 outputs of the SCALER feed into a synchronous one-shot that produces a short output pulse on the rising edge of the input.



SCALER (SCL) ONE-SHOT LOGIC DESIGN

Boolean operators:

* (AND), + (OR), ' (NOT)

Scaler Divide-by-10 Excitation Table:

The divide-by-10 state machine is implemented with a 74161 parallel counter. Control Mode for 74161 Parallel Counter:

<u>NPE</u>	<u>CET</u>	
0	x	LOAD
1	1	COUNT
1	0	HOLD

State	Current				Next				Par In					
	D	C	B	A	D	C	B	A	NPE	CET	D	C	B	A
0	0	0	0	0	0	0	0	1	1	1				
1	0	0	0	1	0	0	1	0	1	1				
2	0	0	1	0	0	0	1	1	1	1				
3	0	0	1	1	0	1	0	0	1	1				
4	0	1	0	0	0	1	0	1	1	1				
5	0	1	0	1	0	1	1	0	1	1				
6	0	1	1	0	0	1	1	1	1	1				
7	0	1	1	1	1	0	0	0	1	1				
8	1	0	0	0	1	0	0	1	1	1				
9	1	0	0	1	0	0	0	0	0	x	0	0	0	0

$$NPE = (D * A)'$$

$$CET = 1$$

One-shot Excitation Table:

The one-shot state machine is implemented with two J-K FFs.

JK flip-flop excitation table:

<u>J</u>	<u>K</u>	
0	0	Qn-1 (no change)
0	1	0
1	0	1
1	1	Qn-1' (toggle)

FN is the one-shot trigger; Q(A) is the one-shot output.

State	Cur		Inp	Nxt		ffB		ffA	
	B	A	FN	B	A	J	K	J	K
IDLE	0	0	0	0	0	0	x	0	x
	0	0	1	0	1	0	x	1	x

HIGH	0 1	0	1 0	1 x	x 1
	0 1	1	1 0	1 x	x 1
LOW	1 0	0	0 0	x 1	0 x
	1 0	1	1 0	x 0	0 x
UNUSED	1 1	0	x x	x x	x x
	1 1	1	x x	x x	x x

The excitation table and logic equations were derived from the CLK subsystem state machine which also performs a one-shot function. The CLK subsystems's FCLK signal was factored out by setting it to zero. The MCLK input is the one-shot trigger; it was renamed FN.

$$\text{ff(B) J} = \text{QA}$$

$$\text{ff(B) K} = \text{FN}'$$

$$\text{ff(A) J} = \text{QB}' * \text{FN}$$


$$\text{ff(A) K} = \text{QA}$$

SCL INPUTS:


<u>I/F</u>	<u>signal</u>	<u>full name</u>	<u>state definition</u>
CLK:	CLK1	CLOCK1	1.024 MHz AGC clock
MON:	SW-SEN	SCALER ENABLE	1=enable counting;
0=hold	NPURST	POWER UP RESET	0=power up reset

SCL OUTPUTS:


<u>signal</u>	<u>full name</u>	<u>state definition</u>
F10X	F10 SCALER ONESHOT	1=timed out (100.0 Hz)
F13X	F13 SCALER ONESHOT	1=timed out (12.5 Hz)
F17X	F17 SCALER ONESHOT	1=timed out (0.78125 Hz)
F1	SCALER OUT F1	51.2 KHz square wave
F2	SCALER OUT F2	25.6 KHz square wave
F3	SCALER OUT F3	12.8 KHz square wave
F4	SCALER OUT F4	6.4 KHz square wave
F5	SCALER OUT F5	3.2 KHz square wave
F6	SCALER OUT F6	1.6 KHz square wave
F7	SCALER OUT F7	0.8 KHz square wave
F8	SCALER OUT F8	0.4 KHz square wave
F9	SCALER OUT F9	0.2 KHz square wave
F10	SCALER OUT F10	0.1 KHz square wave (100 Hz)
F11	SCALER OUT F11	50.0 Hz square wave
F12	SCALER OUT F12	25.0 Hz square wave
F13	SCALER OUT F13	12.5 Hz square wave
F14	SCALER OUT F14	6.25 Hz square wave
F15	SCALER OUT F15	3.125 Hz square wave
F16	SCALER OUT F16	1.5625 Hz square wave
F17	SCALER OUT F17	0.78125 Hz square wave

 

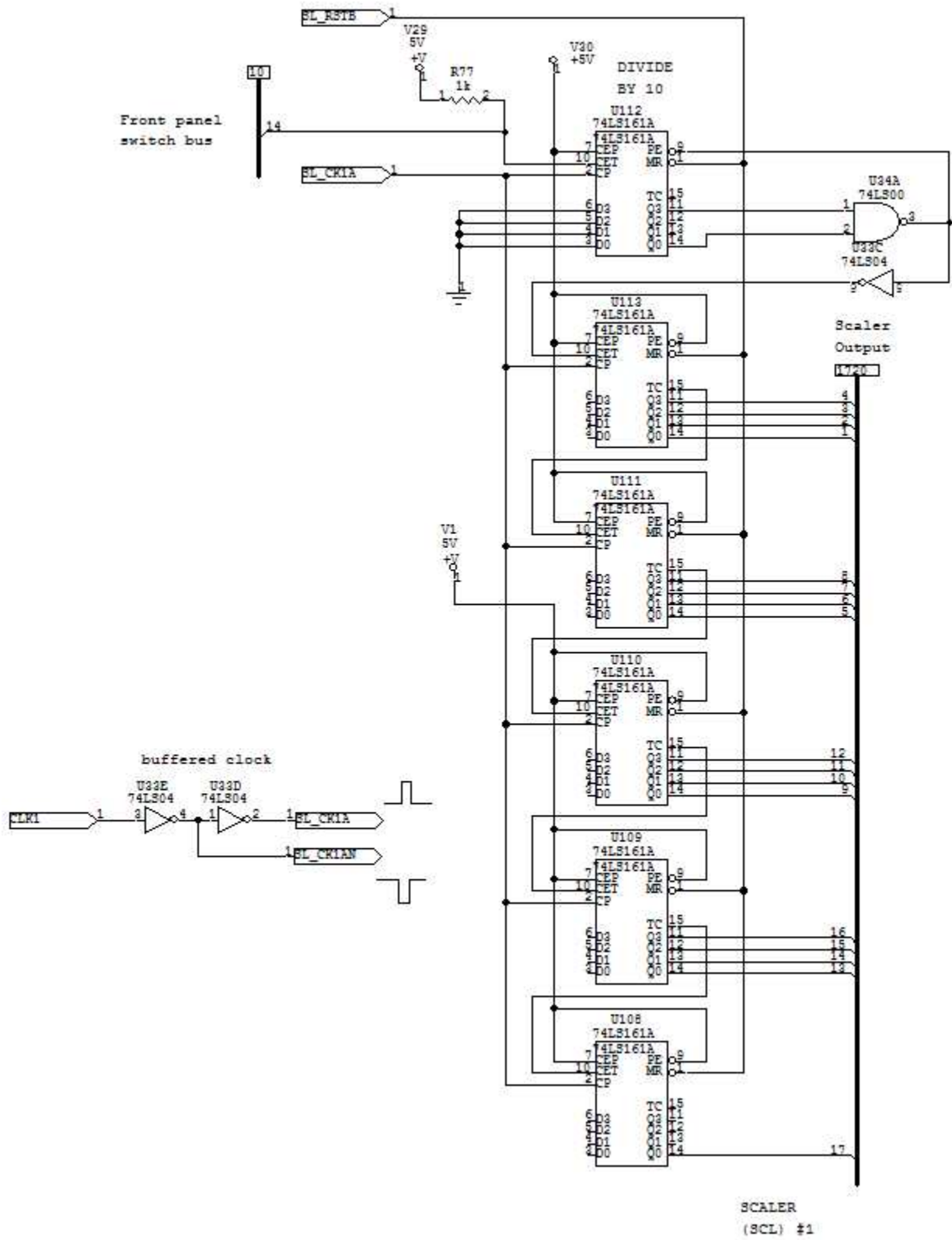Note: One shot outputs are active for one clock pulse.
State transitions occur on the rising edge of CLK1




Scaler
Output
10220

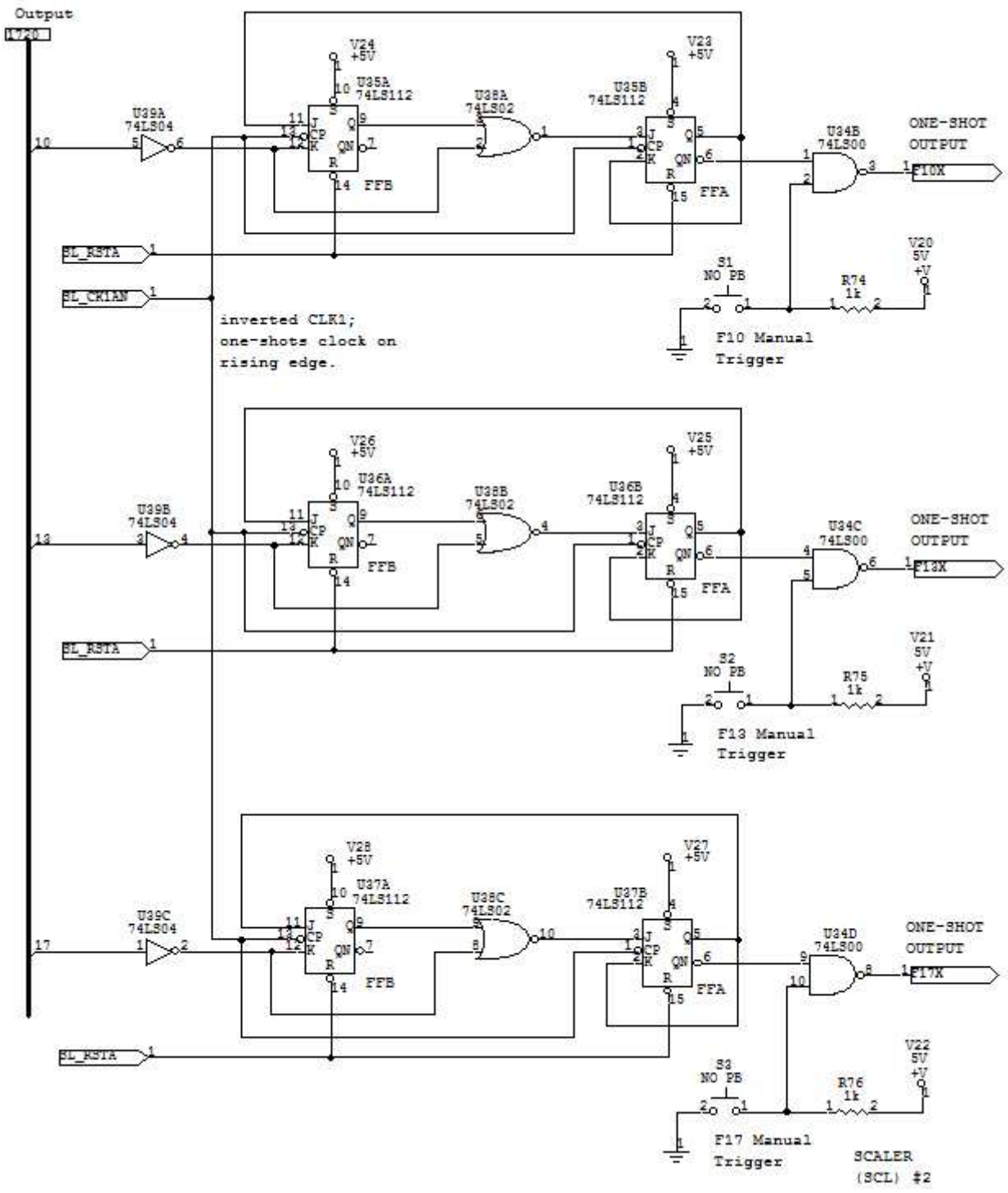

SCALER
(SCL) #2

TPG (Time Pulse Generator)

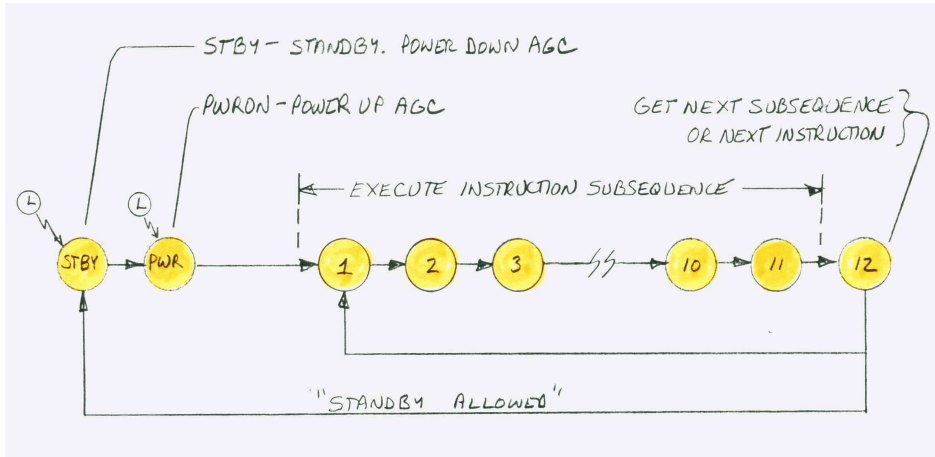

TIME PULSE GENERATOR (TPG) LOGIC DESIGN

Boolean operators:

* (AND), + (OR), ' (NOT)

TPG Internal Control Signals:

These are local to the TPG; if the signal is d, TPG makes a state transition. These signals are the inputs to the excitation

$$TPG_0 = PURST' * (FCLK' + F17X)$$


$$TPG_1 = FCLK' + F13X$$

$$TPG_2 = RUN + (SNI' * INST)$$

$$TPG_3 = SNI * OUT1_8 * SA$$

$$TPG_4 = STEP'$$

$$TPG_5 = STEP + RUN$$

 

asserte decoded table.

TPG Excitation Table:

Control Mode for 74161 Parallel Counter:

<u>NPE</u>	<u>CET</u>	
0	x	LOAD
1	1	COUNT
1	0	HOLD

*denotes active low

<u>State</u>	<u>Current</u>				<u>*Current Decoder</u>	<u>TPG_x</u>					<u>Next</u>				<u>*NPE</u>	<u>CET</u>	<u>Par In</u>			
	<u>D</u>	<u>C</u>	<u>B</u>	<u>A</u>		<u>0</u>	<u>1</u>	<u>2</u>	<u>3</u>	<u>4</u>	<u>5</u>	<u>D</u>	<u>C</u>	<u>B</u>			<u>A</u>	<u>D</u>	<u>C</u>	<u>B</u>
STBY	0	0	0	0	NSTBY	0	x	x	x	x	0	0	0	0	1	0				
						1	x	x	x	x	0	0	0	1	1	1				
PWRON	0	0	0	1	NPWRON	x	0	x	x	x	0	0	0	1	1	0				
						x	1	x	x	x	0	0	1	0	1	1				
TP1	0	0	1	0	NTP1	x	x	x	x	x	0	0	1	1	1	1				
TP2	0	0	1	1	NTP2	x	x	x	x	x	0	1	0	0	1	1				
TP3	0	1	0	0	NTP3	x	x	x	x	x	0	1	0	1	1	1				
TP4	0	1	0	1	NTP4	x	x	x	x	x	0	1	1	0	1	1				
TP5	0	1	1	0	NTP5	x	x	x	x	x	0	1	1	1	1	1				
TP6	0	1	1	1	NTP6	x	x	x	x	x	1	0	0	0	1	1				
TP7	1	0	0	0	NTP7	x	x	x	x	x	1	0	0	1	1	1				
TP8	1	0	0	1	NTP8	x	x	x	x	x	1	0	1	0	1	1				
TP9	1	0	1	0	NTP9	x	x	x	x	x	1	0	1	1	1	1				
TP10	1	0	1	1	NTP10	x	x	x	x	x	1	1	0	0	1	1				
TP11	1	1	0	0	NTP11	x	x	x	x	x	1	1	0	1	1	1				

TP12	1 1 0 1	NTP12	x x x 1 x x	0 0 0 0	0	x	0 0 0 0
			x x 1 0 x x	0 0 1 0	0	x	0 0 1 0
			x x 0 0 x x	1 1 1 0	1	1	
SRLSE	1 1 1 0	NSRLSE	x x x x 0 x	1 1 1 0	1	0	
			x x x x 1 x	1 1 1 1	1	1	
WAIT	1 1 1 1	NWAIT	x x x x x 1	0 0 1 0	0	x	0 0 1 0
			x x x x x 0	1 1 1 1	1	0	

Maxterms:

$$NPE = (NTP12 + TPG_3') * (NTP12 + TPG_2' + TPG_3) * (NWAIT + TPG_5')$$


$$CET = (NSTBY + TPG_0) * (NPWRON + TPG_1) * (NSRLSE + TPG_4) * (NWAIT + TPG_5)$$

$$\text{Par In A,B,C} = 0$$

$$\text{Par In B} = (NTP12' * TPG_3)'$$

TPG INPUTS:


<u>I/F</u>	<u>signal</u>	<u>full name</u>	<u>state definition</u>
MON:	NRUN	RUN/HALT	0=run, 1=step
	INST	INST STEP MODE	1=instruction step,
0=sequence step	NSTEP	SINGLE STEP	0=step (momentary)
	FCLK	CLOCK MODE	1=continuous, 0=single clock
	NSA	STANDBY ALLOWED	0=standby allowed
	NPURST	POWER UP RESET	0=power up reset
CLK:	CLK1	CLOCK1	1024 MHz AGC clock 1
SEQ:	SNI	SELECT NEXT INST	1=select next instruction
SCL:	F17X	F17 SCALER ONESHOT	1=timed out
	F13X	F13 SCALER ONESHOT	1=timed out
OUT:	OUT1_8	STANDBY ENABLED	1=standby enabled; works with STANDBY ALLOWED switch

 

TPG OUTPUTS:


<u>signal</u>	<u>full name</u>	<u>state definition</u>
TPG_Q3	TPG STATE	where Q0 is LSB, Q3 is MSB:
TPG_Q2		00 = STBY
TPG_Q1		01 = PWRON
TPG_Q0		02 = TP1
		03 = TP2
		04 = TP3
		05 = TP4
		06 = TP5
		07 = TP6
		08 = TP7
		09 = TP8
		10 = TP9
		11 = TP10
		12 = TP11
		13 = TP12
		14 = SRLSE
		15 = WAIT

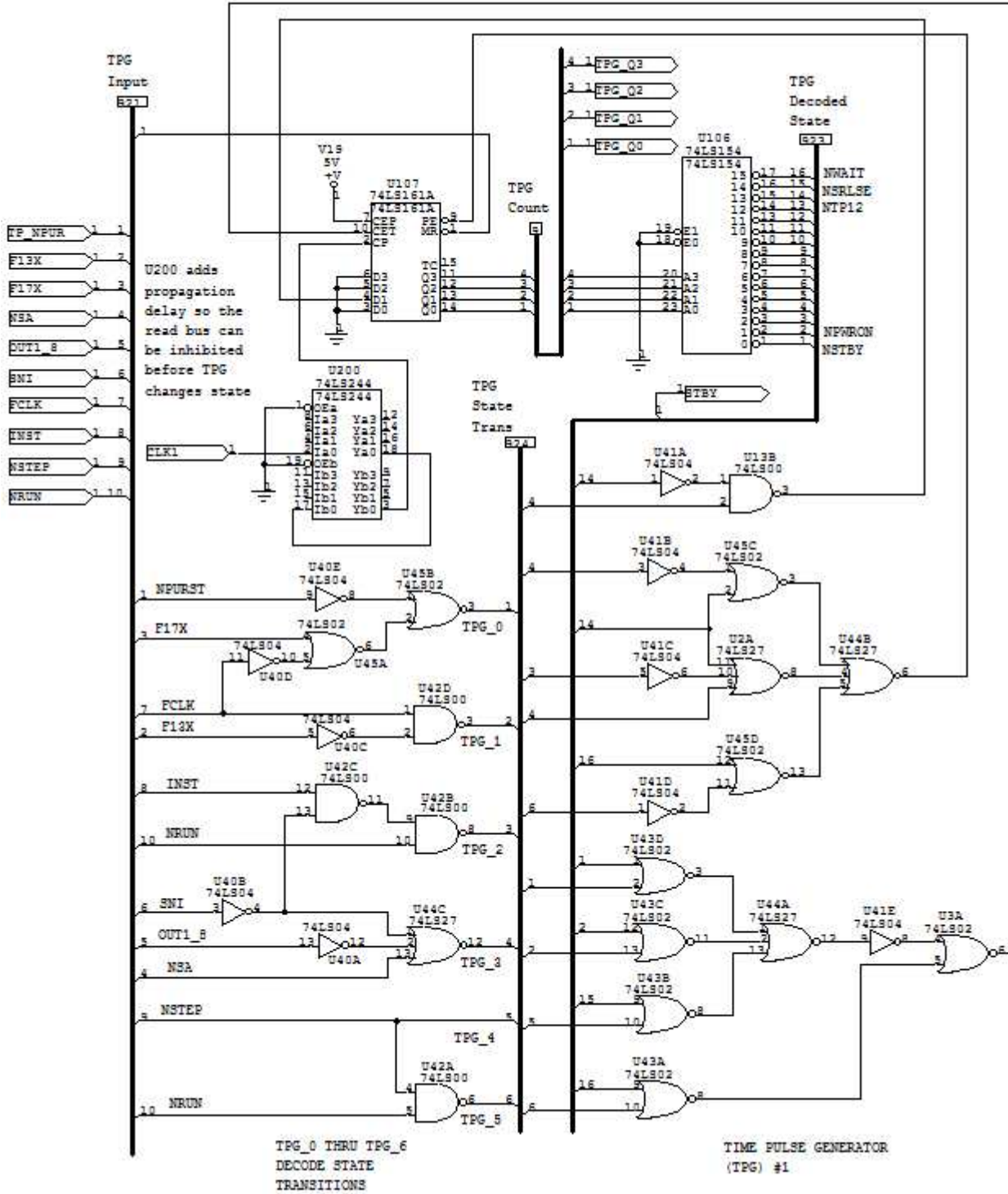STATE CHANGES OCCUR ON
 RISING EDGE OF CLK1




SEQ (Sequence Generator)

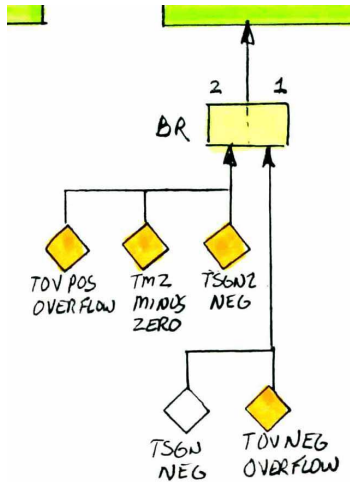The sequence generator contains the stage registers and branch registers that (along with the time pulse generator) control execution of the microinstruction sequence.




 Some back-of-the-envelope design that went into the branch register logic is shown in the next few charts. This is the conceptual design for the branch register. It has 2 flip-flops named BR2 and BR1. The flip-flops are set by the control signals shown as diamonds in this diagram.




The J and K inputs to the BR1 flip-flop are developed in this chart.

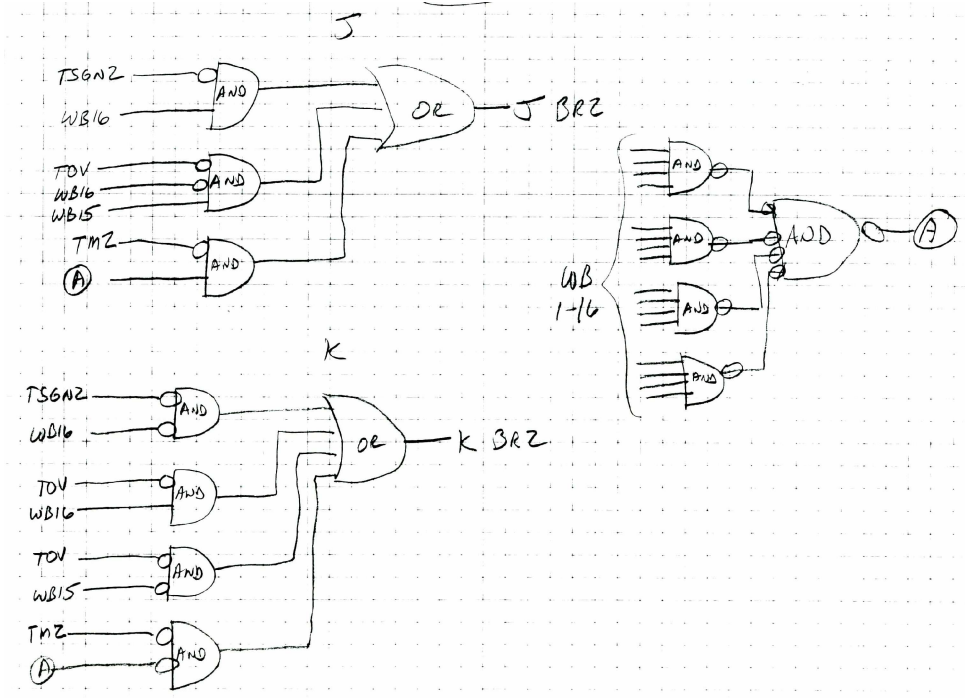
This chart shows the J and K inputs to the BR2 flip-flop. Logic to sense a 1's compliment minus zero from the write bus is also developed.




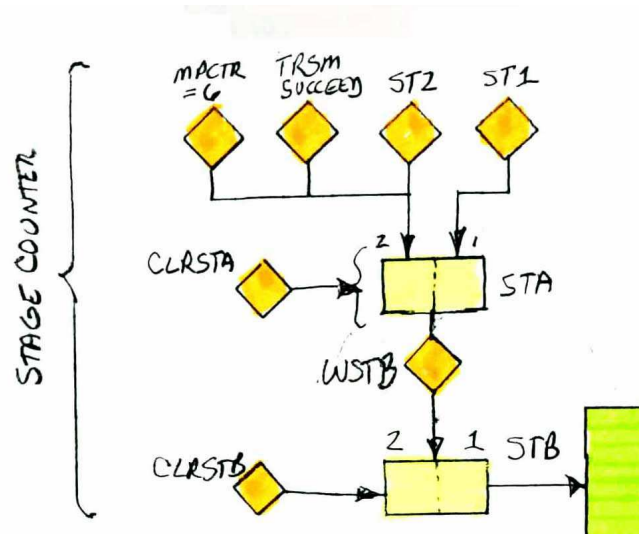
Here are some charts showing the stage register design. This is the conceptual design. There are (2) 2-bit stage registers: STA and STB.



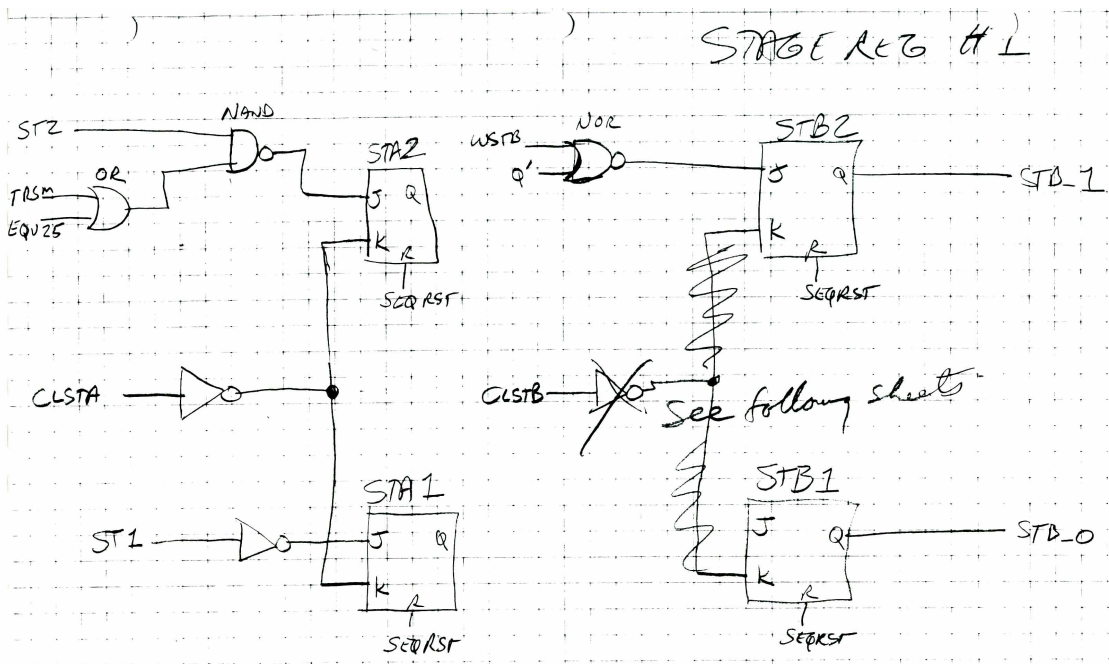This is my initial cut at STA and STB. My initial attempt at CLSTB is scratched out and then developed into the correct solution on the later charts.





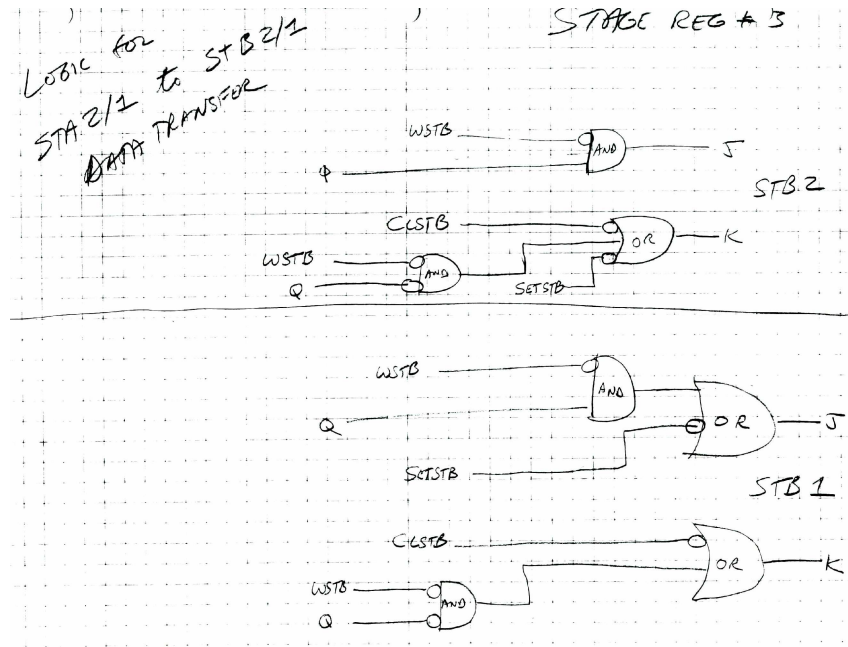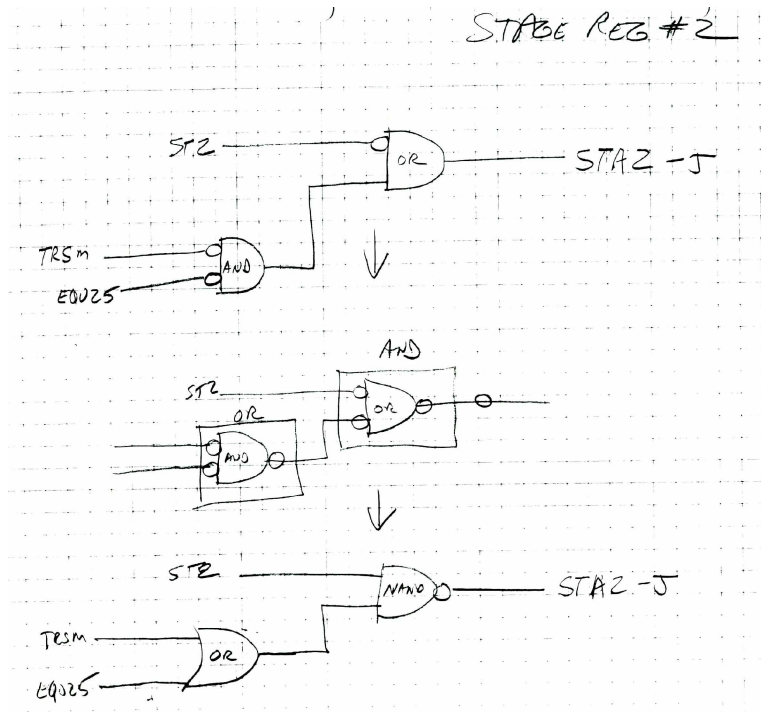This is the J input to the STA2 flip-flop. The initial design is at the top. In the middle, I "DeMorganize" it using some bubble-pushing to get the final implementation at the bottom.




Here's the J and K inputs to STB1 and STB2. This is the logic that transfers the contents of the STA flip-flops to STB.

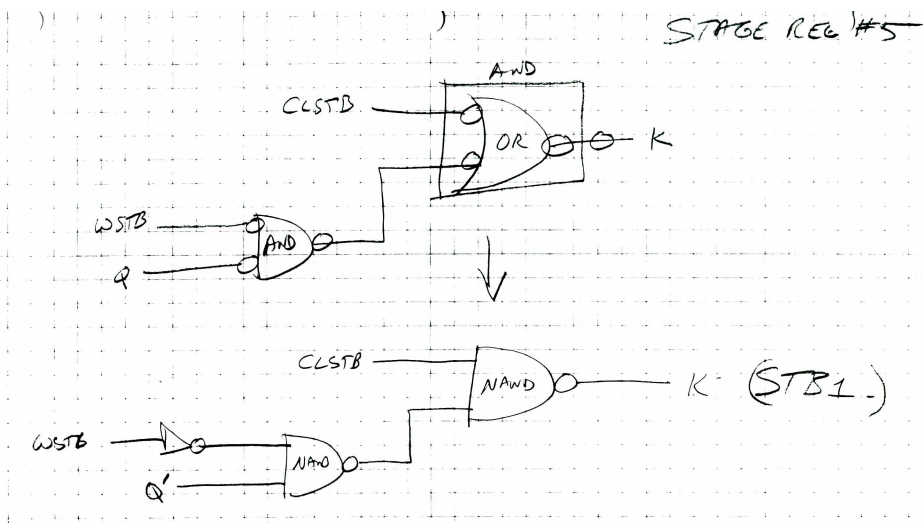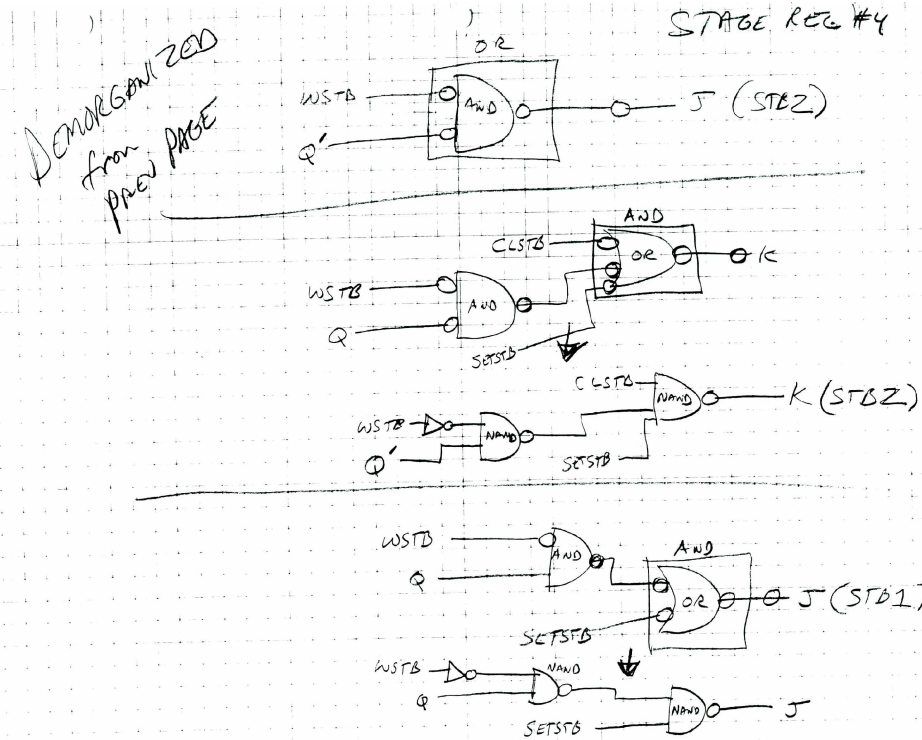The J and K inputs to STB1 and STB2 move through a multi-step DeMorganizing process in the next 2 charts to reach their final state:



SEQ INPUTS:


I/F	signal	full name	state definition
CLK:	CLK2	CLOCK 2	data transfer occurs on falling edge
CPM-C:	GENRST	GENERAL RESET	0=General Reset
	WSQ	WRITE SQ	0=Write SQ
	CLISQ	CLEAR SNI	0=Clear SNI
	CLSTA	CLEAR STA	0=Clear state counter A (STA)
	WSTB	WRITE STB	0=Write stage counter B (STB)
	CLSTB	CLEAR STB	0=Clear state counter B (STB)
	SETSTB	SET ST1	0=Set the ST1 bit of STB
CPM-A:	TRSM	TEST RESUME	0=Test for resume
	TSGN	TEST SIGN	0=Test sign
	TSGN2	TEST SIGN 2	0=Test sign 2
	ST1	SET STAGE 1	0=Stage 1
	ST2	SET STAGE 2	0=Stage 2
	CLCTR	CLR LOOP CTR	0=Clear loop counter
	CTR	INCR LOOP CTR	0=Loop counter
	TMZ	TEST MINUS ZERO	0=Test for minus zero
	TOV	TEST OVF	0=Test for overflow
	NISQ	NEW INSTRUCT SQ reg	0=New instruction to the
WBUS:	WB_01	WRITE BUS 01	
	
	WB_14	WRITE BUS 14	
	WB_15	WRITE BUS 15	US (overflow) bit for write bus
	WB_16	WRITE BUS 16	SG (sign) bit for write bus
ADR:	EQU_25	ADDRESS = 025	0=CADR in register S evaluates to = 025

 

SEQ OUTPUTS:


I/F	signal	full name	state definition
CPM-A:	BR1	BRANCH REG 1	where BR1 is MSB, BR2 is LSB
	BR2	BRANCH REG 2	BR00 =0 BR1=0, BR2=0
			BR01 =1 BR1=0, BR2=1
			BR10 =2 BR1=1, BR2=0
			BR11 =3 BR1=1, BR2=1

SQ_3 SQ_2 SQ_1 SQ_0	INST REG	where SQ_3 is MSB, SQ_0 is LSB
STB_1 STB_0	STAGE REG	where STB_1 is MSB, STB_0 is LSB
LOOP6	LOOPCNTR EQ 6	0=LOOPCNTR is holding the number 6.
SNI	SELECT NEXT INST	1=select next instruction (SNI register)

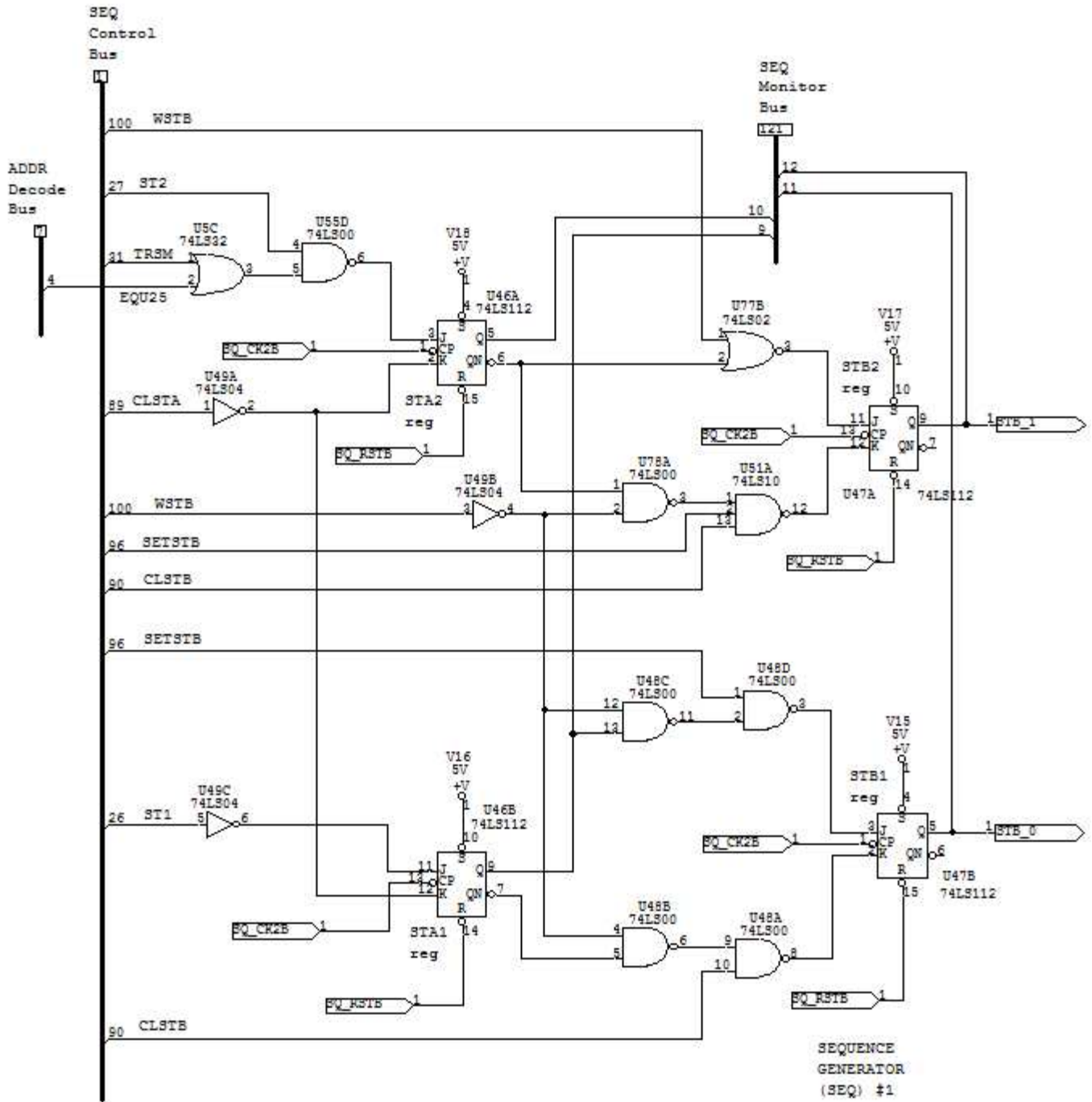


SEQ
Control
Bus



SEQ
internal
write bus

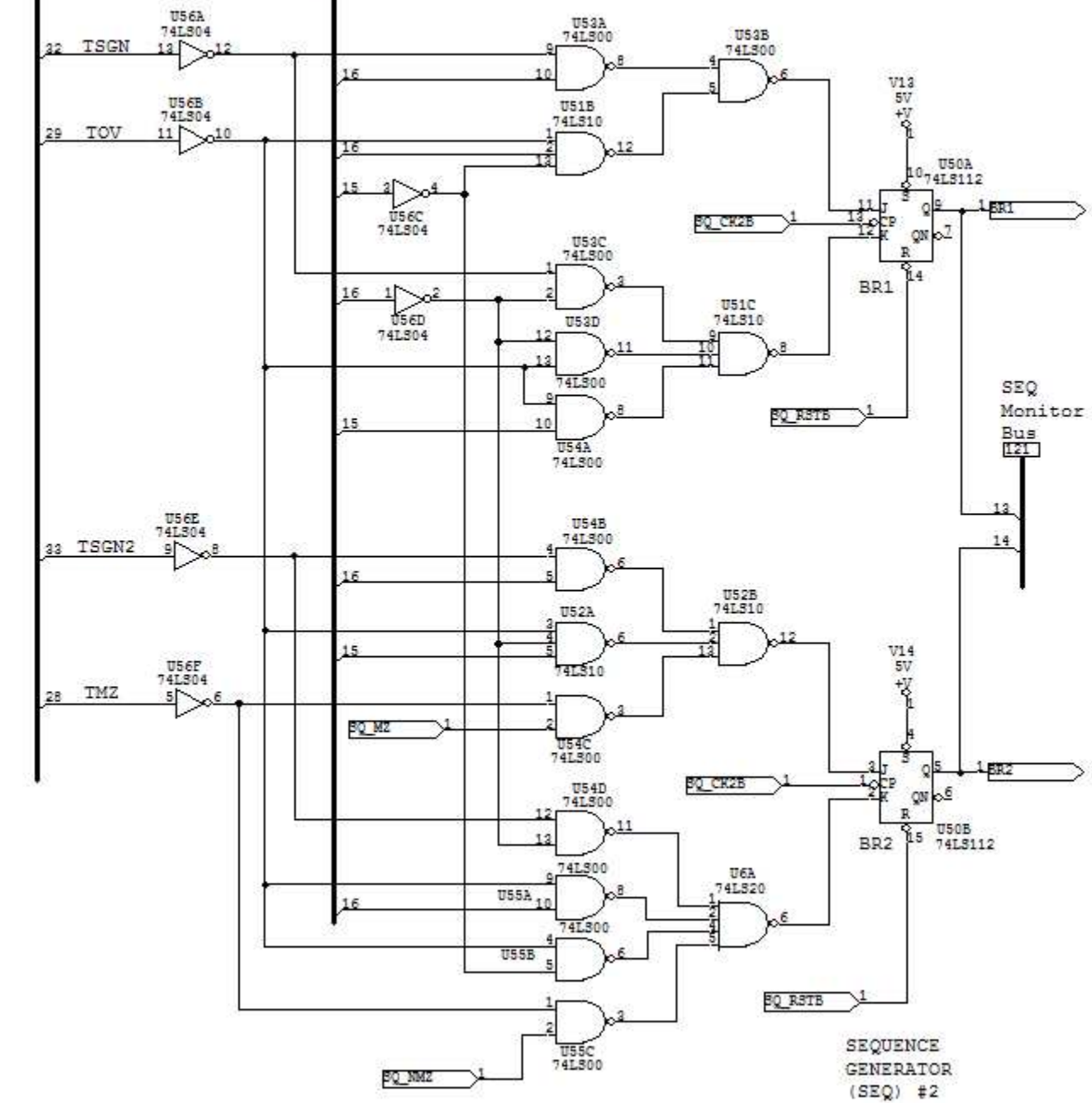

SEQ
Control
Bus

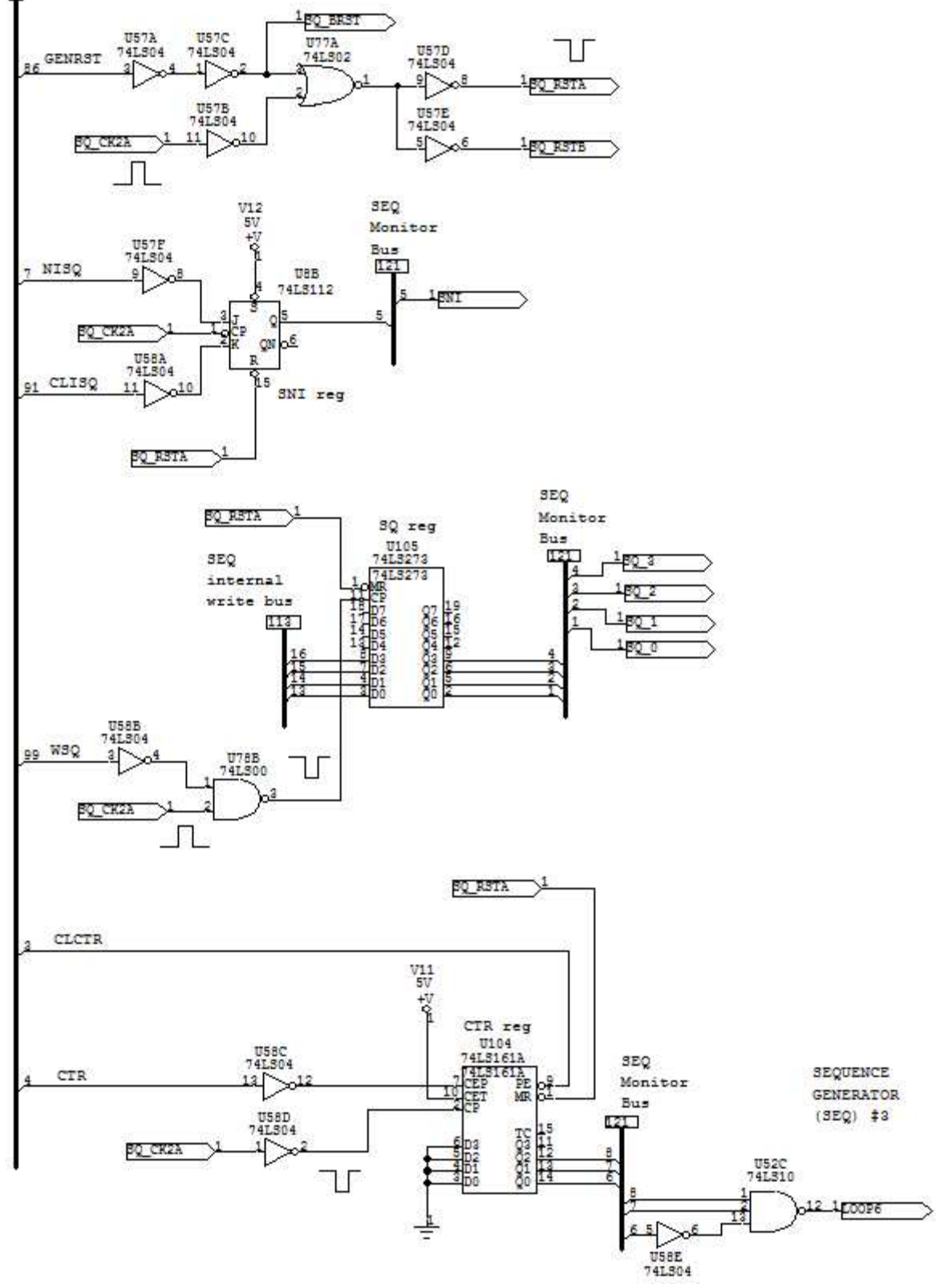

SEQUENCE
GENERATOR
(SEQ) #3

 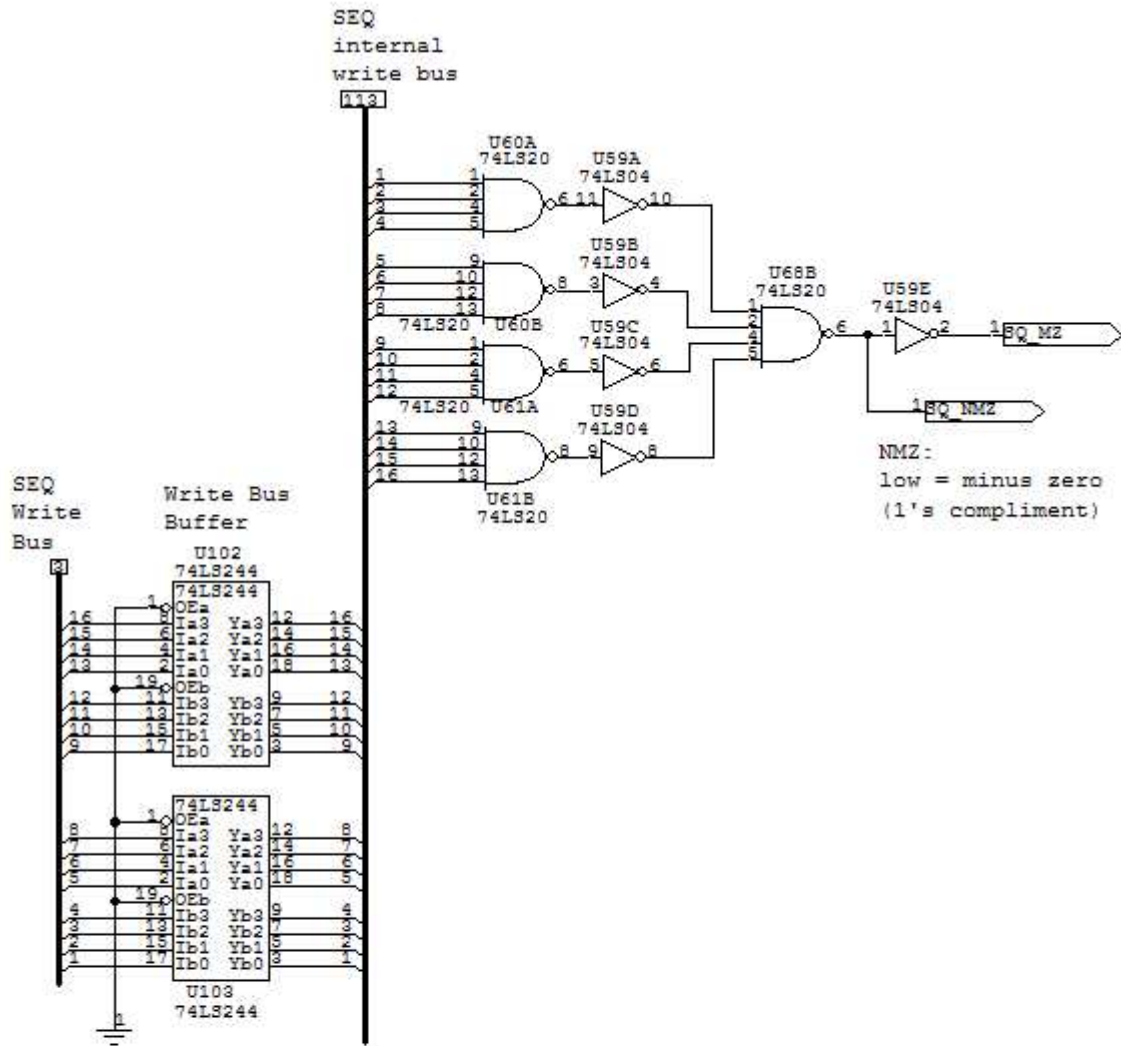

CPM-A (Control Pulse Matrix A)

In this AGC replica, the CPM-A subsequences are implemented in EPROM (they were implemented as a diode matrix in the original). The address into the EPROM is constructed as follows (bit 1 is the LSB):

<u>bit</u>	
13,14	CTR subsequence (2)
9-12:	register SQ (4)
7,8:	register STB (2)
3-6:	register SG (4)
2:	register BR1 (1)
1:	register BR2 (1)

Bits 7-14 (STB, SQ, and CTR) select the instruction subsequence. Bits 1-6 select the control pulses (control logic signals) that are asserted from that subsequence.

SELECTING THE INSTRUCTION SUBSEQUENCE

The 11 AGC instructions, priority counter operations, and interrupt operations are implemented in 22 instruction subsequences. Some instructions (TC) have a single subsequence; others have several subsequences.

The instruction subsequence is chosen by CTR, SQ, and STB. These form bits 7-14 of the CPM-A EPROM address.

CTR (EPROM address bits 13-14)

The CTR signal has 2 lines: SB_02 is the MSB; SB_01 is the LSB. The signal comes from the CTR subsystem in the PROC module. It indicates whether processing needs to be briefly interrupted to insert a PINC or MINC subsequence to increment or decrement a priority counter.

CTR00:	SB_02=0, SB_01=0	no counter; do the next subsequence
CTR01:	SB_02=0, SB_01=1	PINC
CTR10:	SB_02=1, SB_01=0	MINC
CTR11:	SB_02=1, SB_01=1	both; they cancel out, so do the next subsequence

Register SQ (EPROM address bits 9-12)

The 4-bit SQ register holds the currently executing instruction. The code in the SQ register is the same as the op code for these four instructions.

<u>NMEM</u>	<u>SQ REG</u>	<u>OPCODE</u>	<u>USAGE</u>	<u>DESCRIPTION</u>	<u>CYCLES</u>
TC	00	00	TC K	Transfer Control	1 MCT
CCS	01	01	CCS K	Count, Compare, Skip	2 MCT
INDEX	02	02	INDEX K	Index	2 MCT
XCH	03	03	XCH K	Exchange	2 MCT

The SQ register code for these four instructions is the op code + 010 (octal). This happens because all of these instructions have bit 15 set (the sign (SG) bit) while in memory. When

the instruction is copied from memory to the memory buffer register (G) to register B, the SG bit moves from bit 15 to bit 16 and the sign is copied back into bit 15 (US). Therefore, the CS op code (04) becomes (14), and so on.

<u>NMEM</u>	<u>SQ REG</u>	<u>OPCODE</u>	<u>USAGE</u>	<u>DESCRIPTION</u>	<u>CYCLES</u>
CS	014	04	CS K	Clear and Subtract	2 MCT
TS	015	05	TS K	Transfer to Storage	2 MCT
AD	016	06	AD K	Add	2 or 3 MCT
MASK	017	07	MASK K	Bitwise AND	2 MCT

These are the three extended instructions. They are accessed by executing an INDEX 5777 before each instruction. By convention, address 5777 contains 47777. The INDEX instruction adds 47777 to the extended instruction to form the SQ op code. For example, the INDEX adds 4 to the 4 op code for MP to produce the 11 (octal; the addition generates an end-around-carry). SQ register code (the 7777 part is a negative zero).

<u>NMEM</u>	<u>SQ REG</u>	<u>OPCODE</u>	<u>USAGE</u>	<u>DESCRIPTION</u>	<u>CYCLES</u>
MP	011	04	MP K	Multiply	10 MCT
DV	012	05	DV K	Divide	18 MCT
SU	013	06	SU K	Subtract	4 or 5 MCT

STB (EPROM address bits 7-8)

The stage register B (STB) selects the subsequence for a given instruction. Some instructions have multiple subsequences; others (TC) have only one.

The stage register has 2 bits: STB2 is the MSB; STB1 is the LSB. All instructions initially begin with the stage register set to zero. If an instruction needs more than one subsequence, the stage register is incremented to select the next subsequence.

STB00:	STB2=0, STB1=0
STB01:	STB2=0, STB1=1
STB10:	STB2=1, STB1=0
STB11:	STB2=1, STB1=1

INSTRUCTION SUBSEQUENCES

There are 22 instruction subsequences:

TC0	0
CCS0	1
CCS1	2
NDX0	3
NDX1	4
RSM3	5
XCH0	6
CS0	7
TS0	8
AD0	9
MASK0	10
MP0	11
MP1	12

MP3	13
DV0	14
DV1	15
SU0	16
RUPT1	17
RUPT3	18
STD2	19
PINCO	20
MINCO	21

If the CTR signals are 01 (SB_02=0, SB_01=1) the PINC subsequence is selected. If the CTR signals are 10 (SB_02=1, SB_01=0) the MINC subsequence is selected. Otherwise, subsequences for each instruction are selected using the 4-bit SQ register and the 2-bit stage register (STB2, STB1, where STB2 is the MSB). Some instructions (TC) have only one subsequence. At the start of each instruction, the stage counter is initially set to zero. The interrupt call and return sequences are also stored at SQ=00.

	<u>SQ</u>	<u>STB00</u>	<u>STB01</u>	<u>STB10</u>	<u>STB11</u>
TC/RUPT	00:	TC0	RUPT1	STD2	RUPT3
CCS	01:	CCS0	CCS1	----	----
INDEX	02:	NDX0	NDX1	----	RSM3
XCH	03:	XCH0	----	STD2	----
	04:	----	----	----	----
	05:	----	----	----	----
	06:	----	----	----	----
	07:	----	----	----	----
	10:	----	----	----	----
MP	11:	MP0	MP1	----	MP3
DV	12:	DV0	DV1	STD2	----
SU	13:	SU0	----	STD2	----
CS	14:	CS0	----	STD2	----
TS	15:	TS0	----	STD2	----
AD	16:	AD0	----	STD2	----
MASK	17:	MASK0	----	STD2	----

SELECTING THE CONTROL PULSES

Each subsequence consists of 12 steps (TP1 - TP12), with each step asserting up to 5 control pulses (control logic signals). Steps TP1-TP11 are unique to each subsequence; step TP12 is common to all subsequences. Control pulses for TP12 are discussed in CPM-C.

For some steps, selection of the control pulses is also conditional on the state of the 2-bit branch register (BR1 and BR2: BR1 is the MSB and BR2 is the LSB):

BR00	BR1=0, BR2=0
BR01	BR1=0, BR2=1
BR10	BR1=1, BR2=0
BR11	BR1=1, BR2=1

Bits 1-6 of the CPM-A EPROM address is formed as follows:

- 3-6: register SG (4)
- 2: register BR1 (1)
- 1: register BR2 (1)

The column on the far left is the step; columns to the right specify the control pulses that are asserted for that step. Some steps have no control pulses.

subsequence TC0:

TP1	RB	WY	WS	CI	----
TP2					
TP3	WG	----	----	----	----
TP4	RA	WOVI	----	----	----
TP5					
TP6					
TP7	RG	RSC	WB	WP	----
TP8	RZ	WQ	GP	TP	----
TP9	RB	WSC	WG	----	----
TP10	RU	WZ	----	----	----
TP11	NISQ	----	----	----	----

subsequence CCS0:

TP1	RB	WS	----	----	----
TP2	RZ	WY	----	----	----
TP3	WG	----	----	----	----
TP4					
TP5					
TP6	RG	RSC	WB	TSGN	WP
TP7	BR00, RC	TMZ	----	----	----
	BR01, RC	TMZ	----	----	----
	BR10, RB	TMZ	----	----	----
	BR11, RB	TMZ	----	----	----
TP8	BR00, GP	TP	----	----	----
	BR01, R1	WX	GP	TP	----
	BR10, R2	WX	GP	TP	----
	BR11, R1	R2	WX	GP	TP,
TP9	RB	WSC	WG	----	----
TP10	BR00, RC	WA	----	----	----
	BR01, WA	R1C	----	----	----
	BR10, RB	WA	----	----	----
	BR11, WA	R1C	----	----	----
TP11	RU	ST1	WZ	----	----

subsequence CCS1:

TP1	RZ	WY	WS	CI	----
TP2					
TP3	WG	----	----	----	----
TP4	RU	WZ	----	----	----
TP5	RA	WY	CI	----	----
TP6					
TP7	RG	RSC	WB	WP	----
TP8	RU	WB	GP	TP	----

TP9						
TP10	RC	WA	WOVI	----	----	
TP11	RG	RSC	WB	NISQ	----	

subsequence NDX0:

TP1	RB	WS	----	----	----	
TP2						
TP3	WG	----	----	----	----	
TP4	RA	WOVI	----	----	----	
TP5						
TP6						
TP7	RG	RSC	WB	WP	----	
TP8	GP	TP	----	----	----	
TP9	RB	WSC	WG	----	----	
TP10	TRSM	----	----	----	----	
TP11	ST1	----	----	----	----	

subsequence NDX1:

TP1	RZ	WY	WS	CI	----	
TP2						
TP3	WG	----	----	----	----	
TP4	RU	WZ	----	----	----	
TP5						
TP6	RB	WY	----	----	----	
TP7	RG	RSC	WB	WP	----	
TP8	RB	WX	GP	TP	----	
TP9	RB	WSC	WG	----	----	
TP10						
TP11	RU	WB	WOVI	NISQ	----	

subsequence RSM3:

TP1	R24	WS	----	----	----	
TP2						
TP3	WG	----	----	----	----	
TP4						
TP5						
TP6						
TP7	RG	WZ	----	----	----	
TP8						
TP9						
TP10						
TP11	NISQ	----	----	----	----	

subsequence XCH0:

TP1	RB	WS	----	----	----	
TP2	RA	WP	----	----	----	
TP3	WG	----	----	----	----	
TP4	WP2	----	----	----	----	
TP5						
TP6						

TP7	RG	RSC	WB	WP,	----
TP8	GP	TP	----	----	----
TP9	RA	WSC	WG	RP2	----
TP10	RB	WA	WOVI	----	----
TP11	ST2	----	----	----	----

subsequence CS0:

TP1	RB	WS	----	----	----
TP2					
TP3	WG	----	----	----	----
TP4					
TP5					
TP6					
TP7	RG	RSC	WB	WP,	----
TP8	GP	TP	----	----	----
TP9	RB	WSC	WG	----	----
TP10	RC	WA	WOVI	----	----
TP11	ST2	----	----	----	----

subsequence TS0:

TP1	RB	WS	----	----	----
TP2	RA	WB	TOV	WP	----
TP3	WG	----	----	----	----
TP4	BR00,	----	----	----	----
	BR01, RZ	WY	CI	----	----
	BR10, RZ	WY	CI	----	----
	BR11,	----	----	----	----
TP5	BR00,	----	----	----	----
	BR01, R1	WA	----	----	----
	BR10, WA	R1C	----	----	----
	BR11,	----	----	----	----
TP6					
TP7	BR00,	----	----	----	----
	BR01, RU	WZ	----	----	----
	BR10, RU	WZ	----	----	----
	BR11,	----	----	----	----
TP8	GP	----	----	----	----
TP9	RB	WSC	WG	----	----
TP10	RA	WOVI	----	----	----
TP11	ST2	----	----	----	----

(overflow)
(underflow)

subsequence AD0:

TP1	RB	WS	----	----	----
TP2	RA	WY	----	----	----
TP3	WG	----	----	----	----
TP4					
TP5					
TP6					
TP7	RG	RSC	WB	WP	----
TP8	RB	WX	GP	TP	----
TP9	RB	WSC	WG	----	----
TP10					

TP11 RU WA WOVC ST2 WOVI

SUB_MASK0 performs a logical AND using DeMorgan's Theorem: the inputs are inverted, a logical OR is performed, and the result is inverted. The implementation of the OR (at TP8) is somewhat unorthodox: the inverted inputs are in registers U and C. The OR is achieved by gating both registers onto the read/write bus simultaneously. (The bus only transfers logical 1's; register-to-register transfers are performed by clearing the destination register and then transferring the 1's from the source register to the destination). When the 1's from both registers are simultaneously gated onto the bus, the word on the bus is a logical OR of both registers.

subsequence MASK0:

TP1	RB	WS	----	----	----
TP2	RA	WB	----	----	----
TP3	WG	----	----	----	----
TP4	RC	WY	----	----	----
TP5					
TP6					
TP7	RG	RSC	WB	WP	----
TP8	RU	RC	WA	GP	TP
TP9					
TP10	RA	WB	----	----	----
TP11	RC	WA	ST2	WOVI	----

subsequence MPO:

TP1	RB	WS	----	----	----
TP2	RA	WB	TSGN	----	----
TP3	RSC	WG	----	----	----
TP4	BR00, RB	WLP	----	----	----
	BR01, RB	WLP	----	----	----
	BR10, RC	WLP	----	----	----
	BR11, RC	WLP	----	----	----
TP5	RLP	WA	----	----	----
TP6					
TP7	BR00, RG	WY	WP	----	----
	BR01, RG	WY	WP	----	----
	BR10, RG	WB	WP	----	----
	BR11, RG	WB	WP	----	----
TP8	BR00, GP	TP	----	----	----
	BR01, GP	TP	----	----	----
	BR10, RC	WY	GP	TP	----
	BR11, RC	WY	GP	TP	----
TP9	RU	WB	TSGN2	----	----
TP10	BR00, RA	WLP	TSGN	----	----
	BR01, RA	RB14	WLP	TSGN	----
	BR10, RA	WLP	TSGN	----	----
	BR11, RA	RB14	WLP	TSGN	----
TP11	BR00, ST1	WALP	----	----	----
	BR01, R1	ST1	WALP	R1C	----
	BR10, RU	ST1	WALP	----	----
	BR11, RU	ST1	WALP	----	----

subsequence MP1:

TP1	RA	WY	----	----	----
TP2	RLP	WA	TSGN	----	----
TP3	BR00, ----	----	----	----	----
	BR01, ----	----	----	----	----
	BR10, RB	WX	----	----	----
	BR11, RB	WX	----	----	----
TP4	RA	WLP	----	----	----
TP5	RLP	TSGN	----	----	----
TP6	RU	WALP	----	----	----
TP7	RA	WY	----	----	----
TP8	BR00, ----	----	----	----	----
	BR01, ----	----	----	----	----
	BR10, RB	WX	----	----	----
	BR11, RB	WX	----	----	----
TP9	RLP	WA	----	----	----
TP10	RA	WLP	CTR	----	----
TP11	RU	ST1	WALP	----	----

subsequence MP3:

TP1	RZ	WY	WS	CI	----
TP2	RLP	TSGN	----	----	----
TP3	WG	----	----	----	----
TP4	RU	WZ	----	----	----
TP5	RA	WY	----	----	----
TP6	BR00, ----	----	----	----	----
	BR01, ----	----	----	----	----
	BR10, RB	WX	----	----	----
	BR11, RB	WX	----	----	----
TP7	RG	RSC	WB	WP	----
TP8	RLP	WA	GP	TP	----
TP9	RB	WSC	WG	----	----
TP10	RA	WLP	----	----	----
TP11	RU	WALP	NISQ	----	----

subsequence DV0:

TP1	RB	WS	----	----	----
TP2	RA	WB	TSGN	----	----
TP3	RSC	WG	----	----	----
TP4	BR00, RC	WA	----	----	----
	BR01, RC	WA	----	----	----
	BR10, ----	----	----	----	----
	BR11, ----	----	----	----	----
TP5	BR00, R1	WLP	----	----	----
	BR01, R1	WLP	----	----	----
	BR10, R2	WLP	----	----	----
	BR11, R2	WLP	----	----	----
TP6	RA	WQ	----	----	----
TP7	RG	WB	TSGN	WP	----
TP8	RB	WA	GP	TP	----
TP9	BR00, RLP	R2	WB	----	----

	BR01, RLP	R2	WB	----	----
	BR10, ----	----	----	----	----
	BR11, ----	----	----	----	----
TP10	BR00, RB	WLP	----	----	----
	BR01, RB	WLP	----	----	----
	BR10, RC	WA	----	----	----
	BR11, RC	WA	----	----	----
TP11	R1	ST1	WB	----	----

subsequence DV1:

TP1	R22	WS	----	----	----
TP2	RQ	WG	----	----	----
TP3	RG	WQ	WY	RSB	----
TP4	RA	WX	----	----	----
TP5	RLP	TSGN2	----	----	----
TP6					
TP7	RU	TSGN	----	----	----
TP8	BR00, ----	----	----	----	----
	BR01, ----	----	----	----	----
	BR10, RU	WQ	----	----	----
	BR11, RU	WQ	----	----	----
TP9	BR00, RB	RSB	WG	----	----
	BR01, RB	RSB	WG	----	----
	BR10, RB	WG	----	----	----
	BR11, RB	WG	----	----	----
TP10	RG	WB	TSGN	----	----
TP11	BR00, ST1	----	----	----	----
	BR01, ST1	----	----	----	----
	BR10, RC	WA	ST2	----	----
	BR11, RB	WA	ST2	----	----

subsequence SU0:

TP1	RB	WS	----	----	----
TP2	RA	WY	----	----	----
TP3	WG	----	----	----	----
TP4					
TP5					
TP6					
TP7	RG	RSC	WB	WP	----
TP8	RC	WX	GP	TP	----
TP9	RB	WSC	WG	----	----
TP10					
TP11	RU	WA	WOVC	ST2	WOVI

subsequence RUPT1:

TP1	R24	WY	WS	CI,	----
TP2					
TP3	WG	----	----	----	----
TP4					
TP5					
TP6					

TP7					
TP8					
TP9	RZ	WG	----	----	----
TP10	RU	WZ	----	----	----
TP11	ST1	ST2	----	----	----

subsequence RUPT3:

TP1	RZ	WS	----	----	----
TP2	RRPA	WZ	----	----	----
TP3	RZ	KRPT	WG	----	----
TP4					
TP5					
TP6					
TP7					
TP8					
TP9	RB	WSC	WG	----	----
TP10					
TP11	ST2	----	----	----	----

subsequence STD2:

TP1	RZ	WY	WS	CI,	----
TP2					
TP3	WG	----	----	----	----
TP4	RU	WZ	----	----	----
TP5					
TP6					
TP7	RG	RSC	WB	WP	----
TP8	GP	TP	----	----	----
TP9	RB	WSC	WG	----	----
TP10					
TP11	NISQ	----	----	----	----

subsequence PINC:



TP1	WS	RSCT	----	----	----
TP2					
TP3	WG	----	----	----	----
TP4	R1	WY	----	----	----
TP5					
TP6	RG	WX	WP	----	----
TP7	TP	----	----	----	----
TP8	WP	----	----	----	----
TP9	RU	CLG	WPx	----	----
TP10	RU	WGx	WOVR	----	----
TP11					

subsequence MINC:

TP1	WS,	RSCT	----	----	----
TP2					
TP3	WG	----	----	----	----
TP4	WY	R1C	----	----	----

TP5					
TP6	RG	WX	WP	----	----
TP7	TP	----	----	----	----
TP8	WP	----	----	----	----
TP9	RU	CLG	WPx	----	----
TP10	RU	WGx	WOVR	----	----
TP11					

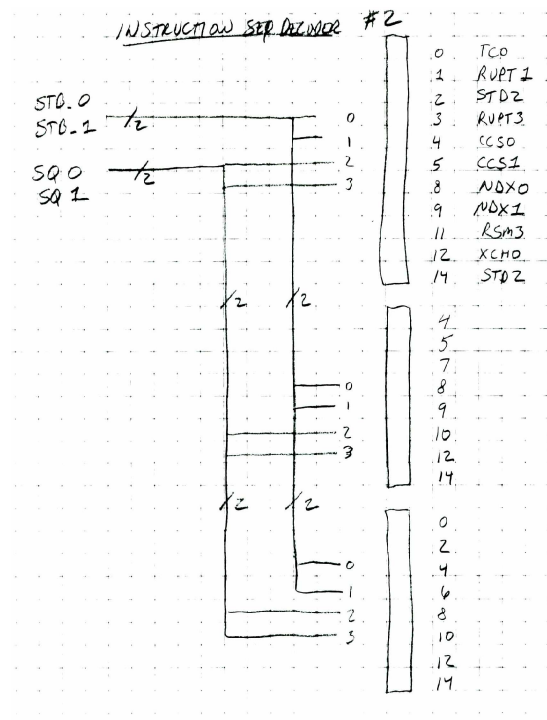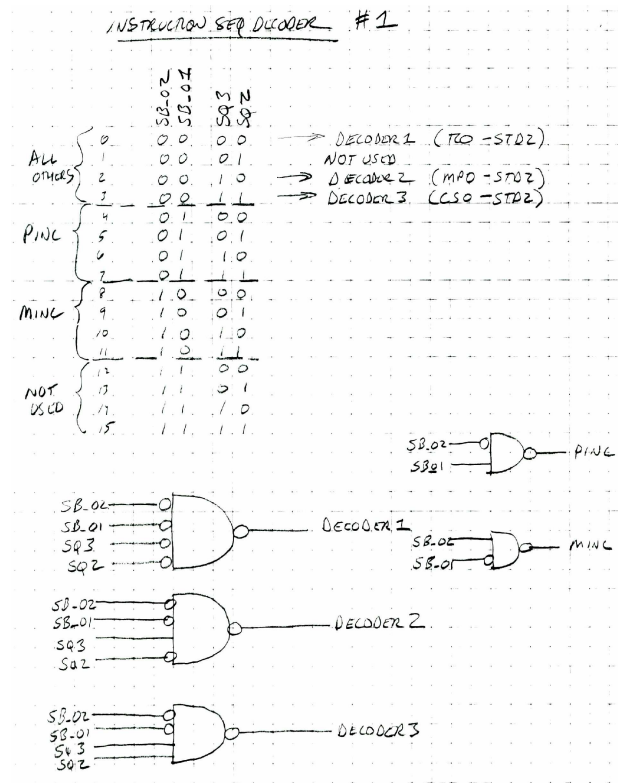Here's some of the analysis used to develop the instruction sequence decoder. This decoder takes in the STB and SQ inputs and decodes the instruction sequence for display to the operator.



CONTROL SIGNAL DEFINITIONS

<u>SIGNAL</u>	<u>#</u>	<u>DESCRIPTION</u>
CI	1	Carry in
CLG	2	Clear G
CLCTR	3	Clear loop counter
CTR	4	Loop counter
GP	5	Generate Parity
KRPT	6	Knock down Rupt priority
NISQ	7	New instruction to the SQ register
RA	8	Read A
RB	9	Read B
RB14	10	Read bit 14
RC	11	Read C
RG	12	Read G
RLP	13	Read LP
RP2	14	Read parity 2
RQ	15	Read Q
RRPA	16	Read RUPT address
RSB	17	Read sign bit
RSCT	18	Read selected counter address
RU	19	Read sum
RZ	20	Read Z
R1	21	Read 1
R1C	22	Read 1 complimented
R2	23	Read 2
R22	24	Read 22
R24	25	Read 24
ST1	26	Stage 1
ST2	27	Stage 2
TMZ	28	Test for minus zero
TOV	29	Test for overflow
TP	30	Test parity
TRSM	31	Test for resume
TSGN	32	Test sign
TSGN2	33	Test sign 2
WA	34	Write A
WALP	35	Write A and LP
WB	36	Write B
Wgx	37	Write G (do not reset)
WLP	38	Write LP
WOVC	39	Write overflow counter
WOVI	40	Write overflow RUPT inhibit
WOVR	41	Write overflow
WP	42	Write P
Wpx	43	Write P (do not reset)
WP2	44	Write P2
WQ	45	Write Q
WS	46	Write S
WX	47	Write X
WY	48	Write Y
Wyx	49	Write Y (do not reset)

WZ 50 Write Z

Control signal outputs from CPM-A used as inputs to CPM-B only (not used outside of CPM):


<u>SIGNAL</u>	<u>#</u>	<u>DESCRIPTION</u>
RSC	51	Read special and central (output to B only, not outside CPM)
WSC	52	Write special and central (output to B only, not outside CPM)
WG	53	Write G (output to B only, not outside CPM)

Control signal outputs from CPM-A used as inputs to CPM-C only (not used outside of CPM):

<u>SIGNAL</u>	<u>#</u>	<u>DESCRIPTION</u>
SDV1	54	Subsequence DV1 is currently active
SMP1	55	Subsequence MP1 is currently active
SRSM3	56	Subsequence RSM3 is currently active

CPM-A INPUTS:

<u>I/F</u>	<u>signal</u>	<u>full name</u>	<u>state definition</u>	
TPG:	TPG_Q3	TPG STATE	where Q3 is MSB, Q0 is LSB:	
	TPG_Q2		00 = STBY	
	TPG_Q1		01 = PWRON	
	TPG_Q0		02 = TP1	
			03 = TP2	
			04 = TP3	
			05 = TP4	
			06 = TP5	
			07 = TP6	
			08 = TP7	
			09 = TP8	
			10 = TP9	
			11 = TP10	
			12 = TP11	
			13 = TP12	
		14 = SRLSE		
		15 = WAIT		
SEQ:	BR1	BRANCH REG 1	BR1 is MSB, BR2 is LSB BR00=0:BR1=0, BR2=0 BR01=1:BR1=0, BR2=1 BR10=2:BR1=1, BR2=0 BR11=3:BR1=1, BR2=1	
	BR2	BRANCH REG 2		
	SQ_3	INST REG		
	SQ_2			
	SQ_1			
	SQ_0		where SQ_3 is MSB, SQ_0 is LSB	
	STB_1	STAGE REG	where STB_1 is MSB, STB_0 is LSB	
	STB_0			
	LOOP6	LOOPCNTR EQ 6	0=LOOPCNTR is holding the number 6.	
	SNI	SELECT NEXT INST	1=select next instruction (SNI register)	
	CTR:	SB_01	SUB SEL 01	SB_01 is LSB; SB_02 is MSB 00=no counter; 01=PINC; 10=MINC
		SB_02	SUB SEL 02	
	INT:			

 

IRQ	INT RQST	0=interrupt requested.
MON:		
NRUN	RUN/HALT	0=run, 1=step

CPM-A OUTPUTS:

<u>signal</u>	<u>full name</u>	<u>state definition</u>
CI	SET CARRY IN	0=Carry in
CLG	CLR G	0=Clear G
CLCTR	CLR LOOP CTR	0=Clear loop counter
CTR	INCR LOOP CTR	0=Loop counter
GP	GEN PARITY	0=Generate Parity
KRPT	KNOCK DOWN RUPT	0=Knock down Rupt priority
NISQ	NEW INSTRUCT	0=New instruction to the SQ reg
RA	READ A	0=Read A
RB	READ B	0=Read B
RB14	READ BIT 14	0=Read bit 14
RC	READ C	0=Read C
RG	READ G	0=Read G
RLP	READ LP	0=Read LP
RP2	READ PARITY 2	0=Read parity 2
RQ	READ Q	0=Read Q
RRPA	READ RUPT ADDR	0=Read RUPT address
RSB	READ SIGN	0=Read sign bit
RSCT	READ CNTR ADDR	0=Read selected counter address
RU	READ U	0=Read sum
RZ	READ Z	0=Read Z
R1	READ 1	0=Read 1
R1C	READ 1 COMP	0=Read 1 complimented
R2	READ 2	0=Read 2
R22	READ 22	0=Read 22
R24	READ 24	0=Read 24
ST1	SET STAGE 1	0=Stage 1
ST2	SET STAGE 2	0=Stage 2
TMZ	TEST MINUS ZERO	0=Test for minus zero
TOV	TEST OVF	0=Test for overflow
TP	TEST PARITY	0=Test parity
TRSM	TEST RESUME	0=Test for resume
TSGN	TEST SIGN	0=Test sign
TSGN2	TEST SIGN 2	0=Test sign 2
WA	WRITE A	0=Write A
WALP	WRITE A/LP	0=Write A and LP
WB	WRITE B	0=Write B
WGx	WRITE G NO RESET	0=Write G (do not reset)
WLP	WRITE LP	0=Write LP
WOVC	WRITE OVF CNTR	0=Write overflow counter
WOVI	WRITE OVF RUPT INH	0=Write overflow RUPT inhibit
WOVR	WRITE OVF	0=Write overflow
WP	WRITE P	0=Write P
WPx	WRITE P NO RESET	0=Write P (do not reset)
WP2	WRITE P2	0=Write P2


WQ	WRITE Q	0=Write Q
WS	WRITE S	0=Write S
WX	WRITE X	0=Write X
WY	WRITE Y	0=Write Y
WYx	WRITE Y NO RESET	0=Write Y (do not reset)
WZ	WRITE Z	0=Write Z

OUTPUTS TO CPM-B ONLY; NOT USED OUTSIDE CPM


RSC	READ SPECIAL REG	0=Read special and central
WSC	WRITE SPECIAL REG	0=Write special and central
WG	WRITE G	0=Write G

OUTPUTS TO CPM-C ONLY; NOT USED OUTSIDE CPM

SDV1	SUBSEQ DV1	0=Subsequence DV1 is selected
SMP1	SUBSEQ MP1	0=Subsequence MP1 is selected
SRSM3	SUBSEQ RSM3	0=Subsequence RSM3 is selected

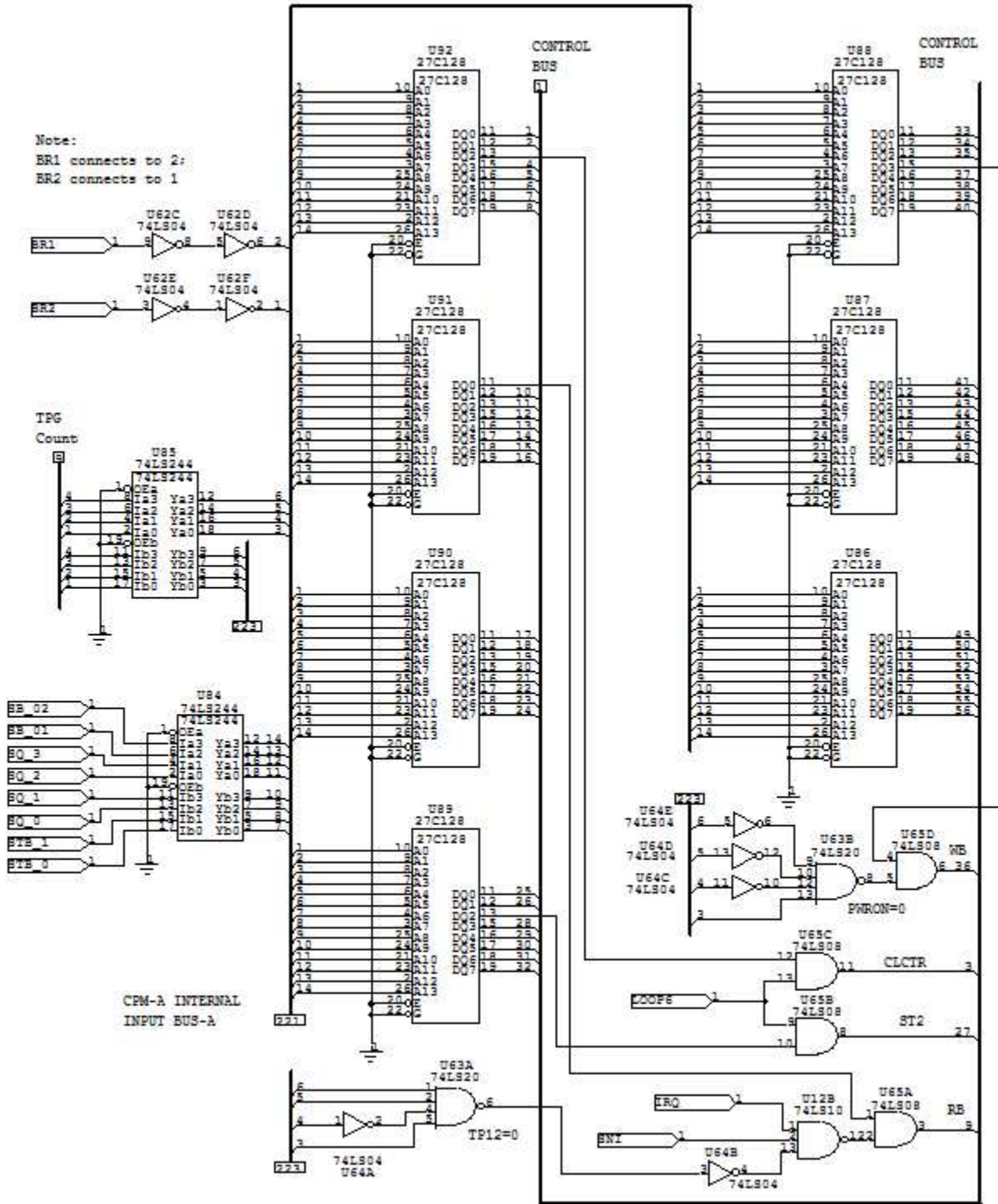

CONTROL PULSE MATRIX A
(CPM-A) #1

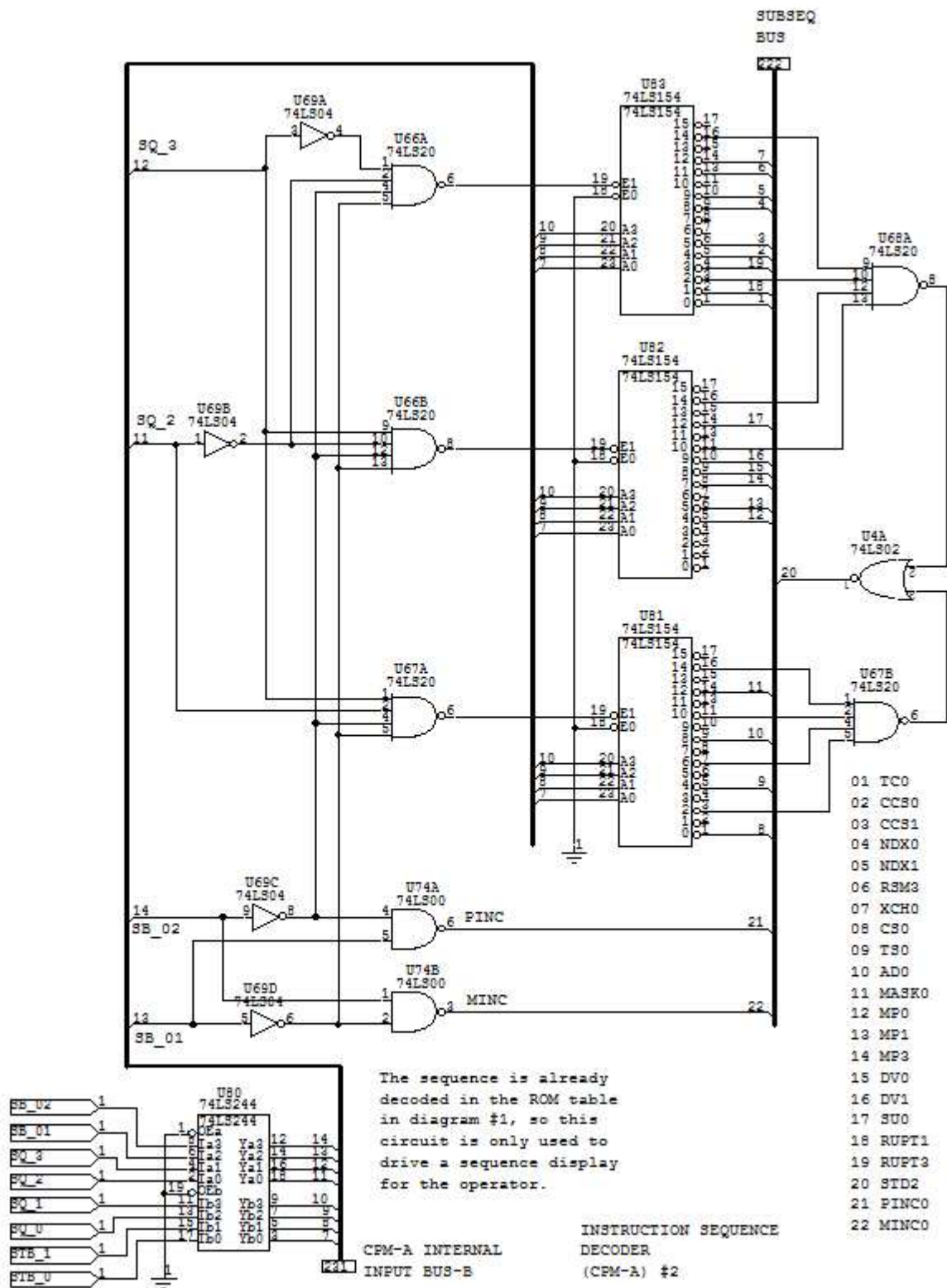

CPM-B (Control Pulse Matrix B)

Some AGC registers are mapped onto low memory addresses (00 - 17 octal), so reading or writing to those addresses causes data to be read from, or written into, flip-flop registers instead of memory. These addresses include the central registers (A, Q, Z, LP), the bank register (BNK), and I/O registers.

Addresses 16 and 17 are used in conjunction with the INDEX instruction to inhibit or enable interrupts; this is a trick used to extend the instruction set; to cram more instructions into a 3-bit op code.

The addresses from 20-23 are in erasable memory, but any data written into those addresses is rotated or shifted. This is implemented through the G register in the MEM module.

Addresses 24-27 are reserved for saving the central register before servicing an interrupt. Registers Z and B are automatically saved by the interrupt subsequence. Registers A and Q must be saved by the interrupt service routine.

SPECIAL REGISTERS

These addresses called special registers. All numbers are in octal.

addr	Flip-Flop registers
00	A register (accumulator)
01	Q register
02	Z register (program counter)
03	LP register
04	IN0 input register 0
05	IN1 input register 1
06	IN2 input register 2
07	IN3 input register 3
10	OUT0 output register 0
11	OUT1 output register 1
12	OUT2 output register 2
13	OUT3 output register 3
14	OUT4 output register 4
15	BANK bank register
16	RELINT
17	INHINT
	Erasable memory registers
20	CYR cycle right
21	SR shift right
22	CYL cycle left
23	SL shift left
24	ZRUPT save register Z
25	BRUPT save register B
26	ARUPT save register A
27	QRUPT save register Q

CPM-B translates the WG, RSC, and WSC signals generated by SUBSYSTEM A into signals that read from or write to these registers. The logic is given below (all numbers are in octal):

if WG is asserted from CPM-A,

...and the address bus = 020:	assert:W20
...and the address bus = 021:	assert:W21
...and the address bus = 022:	assert:W22
...and the address bus = 023:	assert:W23

...otherwise, if the address bus > 17: assert:WGn (not a central register)

if RSC is asserted from CPM-A

...and the address bus = 00:	assert:RA0
...and the address bus = 01:	assert:RA1
...and the address bus = 02:	assert:RA2
...and the address bus = 03:	assert:RA3
...and the address bus = 04:	assert:RA4
...and the address bus = 05:	assert:RA5
...and the address bus = 06:	assert:RA6
...and the address bus = 07:	assert:RA7
...and the address bus = 010:	assert:RA10
...and the address bus = 011:	assert:RA11
...and the address bus = 012:	assert:RA12
...and the address bus = 013:	assert:RA13
...and the address bus = 014:	assert:RA14
...and the address bus = 015:	assert:RBK
...and the address bus = 016:	do nothing
...and the address bus = 017:	do nothing

if WSC is asserted from CPM-A,

...and the address bus = 00:	assert:WA0
...and the address bus = 01:	assert:WA1
...and the address bus = 02:	assert:WA2
...and the address bus = 03:	assert:WA3
...and the address bus = 010:	assert:WA10
...and the address bus = 011:	assert:WA11
...and the address bus = 012:	assert:WA12
...and the address bus = 013:	assert:WA13
...and the address bus = 014:	assert:WA14
...and the address bus = 015:	assert:WBK
...and the address bus = 016:	do nothing
...and the address bus = 017:	do nothing

Here's a table I developed to work out the relationships between addresses and CPM-B logic signals:

CPM-B				IF ASSERTED:			
		GTR17	GTR27	ADR	WCG	RSC	WSC
A	00	1	1	00	N/A	RA0	WA0
Q	01	1	1	01		RA1	WA1
	02	1	1	02		RA2	WA2
LP	03	1	1	03		RA3	WA3
	04	1	1	04		RA4	N/A
	05	1	1	05		RA5	
	06	1	1	06		RA6	
	07	1	1	07		RA7	
	10	1	1	10		RA10	WA10
	11	1	1	11		RA11	WA11
	12	1	1	12		RA12	WA12
	13	1	1	13		RA13	WA13
	14	1	1	14		RA14	WA14
	15	1	1	15		RBK	WBK
	16	1	1	16		N/A	N/A
	17	1	1	17			
	20	0	1	00	W20		
	21	0	1	01	W21		
	22	0	1	02	W22		
	23	0	1	03	W23		
	24	0	1	04	W24		
	25	0	1	05	W25		
	26	0	1	06			
	27	0	1	07			
	30	0	0	10			
	31	0	0	11			
	32	0	0	12			
	33	0	0	13			
	34	0	0	14			
	35	0	0	15			
	36	0	0	16			
	37	0	0	17			
	40	0	0	00			
	41	0	0	01			


CPM-B
 N/A = NO CONTROL SIGNALS ASSERTED

CPM-B CONTROL SIGNALS

<u>SIGNAL</u>	<u>#</u>	<u>DESCRIPTION</u>
RA0	57	Read register at address 0 (A)
RA1	58	Read register at address 1 (Q)
RA2	59	Read register at address 2 (Z)
RA3	60	Read register at address 3 (LP)
RA4	61	Read register at address 4
RA5	62	Read register at address 5
RA6	63	Read register at address 6
RA7	64	Read register at address 7
RA10	65	Read register at address 10 (octal)
RA11	66	Read register at address 11 (octal)
RA12	67	Read register at address 12 (octal)
RA13	68	Read register at address 13 (octal)
RA14	69	Read register at address 14 (octal)
RBK	70	Read BNK
WA0	71	Write register at address 0 (A)
WA1	72	Write register at address 1 (Q)
WA2	73	Write register at address 2 (Z)
WA3	74	Write register at address 3 (LP)
WA10	75	Write register at address 10 (octal)
WA11	76	Write register at address 11 (octal)
WA12	77	Write register at address 12 (octal)
WA13	78	Write register at address 13 (octal)
WA14	79	Write register at address 14 (octal)
WBK	80	Write BNK
WGn	81	Write G (normal gates)
W20	82	Write into CYR
W21	83	Write into SR
W22	84	Write into CYL
W23	85	Write into SL

CPM-B INPUTS:


<u>I/F</u>	<u>signal</u>	<u>full name</u>	<u>state definition</u>
CPM-A			
	RSC	READ SPECIAL REG	0=Read special and central
	WSC	WRITE SPECIAL REG	0=Write special and central
	WG	WRITE G	0=Write G
ADR:			
	AD_4	ADDRESS	AD_4=MSB, AD_1=LSB: (low-order bits of 14-bit address)
	AD_3		
	AD_2		
	AD_1		
	GTR_17	ADDRESS > 017	0=CADR in register S > 017
	GTR_27	ADDRESS > 027	0=CADR in register S > 027

 

CPM-B OUTPUTS:

<u>I/F</u>	<u>signal</u>	<u>full name</u>	<u>state definition</u>
	RA0	READ ADDR 0 (A)	0=Read reg at address 0
	RA1	READ ADDR 1	0=Read reg at address 1 (Q)
	RA2	READ ADDR 2	0=Read reg at address 2 (Z)
	RA3	READ ADDR 3	0=Read reg at address 3 (LP)
	RA4	READ ADDR 4	0=Read reg at address 4
	RA5	READ ADDR 5	0=Read reg at address 5
	RA6	READ ADDR 6	0=Read reg at address 6
	RA7	READ ADDR 7	0=Read reg at address 7
	RA10	READ ADDR 10	0=Read reg at address 10 (octal)
	RA11	READ ADDR 11	0=Read reg at address 11 (octal)
	RA12	READ ADDR 12	0=Read reg at address 12 (octal)
	RA13	READ ADDR 13	0=Read reg at address 13 (octal)
	RA14	READ ADDR 14	0=Read reg at address 14 (octal)
	RBK	READ BNK	0=Read BNK reg
	WA0	WRITE ADDR 0	0=Write reg at address 0 (A)
	WA1	WRITE ADDR 1	0=Write reg at address 1 (Q)
	WA2	WRITE ADDR 2	0=Write reg at address 2 (Z)
	WA3	WRITE ADDR 3	0=Write reg at address 3 (LP)
	WA10	WRITE ADDR 10	0=Write reg at address 10 (octal)
	WA11	WRITE ADDR 11	0=Write reg at address 11 (octal)
	WA12	WRITE ADDR 12	0=Write reg at address 12 (octal)
	WA13	WRITE ADDR 13	0=Write reg at address 13 (octal)
	WA14	WRITE ADDR 14	0=Write reg at address 14 (octal)
	WBK	WRITE BNK	0=Write BNK reg

WGn	WRITE G NORMAL	0=Write G (normal gates)
W20	WRITE ADDR 20	0=Write into CYR
W21	WRITE ADDR 21	0=Write into SR
W22	WRITE ADDR 22	0=Write into CYL
W23	WRITE ADDR 23	0=Write into SL

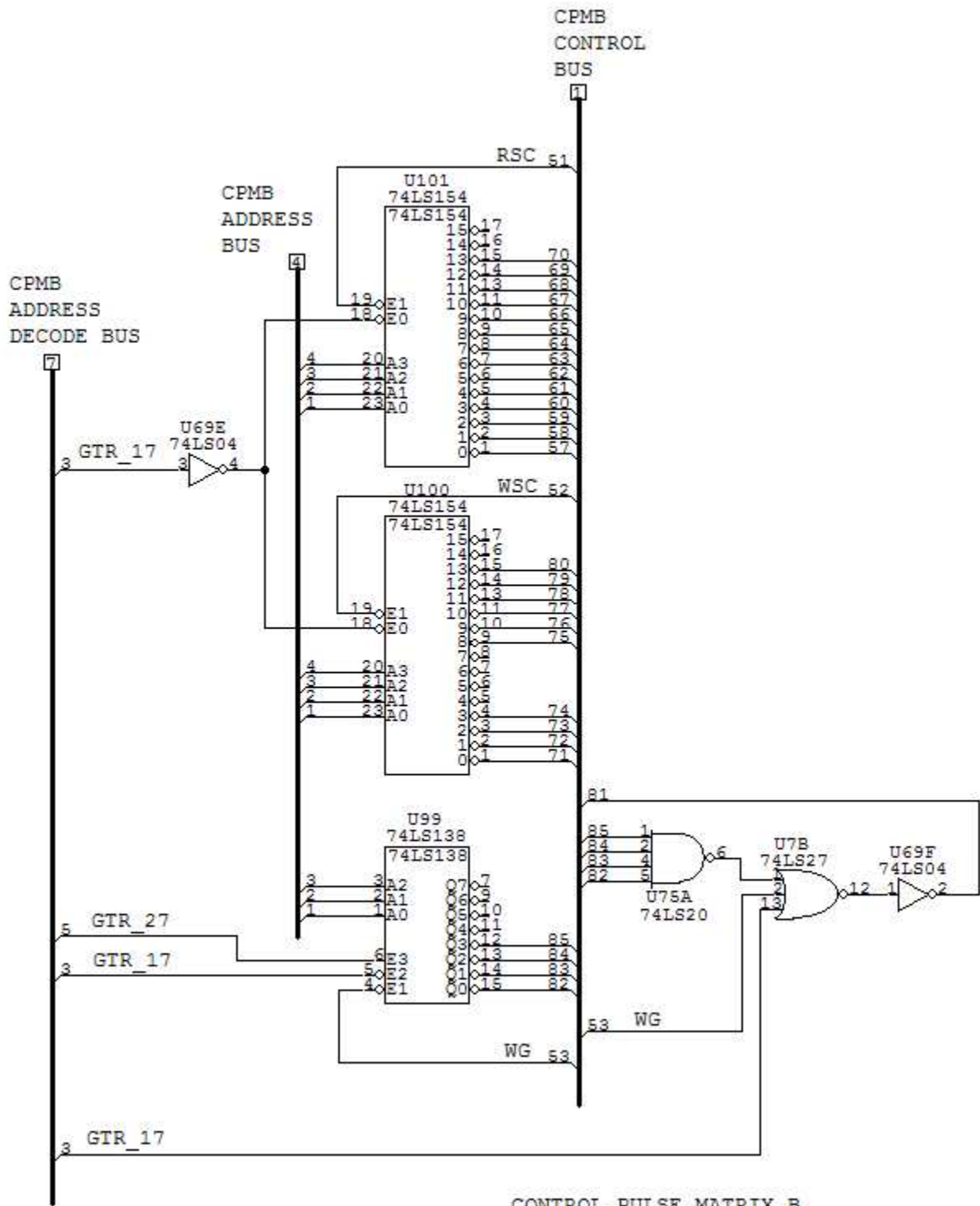

CONTROL PULSE MATRIX B
(CPM-B) #1

CPM-C (Control Pulse Matrix C)

The CPM-C subsystem issues control signals for the memory cycle, selecting the next instruction, and performing priority counter subsequences. These signals are issued at specific points in the 12-step cycle of the time pulse generator (TPG).

STBY:	assert:GENRST	Resets various AGC registers.
PWRON:	assert:R2000	Put the starting address on the read bus. CPM-A asserts:WB, which copies the data into register B, which is the prefetch register for the next instruction. Since the opcode for a branch is 0, the instruction in B becomes TC 2000, which is the first instruction always executed by the AGC.
TP1:	assert:CLISQ	SNI < - 0. Moved from TP12 to TP1 because CLISQ was getting cleared in this hardware AGC replica before TPG was clocked; therefore TPG was not seeing the SNI indication.
TP5:	if: the address bus > 17 and the address bus < 2000 and SDV1 or SMP1 are not asserted then: assert:SBWG	(not a central register) (not fixed memory; must be erasable) (not a loop counter subsequence) read erasable memory into G by TP6
	if: the address bus = 17 then: assert:INH	INHINT instruction (INDEX 017)
	if: the address bus = 16 then: assert:CLINH	RELINT instruction (INDEX 016)
TP6:	if: the address bus > 1777 and SDV1 or SMP1 are not asserted then: assert:SBWG	(not erasable memory) (not a loop counter subsequence) read fixed memory into G register by TP7
TP11:	if: the address bus > 17 and the address bus < 2000 and SDV1 or SMP1 are not asserted then: assert:WE	(not a central register) (not fixed memory; must be erasable) (not a loop counter subsequence) G register written to memory beginning at TP11; Memory updates are in G by TP10 for all normal and extracode instructions, but the PINC and MINC sequences write to G in TP10 because they need to update the parity bit.
	if: SRSM3 is asserted then: assert:CLRP	Additional interrupts are inhibited during servicing of an interrupt; Remove the inhibition when RESUME is executed (INDEX 025)

TP12: assert:WPCTR

```
if:    the SNI register = 1
then:
  if:    IRQ is asserted
  then:
    assert:RPT
    assert:SETSTB
  else:
    assert:CLSTB

endif
assert:WSQ
assert:CLSTA

assert:CLINH1

else:
  if:    CTR00 or CTR11

  then:
    assert:WSTB
    assert:CLSTA
```

Check the priority counters; service any waiting inputs on the next memory cycle.

(if SNI is set, get next instruction)

(if interrupt requested (see CPM-A for similar assertion))

Read the interrupt vector.

STB <- 1. Will cause the RUPT1 subsequence to execute.

(not an interrupt; a normal instruction)

STB <- 0. The CPM-A will assert RB here, which, when accompanied by WSQ (below), will read the next instruction from register B onto the bus. WSQ will write it into SQ.

Write the next instruction (on the write bus) into the SQ register.

Clear STA register.

Clear INHINT1. Removes inhibition of interrupts (if they were) AFTER the next instruction

(not a new instruction)

if previous sequence was not a PINC or MINC, get next subsequence for same instruction. if the previous sequence was PINC or MINC, we already have the subsequence, but it was interrupted by the counter.


Copy STB <- STA. Gets next sequence for same instruction.

STA <- 0


This truth table shows the logic needed at TP12 to produce the RPT, SETSTB, CLSTB, CLSTA, WSQ, WSTB, CLISQ, and CLINH1 signals, given the SNI, IRQ, NRUN, and SB inputs.

INPUTS				OUTPUTS						
SNI	IRQ	NRUN	SB 02 01	RPT	SETSTB	CLSTB	CLSTA WSQ	CLSTA WSTB	CLISQ CLINH1	
0	0	0	0	/	/	/	/	0	0	
0	0	0	1	/	/	/	/	/	0	
0	0	1	0	/	/	/	/	0	0	
0	0	1	1	/	/	/	/	/	0	
0	1	0	0	/	/	/	/	0	0	
0	1	0	1	/	/	/	/	/	0	
0	1	1	0	/	/	/	/	0	0	
0	1	1	1	/	/	/	/	/	0	
1	0	0	0	0	0	/	0	/	0	
1	0	0	1	0	0	/	0	/	0	
1	0	1	0	/	/	0	0	/	0	
1	0	1	1	/	/	0	0	/	0	
1	1	0	0	/	/	0	0	/	0	
1	1	0	1	/	/	0	0	/	0	
1	1	1	0	/	/	0	0	/	0	
1	1	1	1	/	/	0	0	/	0	

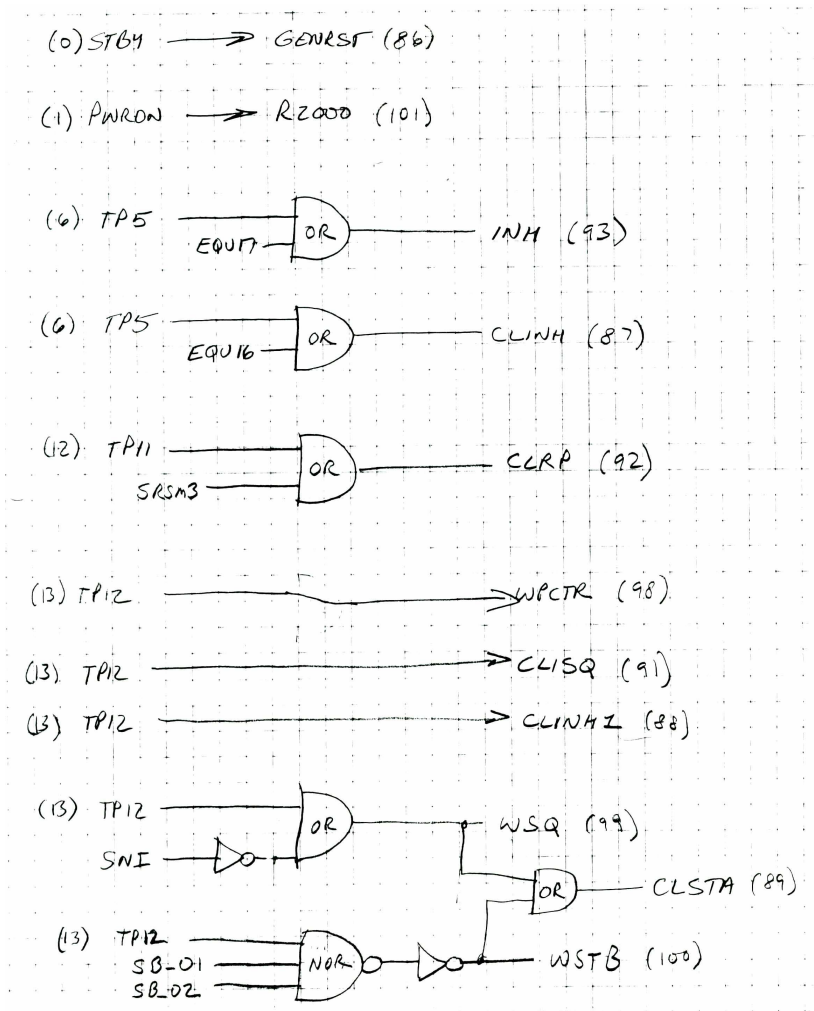This chart shows the logic for some of the more simple control pulses generated by CMP-C. Some pulses reduce to states from the TPG, such as CLISQ, WPCTR, and CLINH1, which reduce to TP12.




This is the logic for RPT and SETSTB.

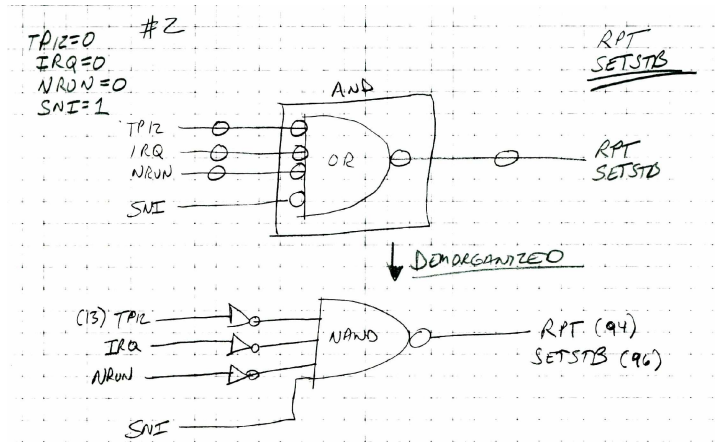


The design for CLSTB is a little more complex. The truth table to the left is reduced through the Karnaugh map to the Minterm equation below the map. A little bubble pushing DeMorganizes the logic to the final solution at the bottom right.


	A	B	C	D	CLSTB
	TP12	SWI	IRQ	NRUN	
0	0	0	0	0	1
1	0	0	0	1	1
2	0	0	1	0	1
3	0	0	1	1	1
4	0	1	0	0	0
5	0	1	0	1	0
6	0	1	1	0	0
7	0	1	1	1	0
8	1	0	0	0	1
9	1	0	0	1	1
10	1	0	1	0	1
11	1	0	1	1	1
12	1	1	0	0	1
13	1	1	0	1	1
14	1	1	1	0	1
15	1	1	1	1	1

 

$$CLSTB = A + B' + (C \cdot D')$$

 

 This is the logic for WE and SBWG, two signals that control memory access.




CPM-C CONTROL SIGNALS

<u>SIGNAL</u>	<u>#</u>	<u>DESCRIPTION</u>
GENRST	86	General Reset
CLINH	87	Clear INHINT
CLINH1	88	Clear INHINT1
CLSTA	89	Clear state counter A (STA)
CLSTB	90	Clear state counter B (STB)
CLISQ	91	Clear SNI
CLRP	92	Clear RPCCELL
INH	93	Set INHINT
RPT	94	Read RUPT opcode
SBWG	95	Write G from memory
SETSTB	96	Set the ST1 bit of STB
WE	97	Write E-MEM from G
WPCTR	98	Write PCTR (latch priority counter sequence)
WSQ	99	Write SQ
WSTB	100	Write stage counter B (STB)
R2000	101	Read 2000

CPM I INPUTS:

<u>I/E</u>	<u>signal</u>	<u>full name</u>	<u>state definition</u>
TPG:	TPG_Q3	TPG STATE	where Q3 is MSB, Q0 is LSB:
	TPG_Q2		00 = STBY
	TPG_Q1		01 = PWRON
	TPG_Q0		02 = TP1
			03 = TP2
			04 = TP3
			05 = TP4
			06 = TP5
			07 = TP6
			08 = TP7
			09 = TP8
			10 = TP9
			11 = TP10
			12 = TP11
			13 = TP12
			14 = SRLSE
			15 = WAIT

 

ADR:	EQU_16	ADDRESS = 016	0=CADR in register S = 016
	EQU_17	ADDRESS = 017	0=CADR in register S = 017
	GTR_17	ADDRESS > 017	0=CADR in register S > 017
	GTR_1777	ADDRESS > 01777	0=CADR in register S > 01777

CPM-A:	SDV1	SUBSEQ DV1	0=Subsequence DV1 is selected
	SMP1	SUBSEQ MP1	0=Subsequence MP1 is selected
	SRSM3	SUBSEQ RSM3	0=Subsequence RSM3 is selected

CTR:	SB_01	SUB SEL 01	SB_01 is LSB; SB_02 is MSB
	SB_02	SUB SEL 02	00=no counter; 01=PINC; 10=MINC


SEQ:	SNI	SELECT NEXT INST	1=select next instruction (SNI register)
------	-----	------------------	--

INT:	IRQ	INT RQST	0=interrupt requested.
------	-----	----------	------------------------

MON:	NRUN	RUN/HALT	0=run, 1=step
------	------	----------	---------------

CPM OUTPUTS:

<u>I/E</u>	<u>signal</u>	<u>full name</u>	<u>state definition</u>
	GENRST	GENERAL RESET	0=General Reset
	CLINH	CLEAR INHINT	0=Clear INHINT
	CLINH1	CLEAR INHINT1	0=Clear INHINT1
	CLSTA	CLEAR STA	0=Clear state counter A (STA)
	CLSTB	CLEAR STB	0=Clear state counter B (STB)
	CLISQ	CLEAR SNI	0=Clear SNI
	CLRP	CLEAR RPCELL	0=Clear RPCELL
	INH	SET INHINT	0=Set INHINT
	RPT	READ RUPT	0=Read RUPT opcode
	SBWG	WRITE G	0=Write G from memory
	SETSTB	SET ST1	0=Set the ST1 bit of STB
	WE	WRITE EMEM	0=Write E-MEM from G
	WPCTR	WRITE PCTR	0=Write PCTR (latch priority counter sequence)
	WSQ	WRITE SQ	0=Write SQ
	WSTB	WRITE STB	0=Write stage counter B (STB)
	R2000	READ 2000	0=Read 2000

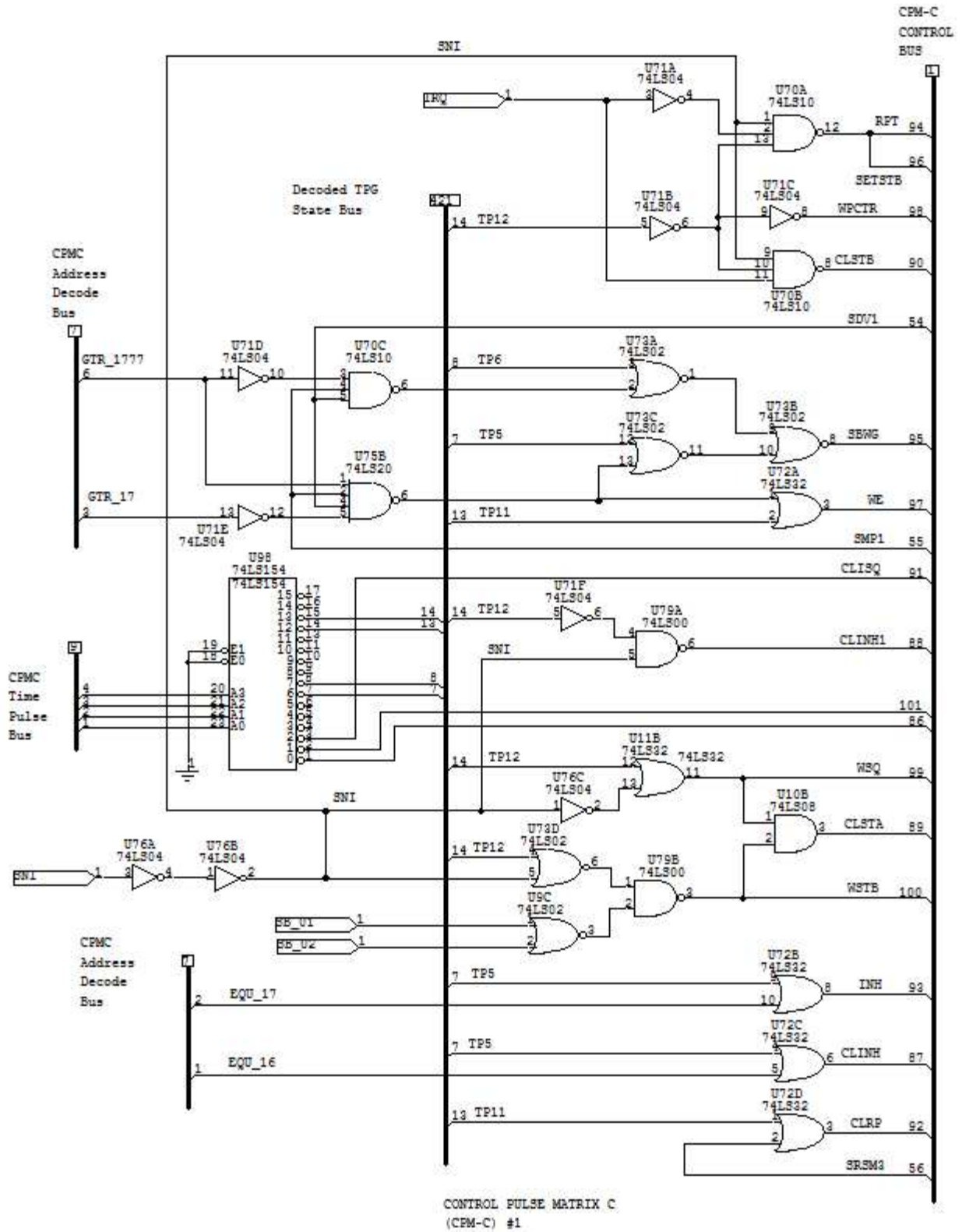

Fabrication

The CTL module is (3) 13"x5" circuit boards, and 1 control panel.

Module Rack

The module framework is designed to resemble a relay rack, but scaled to fit the circuit board dimensions. It is constructed out of 1"x2" pine and spray-painted semi-gloss gray.

Circuit boards are mounted to the rack by 2 phillips screws at either end. Nylon spacers (1/4") are used as standoffs to hold the board edges above the rack. The boards are mounted so the chips are in the back and the pins and wiring are visible from the front.

Power is distributed by 2 heavy aluminum bus bars mounted vertically, one per side, on the back of the module. Machine screws are mounted through the bus bars at evenly-spaced intervals to provide connection points for the boards.


Solid copper wire (24 gauge) connects the boards to the bus bars. Ring terminals are used on the bus bar side of the connection. On the circuit board side, the wires are soldered directly to the supply rails.

Materials were purchased from Home Depot, ACE Hardware, and Radio Shack.

Circuit Boards

The circuit boards are 13"x5" general purpose prototyping boards, epoxy glass with double-side plated through pads on 0.1" centers (JAMECO 21477CL).

 ICs are mounted in level 3 machine tooled wire-wrap sockets: 8, 14, 16, 20, 24, and 28 pin (JAMECO). Each socket has the pin-out labeled with a wire-wrap socket ID marker, which slips onto the socket before wrapping (JAMECO). The part number is written onto the ID marker.



Sockets are arranged in 4 horizontal rows on each board, with about 10 sockets per row.

Power is distributed on the back-side of each board by bare 24-gauge solid copper wire supply rails soldered at equal intervals to Klipwrap terminals: 3-prong terminals with a square tail for wire-wrapping (JAMECO 34163CL). A +5V rail runs above each row of sockets and a ground rail runs below. Each rail connects directly to the aluminum module power bus using a ring tail connector.

On the pin side of the board, all connections are made with 30 AWG Kynar wire-wrap wire (JAMECO). Red wire is used for direct connections to the +5V supply rail. Black wire is used for direct connections to ground. White wire is used for everything else.


Power connections from the supply rails to each ICs are double-wrapped. Bypassing capacitors (.1 uf disc) are soldered across the supply rails at the Klipwrap terminals; about 1 capacitor for every 2 IC packages.

All connections were stripped and hand-wrapped using a Radio Shack hand-wrap tool. As each connection was made, the corresponding line on the schematic was marked with a colored highlighter.

DIP resistor networks (JAMECO) plugged into 20-pin wire-wrap sockets were used as current limiting resistors for the panel indicators.


CTL Printed Circuit Board (PCB) A

 The A board contains the clock (CLK), the scaler (SCL), and the time pulse generator (TPG).




CTL Printed Circuit Board (PCB) B

The B board contains the display indicators, their current-limiting resistor networks, and the open collector drivers. The display panel is a sheet of white styrene plastic. A push pin was used to make holes through the plastic, and the LEDs were inserted in rows. The panel was hand-lettered with an indelible marker. A few chips near the bottom right of the B board are associated with subsystems on the C board.

 

CTL Printed Circuit Board (PCB) C

 The C board contains the sequence generator (SEQ) and control pulse matrixes (CPM-A, CPM-B, and CPM-C). The big ICs at the bottom are the EPROMs that hold the control pulse matrix table for CPM-A. Each EPROM holds the tables for 8 control signals. The large ICs at the top are decoders for the CPM-B and CPM-C logic.



Parts (ICs)

74LS00	(14)	U74,U26,U27,U25,U79,U78,U55,U54,U53,U48,U13,U42,U34,U28
74LS02	(9)	U4,U77,U9,U73,U45,U43,U3,U38,U32
74LS04	(15)	U62,U29,U76,U69,U64,U57,U71,U59,U58,U56,U49,U41,U40,U39,U33
74LS06	(11)	U22,U21,U20,U23,U14,U17,U18,U19,U16,U15,U1
74LS08	(2)	U65,U10
74LS10	(4)	U12,U70,U52,U51
74LS20	(8)	U67,U68,U66,U63,U75,U61,U60,U6
74LS27	(3)	U7,U44,U2
74LS32	(3)	U72,U11,U5
74LS74	(1)	U24
74LS112	(8)	U8,U50,U47,U46,U35,U36,U37,U31
74LS138	(1)	U99
74LS154	(7)	U81,U82,U83,U98,U100,U101,U106
74LS161	(8)	U104,U107,U108,U109,U110,U111,U112,U113
74LS244	(10)	U80,U84,U85,U93,U94,U95,U96,U97,U102,U103
74LS273	(1)	U105
27C128	(7)	U86,U87,U88,U89,U90,U91,U92
4001	(1)	U30
555	(1)	U114

IC's, sockets, PCB's, resistors, capacitors, wire-wrap wire were purchased from JAMECO. The 2.048 MHz crystal and the IDE wire-wrap were from DigiKey. Wire ties, wire-wrap tools, and copper wire were purchased from Radio Shack. IDE ribbon cables were purchased from an online computer supplier.

Power Budget

	<u>qty</u>	<u>mA (ea)</u>	<u>mA (tot)</u>
74LS00	14	2.4	33.6
74LS02	9	2.4	21.6
74LS04	15	3.6	54.0
74LS06	11	3.6	39.6
74LS08	2	4.4	8.8
74LS10	4	1.8	7.2
74LS20	8	1.2	9.6
74LS27	3	3.4	10.2
74LS32	3	4.9	14.7
74LS74	1	4.0	4.0
74LS112	8	4.0	32.0
74LS138	1	6.3	6.3
74LS154	7	6.2	43.4
74LS161	8	19.0	152.0
74LS244	10	32.0	320.0
74LS273	1	17.0	17.0
27C128	7	25.0	175.0
4001	1	0.4	0.4
555	1	3.0	3.0
LED	61	20.0	1220.0

2.2 Amps total
1.0 Amps (excluding LEDs)

EPROM generator program

This C++ program generates all files needed to program the CPM-A EPROMs. The files are generated in Motorola S-Record format.

```
/*
*****
*
* CPM-A EPROM GENERATOR
*
* 9/14/01
*
*****

Versions:
    Derived from AGC C++ simulator 1.15.

Operation:
    Generates all of the CPM-A EPROM files in Motorola s2f S-Record format
    suitable for EPROM programmers.

*/

#include <string.h>
#include <stdlib.h>
#include <ctype.h>
#include <iostream.h>
#include <stdio.h>

#define MAXPULSES 15
#define MAX_IPULSES 5 // no more than 5 instruction-generated pulses active at any time

enum cpType { // **inferred; not defined in original R393 AGC4 spec.
    NO_PULSE=0,

    // OUTPUTS FROM SUBSYSTEM A
    C1          =1,    // Carry in
    CLG         =2,    // Clear G
    CLCTR       =3,    // Clear loop counter
    CTR         =4,    // Loop counter
    GP          =5,    // Generate Parity
    KRPT        =6,    // Knock down Rupt priority
    NISQ        =7,    // New instruction to the SQ register
    RA          =8,    // Read A
    RB          =9,    // Read B
    RB14        =10,   // Read bit 14
    RC          =11,   // Read C
    RG          =12,   // Read G
    RLP         =13,   // Read LP
    RP2         =14,   // Read parity 2
    RQ          =15,   // Read Q
    RRP         =16,   // Read RUPT address
    RSB         =17,   // Read sign bit
    RSCT        =18,   // Read selected counter address
    RU          =19,   // Read sum
    RZ          =20,   // Read Z
    R1          =21,   // Read 1
    R1C         =22,   // Read 1 complimented
    R2          =23,   // Read 2
    R22         =24,   // Read 22
    R24         =25,   // Read 24
    ST1         =26,   // Stage 1
    ST2         =27,   // Stage 2
    TMZ         =28,   // Test for minus zero
    TOV         =29,   // Test for overflow
    TP          =30,   // Test parity
    TRSM        =31,   // Test for resume
    TSGN        =32,   // Test sign
    TSGN2       =33,   // Test sign 2
    WA          =34,   // Write A

```

```

WALP      =35,    // Write A and LP
WB        =36,    // Write B
WGx       =37,    // Write G (do not reset)
WLP       =38,    // Write LP
WOVC      =39,    // Write overflow counter
WOVI      =40,    // Write overflow RUPT inhibit
WOVR      =41,    // Write overflow
WP        =42,    // Write P
WPx       =43,    // Write P (do not reset)
WP2       =44,    // Write P2
WQ        =45,    // Write Q
WS        =46,    // Write S
WX        =47,    // Write X
WY        =48,    // Write Y
WYx       =49,    // Write Y (do not reset)
WZ        =50,    // Write Z

// OUTPUTS FROM SUBSYSTEM A; USED AS INPUTS TO SUBSYSTEM B ONLY;
// NOT USED OUTSIDE CPM
RSC        =51,    // Read special and central (output to B only, not outside CPM)
WSC        =52,    // Write special and central (output to B only, not outside CPM)
WG         =53,    // Write G (output to B only, not outside CPM)

// OUTPUTS FROM SUBSYSTEM A; USED AS INPUTS TO SUBSYSTEM C ONLY;
// NOT USED OUTSIDE CPM
SDV1       =54,    // Subsequence DV1 is currently active
SMP1       =55,    // Subsequence MP1 is currently active
SRSM3      =56,    // Subsequence RSM3 is currently active

// EXTERNAL OUTPUTS FROM SUBSYSTEM B
//
RA0        =57,    // Read register at address 0 (A)
RA1        =58,    // Read register at address 1 (Q)
RA2        =59,    // Read register at address 2 (Z)
RA3        =60,    // Read register at address 3 (LP)
RA4        =61,    // Read register at address 4
RA5        =62,    // Read register at address 5
RA6        =63,    // Read register at address 6
RA7        =64,    // Read register at address 7
RA10       =65,    // Read register at address 10 (octal)
RA11       =66,    // Read register at address 11 (octal)
RA12       =67,    // Read register at address 12 (octal)
RA13       =68,    // Read register at address 13 (octal)
RA14       =69,    // Read register at address 14 (octal)
RBK        =70,    // Read BNK
WA0        =71,    // Write register at address 0 (A)
WA1        =72,    // Write register at address 1 (Q)
WA2        =73,    // Write register at address 2 (Z)
WA3        =74,    // Write register at address 3 (LP)
WA10       =75,    // Write register at address 10 (octal)
WA11       =76,    // Write register at address 11 (octal)
WA12       =77,    // Write register at address 12 (octal)
WA13       =78,    // Write register at address 13 (octal)
WA14       =79,    // Write register at address 14 (octal)
WBK        =80,    // Write BNK
WGn        =81,    // Write G (normal gates)**
W20        =82,    // Write into CYR
W21        =83,    // Write into SR
W22        =84,    // Write into CYL
W23        =85,    // Write into SL

// THESE ARE THE LEFTOVERS -- THEY'RE PROBABLY USED IN SUBSYSTEM C
//
GENRST     =86,    // General Reset**
CLINH      =87,    // Clear INHINT**
CLINH1     =88,    // Clear INHINT1**
CLSTA      =89,    // Clear state counter A (STA)**
CLSTB      =90,    // Clear state counter B (STB)**
CLISQ      =91,    // Clear SNI**
CLRP       =92,    // Clear RPCELL**
INH        =93,    // Set INHINT**
RPT        =94,    // Read RUPT opcode **
SBWG       =95,    // Write G from memory
SETSTB     =96,    // Set the ST1 bit of STB

```

```

WE          =97,    // Write E-MEM from G
WPCTR       =98,    // Write PCTR (latch priority counter sequence)**
WSQ         =99,    // Write SQ
WSTB        =100,   // Write stage counter B (STB)**
R2000       =101,   // Read 2000 **
};

static cpType gbl_cp[MAXPULSES]; // current set of asserted control pulses (MAXPULSES)

enum scType { // identifies subsequence for a given instruction
    SUB0=0,    // ST2=0, ST1=0
    SUB1=1,    // ST2=0, ST1=1
    SUB2=2,    // ST2=1, ST1=0
    SUB3=3,    // ST2=1, ST1=1
};

enum brType {
    BR00 =0,   // BR1=0, BR2=0
    BR01 =1,   // BR1=0, BR2=1
    BR10 =2,   // BR1=1, BR2=0
    BR11 =3,   // BR1=1, BR2=1
    NO_BR =4   // NO BRANCH
};

struct controlSubStep {
    brType br; // normally no branch (NO_BR)
    cpType pulse[MAX_IPULSES]; // contains 0 - MAXPULSES control pulses
};

struct controlStep {
    controlSubStep substep[4]; // indexed by brType (BR00, BR01, BR10, BR11)
};

struct subsequence {
    controlStep tp[11]; // indexed by tpType (TP1-TP11)
};

struct sequence {
    subsequence* subseq[4]; // indexed by scType
};

#define STEP_INACTIVE \
    NO_BR, {NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE}, \
    NO_BR, {NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE}, \
    NO_BR, {NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE}, \
    NO_BR, {NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE}

#define STEP(p1, p2, p3, p4, p5) \
    NO_BR, { p1, p2, p3, p4, p5}, \
    NO_BR, {NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE}, \
    NO_BR, {NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE}, \
    NO_BR, {NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE}

subsequence SUB_TCO = {
    STEP ( RB,          WY,          WS,          CI,          NO_PULSE      ), // TP 1
    STEP_INACTIVE, // TP 2
    STEP ( WG,          NO_PULSE,    NO_PULSE,    NO_PULSE,    NO_PULSE      ), // TP 3
    STEP ( RA,          WOVI,        NO_PULSE,    NO_PULSE,    NO_PULSE      ), // TP 4
    STEP_INACTIVE, // TP 5
    STEP_INACTIVE, // TP 6
    STEP ( RG,          RSC,          WB,          WP,          NO_PULSE      ), // TP 7
    STEP ( RZ,          WQ,          GP,          TP,          NO_PULSE      ), // TP 8
    STEP ( RB,          WSC,          WG,          NO_PULSE,    NO_PULSE      ), // TP 9
    STEP ( RU,          WZ,          NO_PULSE,    NO_PULSE,    NO_PULSE      ), // TP 10
    STEP ( NISQ,        NO_PULSE,    NO_PULSE,    NO_PULSE,    NO_PULSE      ), // TP 11
};

subsequence SUB_CCSSO = {
    STEP ( RB,          WS,          NO_PULSE,    NO_PULSE,    NO_PULSE      ), // TP 1
    STEP ( RZ,          WY,          NO_PULSE,    NO_PULSE,    NO_PULSE      ), // TP 2
    STEP ( WG,          NO_PULSE,    NO_PULSE,    NO_PULSE,    NO_PULSE      ), // TP 3
    STEP_INACTIVE, // TP 4
    STEP_INACTIVE, // TP 5
    STEP ( RG,          RSC,          WB,          TSGN,        WP             ), // TP 6
    BR00, RC,          TMZ,          NO_PULSE,    NO_PULSE,    NO_PULSE      ), // TP 7
    BR01, RC,          TMZ,          NO_PULSE,    NO_PULSE,    NO_PULSE
};

```

```

BR10,  RB,          TMZ,          NO_PULSE,    NO_PULSE,    NO_PULSE,
BR11,  RB,          TMZ,          NO_PULSE,    NO_PULSE,    NO_PULSE,
BR00,  GP,          TP,          NO_PULSE,    NO_PULSE,    NO_PULSE,          // TP 8
BR01,  R1,          WX,          GP,          TP,          NO_PULSE,
BR10,  R2,          WX,          GP,          TP,          NO_PULSE,
BR11,  R1,          R2,          WX,          GP,          TP,
STEP (  RB,        WSC,        WG,          NO_PULSE,    NO_PULSE,          ), // TP 9
BR00,  RC,          WA,          NO_PULSE,    NO_PULSE,    NO_PULSE,          // TP 10
BR01,  WA,          R1C,        NO_PULSE,    NO_PULSE,    NO_PULSE,
BR10,  RB,          WA,          NO_PULSE,    NO_PULSE,    NO_PULSE,
BR11,  WA,          R1C,        NO_PULSE,    NO_PULSE,    NO_PULSE,
STEP (  RU,        ST1,        WZ,          NO_PULSE,    NO_PULSE,          ) // TP 11
};

subsequence SUB_CCS1 = {
STEP (  RZ,        WY,          WS,          CI,          NO_PULSE,          ), // TP 1
STEP_INACTIVE, // TP 2
STEP (  WG,        NO_PULSE,    NO_PULSE,    NO_PULSE,    NO_PULSE,          ), // TP 3
STEP (  RU,        WZ,          NO_PULSE,    NO_PULSE,    NO_PULSE,          ), // TP 4
STEP (  RA,        WY,          CI,          NO_PULSE,    NO_PULSE,          ), // TP 5
STEP_INACTIVE, // TP 6
STEP (  RG,        RSC,        WB,          WP,          NO_PULSE,          ), // TP 7
STEP (  RU,        WB,          GP,          TP,          NO_PULSE,          ), // TP 8
STEP_INACTIVE, // TP 9
STEP (  RC,        WA,          WOVI,       NO_PULSE,    NO_PULSE,          ), // TP 10
STEP (  RG,        RSC,        WB,          NISQ,       NO_PULSE,          ) // TP 11
};

subsequence SUB_NDX0 = {
STEP (  RB,        WS,          NO_PULSE,    NO_PULSE,    NO_PULSE,          ), // TP 1
STEP_INACTIVE, // TP 2
STEP (  WG,        NO_PULSE,    NO_PULSE,    NO_PULSE,    NO_PULSE,          ), // TP 3
STEP (  RA,        WOVI,       NO_PULSE,    NO_PULSE,    NO_PULSE,          ), // TP 4
STEP_INACTIVE, // TP 5
STEP_INACTIVE, // TP 6
STEP (  RG,        RSC,        WB,          WP,          NO_PULSE,          ), // TP 7
STEP (  GP,        TP,          NO_PULSE,    NO_PULSE,    NO_PULSE,          ), // TP 8
STEP (  RB,        WSC,        WG,          NO_PULSE,    NO_PULSE,          ), // TP 9
STEP (  TRSM,     NO_PULSE,    NO_PULSE,    NO_PULSE,    NO_PULSE,          ), // TP 10
STEP (  ST1,     NO_PULSE,    NO_PULSE,    NO_PULSE,    NO_PULSE,          ), // TP 11
};

subsequence SUB_NDX1 = {
STEP (  RZ,        WY,          WS,          CI,          NO_PULSE,          ), // TP 1
STEP_INACTIVE, // TP 2
STEP (  WG,        NO_PULSE,    NO_PULSE,    NO_PULSE,    NO_PULSE,          ), // TP 3
STEP (  RU,        WZ,          NO_PULSE,    NO_PULSE,    NO_PULSE,          ), // TP 4
STEP_INACTIVE, // TP 5
STEP (  RB,        WY,          NO_PULSE,    NO_PULSE,    NO_PULSE,          ), // TP 6
STEP (  RG,        RSC,        WB,          WP,          NO_PULSE,          ), // TP 7
STEP (  RB,        WX,          GP,          TP,          NO_PULSE,          ), // TP 8
STEP (  RB,        WSC,        WG,          NO_PULSE,    NO_PULSE,          ), // TP 9
STEP_INACTIVE, // TP 10
STEP (  RU,        WB,          WOVI,       NISQ,       NO_PULSE,          ), // TP 11
};

subsequence SUB_RSM3 = {
STEP (  R24,     WS,          NO_PULSE,    NO_PULSE,    NO_PULSE,          ), // TP 1
STEP_INACTIVE, // TP 2
STEP (  WG,        NO_PULSE,    NO_PULSE,    NO_PULSE,    NO_PULSE,          ), // TP 3
STEP_INACTIVE, // TP 4
STEP_INACTIVE, // TP 5
STEP_INACTIVE, // TP 6
STEP (  RG,        WZ,          NO_PULSE,    NO_PULSE,    NO_PULSE,          ), // TP 7
STEP_INACTIVE, // TP 8
STEP_INACTIVE, // TP 9
STEP_INACTIVE, // TP 10
STEP (  NISQ,     NO_PULSE,    NO_PULSE,    NO_PULSE,    NO_PULSE,          ), // TP 11
};

subsequence SUB_XCH0 = {
STEP (  RB,        WS,          NO_PULSE,    NO_PULSE,    NO_PULSE,          ), // TP 1
STEP (  RA,        WP,          NO_PULSE,    NO_PULSE,    NO_PULSE,          ), // TP 2
STEP (  WG,        NO_PULSE,    NO_PULSE,    NO_PULSE,    NO_PULSE,          ), // TP 3
STEP (  WP2,     NO_PULSE,    NO_PULSE,    NO_PULSE,    NO_PULSE,          ), // TP 4
STEP_INACTIVE, // TP 5
};

```



```

STEP_INACTIVE, // TP 6
STEP ( RG, RSC, WB, WP, NO_PULSE ), // TP 7
STEP ( GP, TP, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 8
STEP ( RA, WSC, WG, RP2, NO_PULSE ), // TP 9
STEP ( RB, WA, WOVI, NO_PULSE, NO_PULSE ), // TP 10
STEP ( ST2, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 11
};

subsequence SUB_CS0 = {
STEP ( RB, WS, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 1
STEP_INACTIVE, // TP 2
STEP ( WG, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 3
STEP_INACTIVE, // TP 4
STEP_INACTIVE, // TP 5
STEP_INACTIVE, // TP 6
STEP ( RG, RSC, WB, WP, NO_PULSE ), // TP 7
STEP ( GP, TP, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 8
STEP ( RB, WSC, WG, NO_PULSE, NO_PULSE ), // TP 9
STEP ( RC, WA, WOVI, NO_PULSE, NO_PULSE ), // TP 10
STEP ( ST2, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 11
};

subsequence SUB_TS0 = {
STEP ( RB, WS, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 1
STEP ( RA, WB, TOV, WP, NO_PULSE ), // TP 2
STEP ( WG, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 3
BR00, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE, // TP 4
BR01, RZ, WY, CI, NO_PULSE, NO_PULSE, //
overflow
BR10, RZ, WY, CI, NO_PULSE, NO_PULSE, //
underflow
BR11, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE, // TP 5
BR00, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE, // TP 6
BR01, R1, WA, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE, // TP 7
BR10, WA, R1C, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE, // TP 8
BR11, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE, // TP 9
STEP ( GP, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 10
STEP ( RB, WSC, WG, NO_PULSE, NO_PULSE ), // TP 11
};

subsequence SUB_ADO = {
STEP ( RB, WS, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 1
STEP ( RA, WY, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 2
STEP ( WG, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 3
STEP_INACTIVE, // TP 4
STEP_INACTIVE, // TP 5
STEP_INACTIVE, // TP 6
STEP ( RG, RSC, WB, WP, NO_PULSE ), // TP 7
STEP ( RB, WX, GP, TP, NO_PULSE ), // TP 8
STEP ( RB, WSC, WG, NO_PULSE, NO_PULSE ), // TP 9
STEP_INACTIVE, // TP 10
STEP ( RU, WA, WOVC, ST2, WOVI ), // TP 11
};

// Note: AND is performed using DeMorgan's Theorem: the inputs are inverted, a
// logical OR is performed, and the result is inverted. The implementation of the
// OR (at TP8) is somewhat unorthodox: the inverted inputs are in registers U
// and C. The OR is achieved by gating both registers onto the read/write bus
// simultaneously. (The bus only transfers logical 1's; register-to-register transfers
// are performed by clearing the destination register and then transferring the
// 1's from the source register to the destination). When the 1's from both
// registers are simultaneously gated onto the bus, the word on the bus is a logical
// OR of both registers.
subsequence SUB_MASK0 = {
STEP ( RB, WS, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 1
STEP ( RA, WB, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 2
STEP ( WG, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 3

```

```

STEP ( RC, WY, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 4
STEP_INACTIVE, // TP 5
STEP_INACTIVE, // TP 6
STEP ( RG, RSC, WB, WP, NO_PULSE ), // TP 7
STEP ( RU, RC, WA, GP, TP ), // TP 8
(CHANGED)
STEP_INACTIVE, // TP 9
(CHANGED)
STEP ( RA, WB, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 10
STEP ( RC, WA, ST2, WOV1, NO_PULSE ), // TP 11
};

subsequence SUB_MP0 = {
STEP ( RB, WS, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 1
STEP ( RA, WB, TSGN, NO_PULSE, NO_PULSE ), // TP 2
STEP ( RSC, WG, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 3
BR00, RB, WLP, NO_PULSE, NO_PULSE, NO_PULSE, // TP 4
BR01, RB, WLP, NO_PULSE, NO_PULSE, NO_PULSE,
BR10, RC, WLP, NO_PULSE, NO_PULSE, NO_PULSE,
BR11, RC, WLP, NO_PULSE, NO_PULSE, NO_PULSE,
STEP ( RLP, WA, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 5
STEP_INACTIVE, // TP 6
BR00, RG, WY, WP, NO_PULSE, NO_PULSE, // TP 7
BR01, RG, WY, WP, NO_PULSE, NO_PULSE,
BR10, RG, WB, WP, NO_PULSE, NO_PULSE,
BR11, RG, WB, WP, NO_PULSE, NO_PULSE,
BR00, GP, TP, NO_PULSE, NO_PULSE, NO_PULSE, // TP 8
BR01, GP, TP, NO_PULSE, NO_PULSE, NO_PULSE,
BR10, RC, WY, GP, TP, NO_PULSE,
BR11, RC, WY, GP, TP, NO_PULSE,
STEP ( RU, WB, TSGN2, NO_PULSE, NO_PULSE ), // TP 9
BR00, RA, WLP, TSGN, NO_PULSE, NO_PULSE, // TP 10
BR01, RA, RB14, WLP, TSGN, NO_PULSE,
BR10, RA, WLP, TSGN, NO_PULSE, NO_PULSE,
BR11, RA, RB14, WLP, TSGN, NO_PULSE,
BR00, ST1, WALP, NO_PULSE, NO_PULSE, NO_PULSE, // TP 11
BR01, R1, ST1, WALP, R1C, NO_PULSE,
BR10, RU, ST1, WALP, NO_PULSE, NO_PULSE,
BR11, RU, ST1, WALP, NO_PULSE, NO_PULSE,
};

subsequence SUB_MP1 = {
STEP ( RA, WY, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 1
STEP ( RLP, WA, TSGN, NO_PULSE, NO_PULSE ), // TP 2
BR00, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE, // TP 3
BR01, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE,
BR10, RB, WX, NO_PULSE, NO_PULSE, NO_PULSE,
BR11, RB, WX, NO_PULSE, NO_PULSE, NO_PULSE,
STEP ( RA, WLP, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 4
STEP ( RLP, TSGN, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 5
STEP ( RU, WALP, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 6
STEP ( RA, WY, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 7
BR00, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE, // TP 8
BR01, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE,
BR10, RB, WX, NO_PULSE, NO_PULSE, NO_PULSE,
BR11, RB, WX, NO_PULSE, NO_PULSE, NO_PULSE,
STEP ( RLP, WA, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 9
STEP ( RA, WLP, CTR, NO_PULSE, NO_PULSE ), // TP 10
STEP ( RU, ST1, WALP, NO_PULSE, NO_PULSE ), // TP 11
};

subsequence SUB_MP3 = {
STEP ( RZ, WY, WS, CI, NO_PULSE ), // TP 1
STEP ( RLP, TSGN, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 2
STEP ( WG, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 3
STEP ( RU, WZ, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 4
STEP ( RA, WY, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 5
BR00, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE, // TP 6
BR01, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE,
BR10, RB, WX, NO_PULSE, NO_PULSE, NO_PULSE,
BR11, RB, WX, NO_PULSE, NO_PULSE, NO_PULSE,
STEP ( RG, RSC, WB, WP, NO_PULSE ), // TP 7
STEP ( RLP, WA, GP, TP, NO_PULSE ), // TP 8
STEP ( RB, WSC, WG, NO_PULSE, NO_PULSE ), // TP 9
STEP ( RA, WLP, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 10
STEP ( RU, WALP, NISQ, NO_PULSE, NO_PULSE ), // TP 11
};

```

};

```
subsequence SUB_DV0 = {
  STEP ( RB, WS, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 1
  STEP ( RA, WB, TSGN, NO_PULSE, NO_PULSE ), // TP 2
  STEP ( RSC, WG, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 3
  BR00, RC, WA, NO_PULSE, NO_PULSE, NO_PULSE, // TP 4
  BR01, RC, WA, NO_PULSE, NO_PULSE, NO_PULSE,
  BR10, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE,
  BR11, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE,
  BR00, R1, WLP, NO_PULSE, NO_PULSE, NO_PULSE, // TP 5
  BR01, R1, WLP, NO_PULSE, NO_PULSE, NO_PULSE,
  BR10, R2, WLP, NO_PULSE, NO_PULSE, NO_PULSE,
  BR11, R2, WLP, NO_PULSE, NO_PULSE, NO_PULSE,
  STEP ( RA, WQ, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 6
  STEP ( RG, WB, TSGN, WP, NO_PULSE ), // TP 7
  STEP ( RB, WA, GP, TP, NO_PULSE ), // TP 8
  BR00, RLP, R2, WB, NO_PULSE, NO_PULSE, // TP 9
  BR01, RLP, R2, WB, NO_PULSE, NO_PULSE,
  BR10, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE,
  BR11, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE,
  BR00, RB, WLP, NO_PULSE, NO_PULSE, NO_PULSE, // TP 10
  BR01, RB, WLP, NO_PULSE, NO_PULSE, NO_PULSE,
  BR10, RC, WA, NO_PULSE, NO_PULSE, NO_PULSE,
  BR11, RC, WA, NO_PULSE, NO_PULSE, NO_PULSE,
  STEP ( R1, ST1, WB, NO_PULSE, NO_PULSE ), // TP 11
};
```

```
subsequence SUB_DV1 = {
  STEP ( R22, WS, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 1
  STEP ( RQ, WG, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 2
  STEP ( RG, WQ, WY, RSB, NO_PULSE ), // TP 3
  STEP ( RA, WX, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 4
  STEP ( RLP, TSGN2, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 5
  STEP_INACTIVE, // TP 6
  STEP ( RU, TSGN, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 7
  BR00, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE, // TP 8
  BR01, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE,
  BR10, RU, WQ, NO_PULSE, NO_PULSE, NO_PULSE,
  BR11, RU, WQ, NO_PULSE, NO_PULSE, NO_PULSE,
  BR00, RB, RSB, WG, NO_PULSE, NO_PULSE, // TP 9
  BR01, RB, RSB, WG, NO_PULSE, NO_PULSE,
  BR10, RB, WG, NO_PULSE, NO_PULSE, NO_PULSE,
  BR11, RB, WG, NO_PULSE, NO_PULSE, NO_PULSE,
  STEP ( RG, WB, TSGN, NO_PULSE, NO_PULSE ), // TP 10
  BR00, ST1, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE, // TP 11
  BR01, ST1, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE,
  BR10, RC, WA, ST2, NO_PULSE, NO_PULSE,
  BR11, RB, WA, ST2, NO_PULSE, NO_PULSE,
};
```

```
subsequence SUB_SU0 = {
  STEP ( RB, WS, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 1
  STEP ( RA, WY, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 2
  STEP ( WG, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 3
  STEP_INACTIVE, // TP 4
  STEP_INACTIVE, // TP 5
  STEP_INACTIVE, // TP 6
  STEP ( RG, RSC, WB, WP, NO_PULSE ), // TP 7
  STEP ( RC, WX, GP, TP, NO_PULSE ), // TP 8
  STEP ( RB, WSC, WG, NO_PULSE, NO_PULSE ), // TP 9
  STEP_INACTIVE, // TP 10
  STEP ( RU, WA, WOVC, ST2, WOVI ), // TP 11
};
```

```
subsequence SUB_RUPT1 = {
  STEP ( R24, WY, WS, CI, NO_PULSE ), // TP 1
  STEP_INACTIVE, // TP 2
  STEP ( WG, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 3
  STEP_INACTIVE, // TP 4
  STEP_INACTIVE, // TP 5
  STEP_INACTIVE, // TP 6
  STEP_INACTIVE, // TP 7
  STEP_INACTIVE, // TP 8
  STEP ( RZ, WG, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 9
  STEP ( RU, WZ, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 10
};
```

```

        STEP ( ST1, ST2, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 11
};

subsequence SUB_RUPT3 = {
    STEP ( RZ, WS, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 1
    STEP ( RRP, WZ, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 2
    STEP ( RZ, KRPT, WG, NO_PULSE, NO_PULSE ), // TP 3
    STEP_INACTIVE, // TP 4
    STEP_INACTIVE, // TP 5
    STEP_INACTIVE, // TP 6
    STEP_INACTIVE, // TP 7
    STEP_INACTIVE, // TP 8
    STEP ( RB, WSC, WG, NO_PULSE, NO_PULSE ), // TP 9
    STEP_INACTIVE, // TP 10
    STEP ( ST2, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 11
};

subsequence SUB_STD2 = {
    STEP ( RZ, WY, WS, CI, NO_PULSE ), // TP 1
    STEP_INACTIVE, // TP 2
    STEP ( WG, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 3
    STEP ( RU, WZ, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 4
    STEP_INACTIVE, // TP 5
    STEP_INACTIVE, // TP 6
    STEP ( RG, RSC, WB, WP, NO_PULSE ), // TP 7
    STEP ( GP, TP, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 8
    STEP ( RB, WSC, WG, NO_PULSE, NO_PULSE ), // TP 9
    STEP_INACTIVE, // TP 10
    STEP ( NISQ, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 11
};

subsequence SUB_PINC = {
    STEP ( WS, RSCT, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 1
    STEP_INACTIVE, // TP 2
    STEP ( WG, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 3
    STEP ( R1, WY, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 4
    STEP_INACTIVE, // TP 5
    STEP ( RG, WX, WP, NO_PULSE, NO_PULSE ), // TP 6
    STEP ( TP, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 7
    STEP ( WP, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 8
    STEP ( RU, CLG, WPX, NO_PULSE, NO_PULSE ), // TP 9
    STEP ( RU, WGx, WOV, NO_PULSE, NO_PULSE ), // TP 10
    STEP_INACTIVE, // TP 11
};

subsequence SUB_MINC = {
    STEP ( WS, RSCT, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 1
    STEP_INACTIVE, // TP 2
    STEP ( WG, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 3
    STEP ( WY, R1C, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 4
    STEP_INACTIVE, // TP 5
    STEP ( RG, WX, WP, NO_PULSE, NO_PULSE ), // TP 6
    STEP ( TP, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 7
    STEP ( WP, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 8
    STEP ( RU, CLG, WPX, NO_PULSE, NO_PULSE ), // TP 9
    STEP ( RU, WGx, WOV, NO_PULSE, NO_PULSE ), // TP 10
    STEP_INACTIVE, // TP 11
};

subsequence SUB_SHINC = {
    STEP ( WS, RSCT, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 1
    STEP_INACTIVE, // TP 2
    STEP ( WG, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 3
    STEP ( WY, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 4
    STEP_INACTIVE, // TP 5
    STEP ( RG, WYx, WX, WP, NO_PULSE ), // TP 6
    STEP ( TP, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 7
    STEP ( WP, NO_PULSE, NO_PULSE, NO_PULSE, NO_PULSE ), // TP 8
    STEP ( RU, CLG, WPX, NO_PULSE, NO_PULSE ), // TP 9
    STEP ( RU, WGx, WOV, NO_PULSE, NO_PULSE ), // TP 10
    STEP_INACTIVE, // TP 11
};

char* subseqString[] =
{
    "TC0",

```

```

"CCS0",
"CCS1",
"NDX0",
"NDX1",
"RSM3",
"XCH0",
"CS0",
"TS0",
"ADO",
"MASK0",
"MPO",
"MP1",
"MP3",
"DVO",
"DV1",
"SU0",
"RUPT1",
"RUPT3",
"STD2",
"PINCO",
"MINCO",
"SHINCO",
"NO_SEQ"
};

enum subseq {
    TC0      =0,
    CCS0     =1,
    CCS1     =2,
    NDX0     =3,
    NDX1     =4,
    RSM3     =5,
    XCH0     =6,
    CS0      =7,
    TS0      =8,
    ADO      =9,
    MASK0    =10,
    MPO      =11,
    MP1      =12,
    MP3      =13,
    DVO      =14,
    DV1      =15,
    SU0      =16,
    RUPT1    =17,
    RUPT3    =18,
    STD2     =19,
    PINCO    =20,
    MINCO    =21,
    SHINCO   =22,
    NO_SEQ   =23
};

enum tpType {
    STBY      =0,
    PWRON     =1,

    TP1       =2,      // TIME PULSE 1: start of memory cycle time (MCT)
    TP2       =3,
    TP3       =4,
    TP4       =5,
    TP5       =6,
    TP6       =7,      // EMEM is available in G register by TP6
    TP7       =8,      // FMEM is available in G register by TP7
    TP8       =9,
    TP9       =10,
    TP10      =11,     // G register written to memory beginning at TP10
    TP11      =12,     // TIME PULSE 11: end of memory cycle time (MCT)
    TP12      =13,     // select new subsequence/select new instruction

    SRLSE     =14,     // step switch release
    WAIT      =15
};

subseq instructionSubsequenceDecoder(
    int SB2_field, int SB1_field, int SQ_field, int STB_field)

```

```

{
    // Combinational logic decodes instruction and the stage count
    // to get the instruction subsequence.
    static subseq decode[16][4] = {
        { TCO, RUPT1, STD2, RUPT3 }, // 00
        { CCS0, CCS1, NO_SEQ, NO_SEQ }, // 01
        { NDX0, NDX1, NO_SEQ, RSM3 }, // 02
        { XCH0, NO_SEQ, STD2, NO_SEQ }, // 03

        { NO_SEQ, NO_SEQ, NO_SEQ, NO_SEQ }, // 04
        { NO_SEQ, NO_SEQ, NO_SEQ, NO_SEQ }, // 05
        { NO_SEQ, NO_SEQ, NO_SEQ, NO_SEQ }, // 06
        { NO_SEQ, NO_SEQ, NO_SEQ, NO_SEQ }, // 07
        { NO_SEQ, NO_SEQ, NO_SEQ, NO_SEQ }, // 10

        { MPO, MP1, NO_SEQ, MP3 }, // 11
        { DVO, DV1, STD2, NO_SEQ }, // 12
        { SUO, NO_SEQ, STD2, NO_SEQ }, // 13

        { CS0, NO_SEQ, STD2, NO_SEQ }, // 14
        { TSO, NO_SEQ, STD2, NO_SEQ }, // 15
        { ADO, NO_SEQ, STD2, NO_SEQ }, // 16
        { MASK0, NO_SEQ, STD2, NO_SEQ }, // 17

    };

    if(SB2_field == 0 && SB1_field == 1)
        return PINCO;
    else if(SB2_field == 1 && SB1_field == 0)
        return MINCO;
    else
        return decode[SQ_field][STB_field];
}

void clearControlPulses()
{
    for(unsigned i=0; i<MAXPULSES; i++)
        glbl_cp[i] = NO_PULSE;
}

void assert(cpType* pulse)
{
    int j=0;
    for(unsigned i=0; i<MAXPULSES && j<MAX_IPULSES && pulse[j] != NO_PULSE; i++)
    {
        if(glbl_cp[i] == NO_PULSE)
        {
            glbl_cp[i] = pulse[j];
            j++;
        }
    }
}

void assert(cpType pulse)
{
    for(unsigned i=0; i<MAXPULSES; i++)
    {
        if(glbl_cp[i] == NO_PULSE)
        {
            glbl_cp[i] = pulse;
            break;
        }
    }
}

void get_CPM_A(int CPM_A_address)
{
    // EPROM address bits (bit 1 is LSB)
    // 1: register BR2
    // 2: register BR1
    // 3-6: register SG (4)
    // 7,8: register STB (2)
    // 9-12: register SQ (4)
    // 13: STB_01
    // 14: STB_02
}

```

```

//*****
// EPROM emulator
int SB2_field = (CPM_A_address >> 13) & 0x1;
int SB1_field = (CPM_A_address >> 12) & 0x1;
int SQ_field = (CPM_A_address >> 8) & 0xf;
int STB_field = (CPM_A_address >> 6) & 0x3;
int SG_field = (CPM_A_address >> 2) & 0xf;
int BR1_field = (CPM_A_address >> 1) & 0x1;
int BR2_field = (CPM_A_address >> 0) & 0x1;

// Decode the current instruction subsequence (gbl_subseq).
subseq gbl_subseq = instructionSubsequenceDecoder(SB2_field, SB1_field, SQ_field, STB_field);

static subsequence* subsp[] =
{
&SUB_TC0,      &SUB_CCS0,      &SUB_CCS1,      &SUB_NDX0,      &SUB_NDX1,      &SUB_RSM3,
&SUB_XCH0,     &SUB_CS0,       &SUB_TSO,      &SUB_ADO,      &SUB_MASK0,     &SUB_MPO,
&SUB_MP1,     &SUB_MP3,      &SUB_DV0,      &SUB_DV1,      &SUB_SU0,       &SUB_RUPT1,
&SUB_RUPT3,   &SUB_STD2,     &SUB_PINC,     &SUB_MINC,     &SUB_SHINC,0
};

// Clear old control pulses.
clearControlPulses();

// Get new control pulses for the current instruction subsequence.
if(gbl_subseq != NO_SEQ && // THIS TESTS OUT OK
SG_field >= TP1 &&
SG_field <= TP11)
{
subsequence* subseqP = subsp[gbl_subseq];
if(subseqP)
{
// index t-2 because TP1=2, but array is indexed from zero
controlStep& csref = subseqP->tp[SG_field-2];

brType b = (brType)((BR1_field << 1) | BR2_field);
controlSubStep& cssref = csref.substep[b];
if(cssref.br == NO_BR)
cssref = csref.substep[0];

cpType* p = cssref.pulse;
assert(p);
}
}

// Implement these here, because the instruction sequence decoder
// function is buried in the CPM-A ROM and so, identification of
// the sequences is not available outside CPM-A. CPM-C needs info
// on these 3 sequences.
switch(gbl_subseq)
{
case DV1:      assert(SDV1); break;
case MP1:      assert(SMP1); break;
case RSM3:     assert(SRSM3); break;
}

//*****
}

char* cpTypeString[] =
{
"NO_PULSE",

// OUTPUTS FROM SUBSYSTEM A
"CI", "CLG", "CLCTR", "CTR", "GP", "KRPT", "NISQ", "RA", "RB",
"RB14", "RC", "RG", "RLP", "RP2", "RO", "RRPA", "RSB", "RSCT",
"RU", "RZ", "R1", "R1C", "R2", "R22", "R24", "ST1", "ST2", "TMZ",
"TOV", "TP", "TRSM", "TSGN", "TSGN2", "WA", "WALP", "WB", "WGx",
"WLP", "WOVC", "WOVI", "WOVR", "WP", "WPx", "WP2", "WQ", "WS",
"WX", "WY", "WYx", "WZ",

// OUTPUTS FROM SUBSYSTEM A; USED AS INPUTS TO SUBSYSTEM B ONLY;
// NOT USED OUTSIDE CPM

```

```

//
"RSC", "WSC", "WG",

// OUTPUTS FROM SUBSYSTEM A; USED AS INPUTS TO SUBSYSTEM C ONLY;
// NOT USED OUTSIDE CPM
//
"SDV1", "SMP1", "SRSM3",

// EXTERNAL OUTPUTS FROM SUBSYSTEM B
//
"RA0", "RA1", "RA2", "RA3", "RA4", "RA5", "RA6", "RA7", "RA10", "RA11",
"RA12", "RA13", "RA14", "RBK", "WAO", "WA1", "WA2", "WA3", "WA10",
"WA11", "WA12", "WA13", "WA14", "WBK", "WGn", "W20", "W21", "W22", "W23",

// THESE ARE THE LEFTOVERS -- THEY'RE PROBABLY USED IN SUBSYSTEM C
//
"GENRST", "CLINH", "CLINH1", "CLSTA", "CLSTB", "CLISQ", "CLRP", "INH",
"RPT", "SBWG", "SETSTB", "WE", "WPCTR", "WSQ", "WSTB", "R2000"
};

// for debug purposes only
char* printControlPulses()
{
    static char buf[MAXPULSES*6];
    strcpy(buf, "");

    for(unsigned i=0; i<MAXPULSES && glbl_cp[i] != NO_PULSE; i++)
    {
        strcat(buf, cpTypeString[glbl_cp[i]]);
        strcat(buf, " ");
    }
    //if(strcmp(buf, "") == 0) strcat(buf, "NONE");
    return buf;
}

// return the EPROM word corresponding to the pulses
// in glbl_cp.
unsigned writeEPROM(int lowBit)
{
    unsigned EPROMword = 0x00; // no pulses; default
    for(unsigned i=0; i<MAXPULSES && glbl_cp[i] != NO_PULSE; i++)
    {
        int pulse = glbl_cp[i] - lowBit;
        if(pulse < 0 || pulse > 7)
            continue; // pulse is not in this EPROM
        EPROMword |= 0x01 << pulse;
    }
    // printf("%02X\n", EPROMword);
    //return EPROMword;

    // The CPM-A control signals are negative logic, so we need to
    // bit-flip the word. No signal is a 1, and an asserted signal is
    // a 0:
    return ((~EPROMword) & 0xff);
}

const unsigned agcMemSize = 0x3fff+1; // # of cells in a 16-bit address range

void writeEPROM(FILE* fObj, int lowBit)
{
    // Write an EPROM file using Motorola's S-Record format (s2f).

    // Some parameters that control file format. You can change maxBytes
    // without affecting anything else. 'addressBytes' is determined by
    // the chosen S-Record format.
    const int maxBytes = 20; // set limit on record length
    const int addressBytes = 3; // 24-bit address range
    const int sumCheckBytes = 1;

    const int maxdata = maxBytes - addressBytes - sumCheckBytes;

    int i=0; // current EPROM address
    int sumCheck = 0;
    while (i < agcMemSize)
    {

```



```

        // get dataByteCount; the number of bytes of EPROM data per record.
int dataByteCount = maxdata;
if(i + dataByteCount >= agcMemSize)
{
    dataByteCount = agcMemSize - i;
}
    // write record header (** 3 byte address assumed **)
int totalByteCount = dataByteCount + addressBytes + sumCheckBytes;
fprintf(fpObj, "S2%02X%06X", totalByteCount, i);
sumCheck = totalByteCount & 0xff;
sumCheck = (sumCheck + ((i & 0xff0000) >> 16)) % 256;
sumCheck = (sumCheck + ((i & 0x00ff00) >> 8)) % 256;
sumCheck = (sumCheck + ((i & 0x0000ff) >> 0)) % 256;

    // write data bytes into record
for(int j=0; j<dataByteCount; j++)
{
    get_CPM_A(i+j); // get CPM-A pulses for address i+j
int data = writeEPROM(lowBit); // convert pulses to EPROM format
fprintf(fpObj, "%02X", data);
sumCheck = (sumCheck + data) % 256;
}
    // terminate record by adding the checksum and a newline.
fprintf(fpObj, "%02X\n", (~sumCheck) & 0xff);

    i += dataByteCount;
}
    // write an end-of-file record here
i = 0; // use address zero for last record
sumCheck = 0x04; // byte count
sumCheck = (sumCheck + ((i & 0xff0000) >> 16)) % 256;
sumCheck = (sumCheck + ((i & 0x00ff00) >> 8)) % 256;
sumCheck = (sumCheck + ((i & 0x0000ff) >> 0)) % 256;
fprintf(fpObj, "S804%06X%02X", i, (~sumCheck) & 0xff);
}

```

```

void main(int argc, char* argv[])
{
    FILE* fpObj = 0;

    fpObj = fopen("CPM1_8.hex", "w");
    if(!fpObj)
    {
        perror("fopen failed for object file");
        exit(-1);
    }
    writeEPROM(fpObj, 1); // pulses 1-8
    fclose(fpObj);

    fpObj = fopen("CPM9_16.hex", "w");
    if(!fpObj)
    {
        perror("fopen failed for object file");
        exit(-1);
    }
    writeEPROM(fpObj, 9); // pulses 9-16
    fclose(fpObj);

    fpObj = fopen("CPM17_24.hex", "w");
    if(!fpObj)
    {
        perror("fopen failed for object file");
        exit(-1);
    }
    writeEPROM(fpObj, 17); // pulses 17-24
    fclose(fpObj);

    fpObj = fopen("CPM25_32.hex", "w");

```

```
if(!fpObj)
{
    perror("fopen failed for object file");
    exit(-1);
}
writeEPROM(fpObj, 25); // pulses 25-32
fclose(fpObj);
```

```
fpObj = fopen("CPM33_40.hex", "w");
if(!fpObj)
{
    perror("fopen failed for object file");
    exit(-1);
}
writeEPROM(fpObj, 33); // pulses 33-40
fclose(fpObj);
```

```
fpObj = fopen("CPM41_48.hex", "w");
if(!fpObj)
{
    perror("fopen failed for object file");
    exit(-1);
}
writeEPROM(fpObj, 41); // pulses 41-48
fclose(fpObj);
```

```
fpObj = fopen("CPM49_56.hex", "w");
if(!fpObj)
{
    perror("fopen failed for object file");
    exit(-1);
}
writeEPROM(fpObj, 49); // pulses 49-56
fclose(fpObj);
```

```
}
```